

Easy to build projects for everyone

Everyday ELECTRONICS

JAN 80
33E £.85


FREEZE-UPS • BURSTS • FLOODS
PROTECT YOUR HOME WITH THE

EE LOFT ALERT

**SPRING-LINE
REVERB UNIT**

MAINS ON/OFF TIMER

**RADIO CONTROL
RECEIVER**

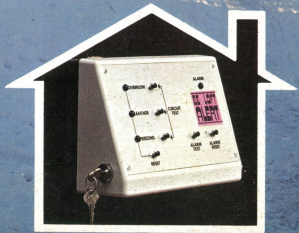

New 'L' series irons, designed to latest safety standards. Outstanding performance, lightweight and easy maintenance. New non-roll GRP safety handles. Ceramic and mica insulated elements enclosed in stainless steel shafts.

Fully earthed with screw connected 3-core leads. Interchangeable, non-seize iron-coated bits.

MODEL LC18 18 watts



Lightweight, high-performance iron for all soldering from calculators to T.V. sets. Fitted with 3.2 mm bit and complete with spare bits 1.6 mm, 2.4 mm and 4.7 mm. £7.89 including P & P and V.A.T. 240 volts standard but also available 12 and 24 volts.


MODEL LA12 12 watts



Similar to LC18 but with extra slim shaft and bits for fine work. Fitted with 2.4 mm bit and complete with spare bits 1.2 mm and 3.2 mm £6.69 including P & P and V.A.T. 240 volts standard, also available 6, 12 and 24 volts.

No. 3 SAFETY SPRING STAND for LC18 & LA12

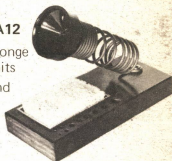Complete with sponge and location for spare bits £3.63 including P & P and V.A.T.




JOIN UP WITH LITESOLD.

C35S CORDLESS SOLDERING IRON

Built-in rechargeable batteries and twin spotlights. Heats in seconds. Solders safely anywhere. Complete with mains charger, sponge, 3 different tips and screwdriver. Best of its kind available. £23.93 including P & P and V.A.T.



NEW G100 SOLDERING GUN

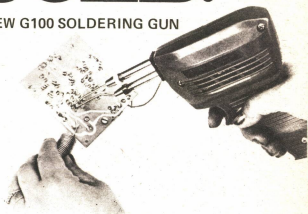

Safe 100 watt instant-heat, trigger operated tool. Heats and cools in seconds. With spotlight. For difficult or large joints, and shaping plastics. Ideal domestic and workshop tool. Complete with 2 spare tips, spanner, solder and flux £13.65 including P & P and V.A.T.

TRANSISTOR TESTER

Tests and identifies PNP or NPN devices both in or out of circuit. Two self-identifying leads, using coloured LED indicators, self-powered by PB3 battery £22.62 including Battery, P & P and V.A.T.



Order direct at these special mail order prices. Leaflets giving full information available on request from:

Light Soldering Developments Limited,
97/99 Gloucester Road, Croydon CRO 2DN
Telephone: 01-689 0574 Telex: 8811945

LITESOLD

LIGHT SOLDERING DEVELOPMENTS LIMITED

MAGENTA ELECTRONICS LTD.

E.E. PROJECT KITS

Make us **YOUR No. 1 SUPPLIER OF KITS AND COMPONENTS** for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Project kits include **ALL THE ELECTRONICS AND HARDWARE** you have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own **FREE COMPONENT IDENTIFICATION SHEET**. We supply—you construct. **PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED.** IF YOU DO NOT HAVE THE **INSTRUCTIONS** WHICH CONTAINS THE PROJECT—YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA—39p. each.

BABY ALARM. Nov. 79 £2.29
OPTO ALARM. Nov. 79 £3.36 inc. optional parts.
NEW I.W. RADIO TUNER. Nov. 79 £15.90 less dist.
3 FUNCTION GENERATOR. Nov. 79 £16.44 less post. case extra £7.18.
ONE ARMED BANDIT. Oct. 79 £19.39. case extra £3.18.
HIGH IMPEDANCE VOLTMETER. Oct. 79 £10.25.
LIGHTS ON REMINDER. Oct. 79 £4.62.
SIGNAL LEVEL INDICATOR. Oct. 79 £4.91 (intro).
UNIVERSAL OSCILLATOR. Oct. 79 £19.39.
VISOR CHARGER. Sept. 79 £16.95.
WATER TAP M.W. RADIO. Sept. 79 £5.95.
SIMPLE TRANSISTOR TESTER. Sept. 79 £2.95.
ELECTRONIC TUNING FORK. Aug. 79 £2.95. Suitable microphone + plug £1.59 extra.
WAKING TUNER. Aug. 79 £2.25.
POWER SUPPLY. Aug. 79 £8.94 inc. pcb.
FLAME WHISTLER. Aug. 79 £3.19.
TOUCH ON PLOT LIGHT. Aug. 79 £2.95.
QUIZ REFERENCE. Aug. 79 £5.81.
SOLDERING IRON BIT SAVER. July 79 £19.15.
VOLTAGE SPLITTER. July 79 £3.37.
DARKROOM TIMER. July 79 £2.41.
WATER LEVEL INDICATOR. July 79 £4.60.
TREMLO UNIT. June 79 £10.95.
ELECTRONIC CANNY. June 79 £4.95.
LOW COST METAL LOCATOR. June 79 £3.44.
Handle & coil former parts extra £4.95.
FLAME AMPLIFIER. June 79 £4.19.
QUAD SIMULATOR. May 79 £19.39.
INTRUDER ALARM. May 1979 £19.44.
500m. buzzer & amp and Loop Components.
SHORT WAVE CONVERTER. May 79 £19.39 inc. case.
THERMOSTAT "PHOTO" SOLUTIONS. May 79 £15.75. Less socket, bulb and grease.
FLAME INVERTER. April 79 £19.39.
TRANSISTOR TESTER. April 79 £2.95.
COIL BLEEPER. April 79 £3.36.
ONE TRANSISTOR RADIO. Mar. 79 £19.39. Ampifier + Headset. Less case. £4.84.
TIME DELAY INDICATOR. Mar. 79 £7.95.
VERSATILE POWER SUPPLY. Mar. 79 £9.95.
CHOKO WARNING DEVICE. Apr. 79 £7.95.
AUDIO MODULATOR. Feb. 79 £5.95 less case and pins.
CONVERTER. Feb. 79 £4.46.
THYRISTOR TESTER. Feb. 79 £2.95.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

3 BAND SHORT WAVE RADIO

Simple tri band covering 1-2.4MHz. Covers most amateur bands and short wave broadcast bands. Five controls—band, bandspread, reaction, wavechange and attenuator. Uses an internal 9v battery—very low current consumption. The 3 coils are all mounted on the pcb—selection is by a wavechange switch. Use with headphones or a crystal earpiece. Kit contains all the components required including the pcb and case. Instructions included with this kit. Headphones are not included—we recommend our high impedance mono headphones.

KIT £18-97

HEADPHONES EXTRA £3-28.

1980 ELECTRONICS CATALOGUE

MAGENTA'S CATALOGUE HAS BEEN SPECIALLY DESIGNED FOR E.E. READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR THE CONSTRUCTOR. CATALOGUE INCLUDES CIRCUIT IDEAS FOR YOU TO BUILD.

MAGENTA ELECTRONICS LTD.

EN12, 96 CALAIS ROAD, BURTON-ON-TRENT, STAFFS.

DE13 0UL. 0283-65435. 9-12. 25 MON.-FRI.

OFFICIAL ORDERS FROM SCHOOLS, UNIVERSITIES ETC. WELCOME.

MAIL ORDER ONLY.

ALL PRICES INCLUDE 15% VAT AND POST AND PACK CHARGE.
30% TO ORDERS UNDER £10.
QUIRIES MUST INCLUDE S.A.E.

MAGENTA gives you **FAST DELIVERY BY FIRST CLASS POST OF QUALITY COMPONENTS & KITS**. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—**HAVE YOU TRIED US?**

ONE-ARMED BANDIT

Oct 79
 Complete with 0-2" LED's and all components. £18-39.
 Case extra £3-98

CHASER LIGHTS

Sept 79
 Complete kit — with Case, plugs and sockets etc. £18-95

G. P. POWER SUPPLY

Feb 79
 0-20V 0-1A. Variable with calibrated VOLTMMETER and AMMETER.
 All components and Hardware £25-17.
 Case (horizontal & layout) £25-21 extra.

DOING IT DIGITALLY

Complete kit of top quality components as specified by **EVERYDAY ELECTRONICS**. Kit comes complete with free component identification sheets.

TUTOR DECK £23-84.
FIRST 5 months COMPONENTS £4-98.
COMPONENTS FOR PARTS 7, 8, 9 & 10 £19-95. Includes: photocells, I.C.'s, Resistors, Capacitors, thermistors, microphone, speaker, potentiometer etc.
PART 11 £2-73. PART 12 £3-19.
 Reprints—Part 1—78p other 39p each.

LOW COST METAL LOCATOR

E.E. June 79
 WE HAVE MADE UP A COMPLETE HARDWARE KIT FOR THIS PROJECT, WITH HANDLE, COIL FORMER AND SCREWS etc. Everything you need for the project, including electronics and case £19-39.
 Or separately:
 Electronics—Case £3-14.
 Hardware Kit £4-95.

EACH 80

NEW SERIES—ALL COMPONENTS IN STOCK NOW FOR FAST DELIVERY. All top quality components as specified by **Everyday Electronics**. Our kit comes complete with **FREE COMPONENT IDENTIFICATION SHEET**. Follow this educational series and learn about electronics—Start today! **SEND £22-95 for the TUTOR DECK and ADDITIONAL COMPONENTS PARTS 1-6.** All orders sent by **FIRST CLASS POST**. Our kit contains all the following parts:

TUTOR DECK: METER, BREADBOARD, TRANSFORMER, L.E.D.s, POTENTIOMETERS, SWITCHES, SPEAKER, PLUGS, SOCKETS, BATTERY CLIPS, WIRE, CABLE, FUSES, FUSEHOLDERS, KNOBS, ADDITIONAL COMPONENTS, PARTS 1-6, RESISTORS, PHOTOCELL, DIODES, CAPACITORS.

CASE WOODWORK KIT £4-98 extra. Complete kit for tutor deck woodwork, contains all the softwood, hardboard, ramin, panel pins, adhesive, screws, felt, strap-handle, and fixings. Cut to size and ready to assemble.

IDEAL SOLDERING EQUIPMENT FOR THE TEACH IN AND ELECTRONICS

ANTEX X25 SOLDERING IRON 25W £4-98
SOLDERING IRON STAND £2-03
SPARE BITS. Small, Standard, Large. 65p each.
SOLDER. Handy size 78p.

DESOLDER BRAID 60p
HOW TO SOLDER BOOKLET 12p
HEAT SINK TWEEZERS 15p.
SOLDER BOBBIN 30p
DESOLDER PUMP £6-98

SWING STORED TUNERS £6-98.
MULTIMETER TYPE 3 100,000 o.p.v. with transistor tester ranges £29-95.
WIRELESS INTERCOM 2 STATION £42-95.
SIREN. 12V 65.5V.
P.C.B. ASSEMBLY JIG £11-98.
P.C.B. ETCHING KIT £4-98.
A.M.-F.M. AIRCRAFT BAND PORTABLE RADIO £19-95.
WIRE STRIPPERS & CUTTERS £2-31.
ULTRASONIC TRANSDUCERS. £5-50 plus.
P.A. MICROPHONE coiled lead & switch £6-98.
STEREO MICROPHONE PAIR £10-95.
MULTIMETER TYPE 1. 1,000 o.p.v. with probes. 9" x 3" x 1" £24-95.
MULTIMETER TYPE 2. 20,000 o.p.v. with case and probes. 5" x 3" x 1" £14-25.
F.M. INDOOR AIRCRAFT 370p.
TELESCOPIC AIRLINE. 120 c.m. £2-98.
CRYSTAL MICROPHONE INSERT. 50p.
SPEAKERS MINIATURE. 8 ohm 50p. 64 ohm 80p. 50 ohm 41-38.
PILLOW SPEAKER. 8 ohm 95p.
6" ROUND SPEAKER. 8 ohm 5V. £2-28.
CABINET SPEAKER. 8 ohm. 5W. 5" speaker. Cabinet 10" x 7" x 4". £4-75.
RE-ENTRANT HORN SPEAKER. 8 ohm 5W. 10" £2-97.
SARPIECES. Crystal 40p. Magnetic 15p.
STETHOSCOPE ATTACHMENT. Fits all stethoscopes. 40p.
BUZZER. 6V 80p. 12V 85p.
MONO HEADPHONES. 2K. Padded. Superior. Sensitive. 40p.
STEREO HEADPHONES. 8 ohm. Padded. 44-35.
INTERCOM. Station. Desk. £7-48.
MICROPHONE DYNAMIC. 600 ohm. Cassette type. £1-38.

DENTISTS MIRROR. Adjustable. £2-44.
JEWELLERS EYGLASS. £1-05p.
TRIPLE MAGNIFIER. £1-84.
HAND MAGNIFIER. 3" Lens. £3-43.
SPECTACLE MAGNIFIER. Clips on to spectacle frame. £4-65.
ILLUMINATED MAGNIFIERS. 1 1/2" lens £1-16. 3" lens £2-98.
POCKET TOOL SET. 21pc. £14-98.
SCREWDRIVER SET. Six pieces. £12-98.
Q MAX PUNCH. 1" £2-14. 1 1/2" £2-39. 1 1/2" £2-41. 1 1/2" £2-50.
12V 250V. Hand or stand use. £19-95. Stand £8-98.
CAPACITANCE SUBSTITUTION BOX. Nine values. 100p-0.22µf. £2-98.
QUICKEST. Mains connection. £4-41.
PLUG IN POWER SUPPLY. 6, 7.5-9V. £3-90M. £4-65.
SPRINGS—SMALL. 10 Ass'd. £1-98.
CROC CLIP TEST LEAD SET. 10 leads with 30cm chrome gold. £1-48.
DIMMER SWITCH. 240V. 800W. £4-48.
TRADITIONAL STYLE BELL. 3-4V. 70mm chrome gold. £1-98.
UNDERDECK BELL. 4-10V. Smart. Dlx. 70mm. £2-27.
TOWERS INTERNATIONAL TRANSISTOR SELECTOR. New edition. £4-94.
F.M. TUNER CHASSIS. 8-10MHz. 9V dc. £2-49.
MORSE KEY. High speed. £2-63.
PANEL METERS. 60 x 45mm. Modern style. 500uA, 100uA, 1mA, 15V dc. £2-48.
NIGHT LIGHT. Plug type. £1-08.
CONNECTING WIRE PACK. 5 x Syd. cond. 100cm. £1-98.
VERO SPOT FACE CUTTER. £1-09.
VERO PIN INSERTION TOOL. 0-1" £1-98.
RESISTOR COLOUR CODE CALCULATOR. 21p.

SEIKO MEMORY BANK

Calendar watch M354
Hours, mins, secs.
Month, day, date in
12 or 24 hour format
all indicated continuously.
Monthly calendar display
month, year and all dates
for any selected month over
80 year period.
Memory bank function.
Any desired dates up to 11
can be stored in advanced.
2 year battery life.
Water resistant.
Metac Price



M11

£79.50

SEIKO Alarm Chronograph

With WEEKLY Alarm.
Hours, mins, secs, month,
date, day, am/pm.
Weekly alarm - can be set
for every day at designated
time e.g. 6.30 am on Mon,
Wed and Friday.
Alarm set time displayed
above time of day.
Full stopwatch functions,
laptime, split etc.



M10

£89.95

SEIKO Melody Alarm Chronograph

Chiming Alarm,
plus chrono.
Hours, mins, secs, date,
day, 24 hour alarm, 12
hour chronograph, 1/10th
secs, Laptime, Back light.
Stainless steel, mineral
glass.



M19

METAC PRICE

£92.95

SEIKO Calculator Watch

Full specification
calculator with
memory, plus multi
function watch.
Hours, mins, secs,
day, date, backlight.
Automatic calendar.
Long life battery.



M27

£99.95

CASIO CHRONO 95QS-3LB

Stainless steel case,
water resistant to 66 feet.
Hours, mins, secs, am/pm,
year, month, date, day.
Auto-calendar
pre-programmed
until the year 2029.
12/24 hour. Stopwatch
function.
Range 7 hours, 1/100 sec.
(Mode) Net time/lap-time/
1st-2nd place times.
Dual time function.
Accuracy 15 secs per month.
Battery life approx 4 years.



M22

£22.95

CASIO LADIES 86CL-23B-1

Elegant slim line.
Stainless steel bracelet,
fully adjustable.
Hour, mins, 10 sec symbol
second by flash, am/pm.
Month, date, day.
Auto-calendar preprogrammed
for 28th day in Feb.
Accuracy per month 15 secs.
Battery life approx 15 months.



M23

£29.95

CASIO F-200 Sports Chrono

Attractive Mans watch
in black resin with
mineral glass.
Hours, mins, secs, am/pm.
Month, date,
alpha-numeric day.
Auto-calendar set
28th Feb.
Stopwatch working
range 1 hour,
with 1/100 sec. Mode.
Net Time/lap/time/
1st-2nd place times.
Accuracy approx 15 secs
per month.
Battery-12 months.



M24

£14.95

CASIO ALARM CHRONO 81CS-36B

Hours, mins, secs, day,
and also day, month and year
perpetual automatic calendar.
100th sec chronograph to
7 hours.
Net time/lap/time/1st
and 2nd place times. User
optional 12/24 hr display. 24
Alarm. User optional.
hourly chime.
Backlight, mineral glass,
stainless steel.
Water resistant to
100ft.
Battery life approx 4 years.



M25

£34.95

BELTIME Chronograph

(8-Functions)
Hours, mins, secs,
day, date, month,
interchange feature,
automatic calendar,
backlight, Net
time/lap/time.
Stainless steel bracelet.
Battery life 1 year.



M34

£14.95

BELTIME Multi Alarm

28 Functions
Hours, mins, secs,
date, day.
Alarm, chronograph,
Light.
Watch 8 Functions,
Alarm 4 functions,
chronograph 17
functions.
Stainless steel
bracelet.



M35

£29.95

CASIO F-8C 3 Year Battery life.

Hours, mins, secs,
am/pm, date, day.
Auto calendar set
28th Feb.
Stopwatch function.
Accuracy 15 secs per
month. Battery life
approx 3 years.



M36

£9.95

CASIO CALENDAR 200 47CS-23B-1 Black. Stainless steel.

Hours, mins, 10 second
symbol, second (by flash),
am/pm. Month, day, date.
Auto-calendar set from
1901 to 2009.
Full month calendar display.
Dual time function.
Accuracy 10 secs per
month. Battery life
approx 15 months.



M37

£59.95

MELODY Multi Alarm Chronograph

Hours, mins, secs,
Day, Date, Count-
down alarm,
Dual time zone,
1/100th sec
stopwatch.
Lap/split time,
1st and 2nd place
times, Melody test
function.



M30

£26.95

DUAL TIME-ALARM CHRONOGRAPH

Incorporating module
of world famous
Japanese watch
manufacture.
Hours, mins, secs,
days of week, month,
day and date,
24 hour alarm,
12 hour chronograph,
1/10th sec.
lap time, Back light,
stainless steel case
and bracelet,
Mineral glass,
Battery hatch,
long life battery.



M12

£35.00

PICOQUARTZ Microprocessor Alarm Chronograph

Multilanguage-day of
the week can be set
to English, French,
German, Italian or
Spanish.
China - every full
hour combined with a
response signal,
beeping at every
pressing of the
functions.
Can be switched off.
12-24 hour format.
Backlight.
Chrono - full, full scale
chrono with lap
counting hours up to
24 hrs. Mins, secs,
1/100th secs.
Two Alarm systems.
Two time zones.



M32

£37.95

SEIKO CHRONOGRAPH

Hours, mins, secs
and day of the week.
Month date and
day of the week.
Stopwatch display -
Hours, mins, secs
up to 12 hours
(mins, secs, 1/100 secs
up to 20 minutes).
Lap timing.
Continuous time
measurement of two
competitors.
Stainless steel,
mineral glass.



M33

£56.00

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

QUARTZ LCD 5 Function

Hours, mins, secs,
month, date, auto
calendar, back-light,
quality metal
bracelet.

£6.65

Guaranteed same
day despatch.
Very slim,
6mm thick.



M1

SOLAR QUARTZ LCD 5 Function

Genuine solar panel
with battery back-up.
Hours, mins, secs, day,
date. Fully adjustable
bracelet. Back-light.
Only 7mm thick.

£8.65

Guaranteed same day
despatch.



M2

QUARTZ LCD 11 Function

6 digit, 11 functions.
Hours, mins, secs, day,
date, day of week.
1/100th, 1/10th, secs.
10X secs, mins.
Split and lap modes.
Back-light, auto calendar.
Only 8mm thick.
Stainless steel bracelet
and back.
Adjustable bracelet.
Metac Price



£10.65 Thousands sold!
Guaranteed same day despatch.

M3

QUARTZ LCD ALARM 7 Function

Hours, mins, secs,
month, date, day.
6 digits, 3 flags plus
continuous display
of day and date or
seconds. Back-light
Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

MULTI ALARM 6 Digits 10 Functions

- Hours, mins, secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.



£18.65

M5

FRONT-BUTTON Alarm Chrono Dual Time

6 digits, 5 flags,
22 functions.
Constant display of
hours and mins, plus
optional seconds or
date display.
AM/PM indication, month, date.
Continuous display of day.
Stop-watch to 12 hours.
59.9 secs. in 1/10 second steps.
Split and lap timing modes.
Dual time zones.
Only 8mm thick.
Back-light. Fully adjustable
open bracelet.
Guaranteed same day despatch



£22.65

M6

SOLAR QUARTZ LCD Chronograph with Alarm

Dual Time Zone
Facility
6 digits, 5 flags,
22 functions.
Solar panel with
battery back-up.
6 basic functions.
Stop-watch to 12 hours
59.9 secs. in 1/10 sec.
steps.
Split and lap timing modes.
Dual time zones.
Alarm. 8mm thick. Back-light.
Fully adjustable bracelet.



£27.95

M7

ALARM CHRONO with 9 world time zones

- 6 digits, 5 flags.
- 6 basic functions.
- 9 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours
59.9 secs.
- in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.



£29.65

M8

SOLAR QUARTZ LCD Chronograph

Powered from solar
panel with battery back-up.
6 digit, 11 functions.
Hours, mins, secs, day,
date, day of week.
1/100th, 1/10th, secs.
10X secs, mins.
Split and lap modes.
Back-light, auto
calendar. Only 8mm
thick.
Stainless steel bracelet
and back.
Adjustable bracelet.
Metac Price



£13.65

Guaranteed same day despatch.

M9

QUARTZ LCD Ladies Day Watch

Only 25 x 20mm and
6mm thick.
Hours, minutes, seconds,
date, day, back-light and
auto calendar.
Elegant metal
bracelet in silver or
gold fully adjustable
to suit very slim
wrists.
State colour preference.



£9.95

Guaranteed same day despatch.

M15

QUARTZ LCD Ladies Fashion Watch

Elegant bracelet in
bronze/gold finish or
silver colour.
Hours, mins, secs, day,
date, back-light and auto
calendar. Adjustable for
the slimmest of wrists.
State colour preference.



£14.95

Guaranteed same day despatch

M17

QUARTZ LCD Ladies Cocktail Watch

Highly functional watch
which also suits those
special occasions.
Beautifully designed
with a very thin bracelet
which retains strength as
well as elegance.
Hours, mins, secs, day, date,
back-light and auto-calendar.
Bracelet fully adjustable to
suit slim wrists.
State gold or silver finish.




£19.95

Guaranteed same day despatch

M18

HANIMEX Electronic LED Alarm Clock

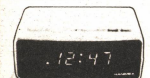

Features and Specification:
Hour/minute display. Large LED display with
p.m. and alarm on indicator. 24 hours alarm with
on/off control. Display flashing for power loss
indicator. Repeatable 9 minute snooze. Display
brightness modes control. Size: 5.15" x 3.93" x
2.36" (131mm x 11mm x 60mm)
Weight: 1.43 lbs (0.65 kg)

AC power 220V.

£10.20 Thousands sold!

Mains operated.

Guaranteed same
day despatch.

M13

EXECUTIVE ALARM WATCH

6 Functions plus Alarm:
Conference signal.
5 minute snooze alarm.
Conference signal sounds
4 secs. before main alarm
to give advance warning and
an option to cancel.
Snooze sounds 5 mins.
after main alarm and is
always preceded
by the conference signal.



£14.95

M60

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and order details clearly, enclose 40 pence per single item for post and packing or the amount stated in the advert. All products carry 1 year written guarantee and full money-back 10 day reassurance. Battery fitting and electronic calibration service is available to customers at any Metac shop. All prices include VAT currently at 15%.

Metac Wholesale:

Trade enquiries - send for a complete list of prices for all the goods advertised plus many more not shown also minimum order details.
Telephone orders: Credit card customers can telephone orders direct to Davenport (03272) 76545 or Edgeware Rd. 01-723 4753 24 hours a day.



Service Enquiries 03272-77659
CALLERS WELCOME Shops open 9-30am-6.00

MACY QUARTZ ANALOGUE

Automatic Calendar
Day and Date
infinite bracelet.
This mins watch has
elegance as well as the
robust appearance provided
by a watch with traditional
features. Accuracy is
provided by a quartz
crystal powered by a
long life miniature
battery.



£24.95

M21

Metac: price breakthrough for an Alarm
Chronograph with Dual Time
only

£18.95

OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- **CALENDAR FUNCTIONS.** include the date and day in each time zone.
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
- On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!


Guaranteed same day despatch. **M16**

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

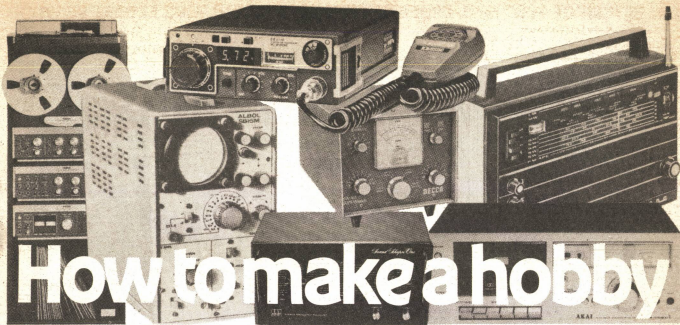South of England
327 Edgeware Road
LONDON W.2
Telephone: (01) 723 4753



How to make a hobby

The opportunities in electronics, today, and for the future are limitless — throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics — especially for the servicing of radio, TV and all associated equipment — can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.

We give modern training courses in all fields of electronics — practical D.I.Y. courses — courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.


All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.

and a career.


COURSES AVAILABLE

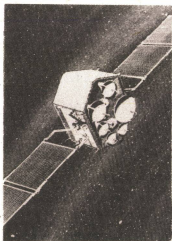- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free 32 page
Colour Booklet.

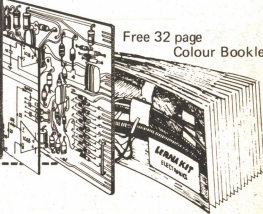

WE ARE AN INTERNATIONAL SCHOOL
SPECIALISING IN ELECTRONICS
TRAINING ONLY AND HAVE OVER
40 YEARS EXPERIENCE IN THIS
SUBJECT.

EEA/1/80

NAME
ADDRESS

Block Caps Please

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO and
ELECTRONICS SCHOOL**

P.O. Box 156, Jersey,
Channel Islands.

Send your orders to:-
DEPT. EE1, PO BOX 6, WARE, HERTS. Tel: 0920-3182
Visit our NEW shop: 3 BALDOCK ST, WARE HERTS Telex: 817861

EXPERIMENTOR BREADBOARDS

FROM **CSC**

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboard of any size.

All EXP breadboards have two bus-bars as an integral part of the board. If you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP-4B.

EXP.325. The ideal breadboard for 1 chip circuits.
 Accepts 8, 14, 16 and up to 22 pin IC's.
ONLY £1-70



EXP.350. £3-73
 270 contact points with two 20-pin bus-bars.



EXP.300. 550 contacts with two 40-pin bus-bars.
£6-13



EXP.650 for Micro-processors. **£3-83**



EXP.4B. More bus-bars.
£2-45
 ALL EXP.300 Breadboards mix and match with 600 series.



ANTEX IRONS

- 1943 15 watt quality soldering iron with 3/32" bit **£4-88**
- 1947 Replacement element for 1943 **£2-18**
- 1944 Iron coated bit 3/32" for 1943 **£0-53**
- 1945 Iron coated bit 1/8" for 1943 **£0-53**
- 1946 Iron coated bit 3/16" for 1943 **£0-53**
- 1948 18 watt iron with iron coated bit **£4-59**
- 1952 Replacement element for 1948 **£2-18**
- 1949 Iron coated bit 3/32" for 1948 **£0-53**
- 1950 Iron coated bit 1/8" for 1948 **£0-53**
- 1951 Iron coated bit 3/16" for 1948 **£0-53**
- 1951 X25 25 watt iron, ceramic shaft and another shaft of stainless steel to ensure strength **£4-88**
- 1935 Replacement element for 1931 **£1-84**
- 1932 Iron coated bit 1/8" for 1931 **£0-57**
- 1933 Iron coated bit 2/16" for 1931 **£0-57**
- 1934 Iron coated bit 3/32" for 1931 **£0-57**
- 1953 SK1 soldering kit - contains 15 soldering iron with 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to Solder' **£6-38**
- 1939 23 iron stand made from high grade bakelite chrom plated steel spring, suit all models - includes accommodation for six bits and two sponges to keep the iron bits clean **£1-86**
- 1724 Model MLX as X25 iron but 12 volts **£5-29**

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA110	£0-09	BY105	£0-25	BV211	£0-52	OA90	£0-11
AA120	£0-09	BY106	£0-25	BV212	£0-46	OA91	£0-11
AA129	£0-09	BY107	£0-25	BV213	£0-46	OA92	£0-11
AA130	£0-09	BY114	£0-25	BV216	£0-47	OA182	£0-11
AA213	£0-17	BY124	£0-25	BV217	£0-41	OA200	£0-09
BA100	£0-11	BY126	£0-17	BV218	£0-41	OA202	£0-09
BA102	£0-37	BY127	£0-18	BV219	£0-41	SO10	£0-07
BA148	£0-17	BY128	£0-18	GA5	£0-09	SD19	£0-07
BA155	£0-16	BY133	£0-24	GA6	£0-09	IN344	£0-06
BA172	£0-17	BY164	£0-08	GA9	£0-09	IN345	£0-06
BB104	£0-17	BY176	£0-08	GA9	£0-11	IN316	£0-07
BAK13	£0-08	BV206	£0-34	GA81	£0-11	IN1448	£0-07
BAK16	£0-09	BV210	£0-51	GA85	£0-11	IS44	£0-06
						IS920	£0-07

CASES AND BOXES

INSTRUMENT CASES in two sections vinyl covered top and sides, aluminium bottom, front and back.				
No.	Length	Width	Height	Price
155	6in	5 1/2in	2in	£1-72
156	6in	1 1/2in	3in	£1-11
157	6in	4in	1 1/2in	£1-79
158	6in	4in	2 1/2in	£1-43
ALUMINIUM BOXES made from bright, all, folded construction each box complete with half inch deep lid and screws.				
No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0-85
160	4in	4in	1 1/2in	£0-85
161	4in	2 1/2in	1 1/2in	£0-85
162	5 1/2in	2 1/2in	1 1/2in	£0-85
163	4in	2 1/2in	2in	£0-87
164	5 1/2in	2 1/2in	2in	£0-87
165	7in	5in	2 1/2in	£1-43
166	8in	6in	3in	£1-82
167	6in	4in	1 1/2in	£1-18
SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front - strong construction easily accessible.				
No.	Length	Width	Height	Price
168	2 1/2in	5 1/2in	1 1/2in	£3-45
169	2 1/2in	4in	1 1/2in	£1-11
VERO plastic case box. These boxes consist of top and bottom sections which include fixings points for horizontal mounting PCB boards. Each case is made of two sections held together by four screws which enter through the base and are concealed by plastic feet.				
No.	Length	Width	Height	Price
170	140mm	40mm	205mm	£4-14
171	140mm	75mm	205mm	£5-85
172	140mm	110mm	205mm	£6-00

SPECIAL OFFERS

MINI-DRILL 12v hand held battery-operated mini drill, 7,500 r.p.m. Collect chuck. Ideal for drilling printed circuits or metal making No. 1402 **£7-79**

TRANSFORMER 240v Primary 0-20v $\pm$ 2A Secondary. By removing 5 turns for each volt from the secondary winding, any voltage up to 20v $\pm$ 2A is obtainable. Ideal for the experimenter. No. 2042 **£1-50** + 86p. P & P

ANTEX MLX Soldering Iron. Study 25 watt iron complete with: 41 metres of 2-core cable. Works off a 12 volt battery. Ideal for Car, Boat, Caravan. No. 1724. **£5-29**

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors assorted into the following groups.

16213	60 mixed 1/8w 100ohms-820ohms	£0-89
16214	60 mixed 1/8w 10Kohms-82Kohms	£0-89
16215	60 mixed 1/8w 10Kohms-83Kohms	£0-89
16216	60 mixed 1/8w 100Kohms-820Kohms	£0-89
16217	40 mixed 1/2w 10Kohms-820ohms	£0-89
16218	40 mixed 1/2w 10Kohms-82Kohms	£0-89
16219	40 mixed 1/2w 10Kohms-82Kohms	£0-89
16220	40 mixed 1/2w 100Kohms-820Kohms	£0-89

CERAMIC PAKS

16160	24.3 or each value 22p 27p 33p 39p 47p 56p	£0-89
16161	24.3 or each value 100p 120p 150p 180p 220p 270p 330p	£0-89
16162	24.3 or each value 470p 560p 680p 1000p 1500p 2200p 3300p	£0-89
16163	24.3 or each value 4700p 6800p 01uf 015uf 022uf 033uf 047uf	£0-89

ELECTROLYTIC PAKS

16201	values from 47mfd - 10mfd	£0-89
16202	values from 10mfd - 100mfd	£0-89
16203	values from 100mfd - 680mfd	£0-89

COMPONENT PAKS

16164	200 resistors mixed value approx (count by weight)	£0-89
16165	150 capacitors mixed value approx (count by weight)	£0-89
16167	15w resistors mixed values	£0-89
16168	5 pieces assorted ferrite rods	£0-89
16169	2 turning gauges MW LV VHF	£0-89
16170	1 pack wire 50 metres assorted colours single strand	£0-89
16171	10 reed switches	£0-89
16172	3 micro switches	£0-89
16173	15 assorted pins	£0-89
16175	30 paper condensers - mixed values	£0-89
16176	20 electrolytic tanks, types	£0-89
16177	10 assorted hardware - nuts, bolts gromets etc	£0-89

BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	40p
BP14	2nd Book Transistor Equiv & Subs	£1-10
BP22	50 Circuits for Gem/Silicon Diodes	75p
BP24	52 Projects Using IC741 for Equiv	75p
BP26	Radio Antenna Book Long Distance	85p
BP27	Client Chart of Radio Electronic	85p
BP28	Recruitment & Training Symbols	85p
BP32	Build Metal & Treasure Location	85p
BP34	Practical Radio & Television	95p
BP35	Handbook of IC Audio Amplifier & Power Amplifier Construction	95p
BP36	50 Circuits for Gem/Silicon Diodes	95p
BP37	50 Field Effect Trans Projects	£1-10
BP39	Digital IC Equiv & Pin Connection	£1-25
BP40	Linear IC Equiv & Pin Connection	£2-50
BP41	50 Simple LED Circuits	£2-75
BP42	How to make Walk-Talkies	£1-25
BP44	IC 555 Timer Projects	£1-45
BP45	Projects on Opto-electronics	£1-25
BP46	Radio Circuits Using IC's	£1-35
BP47	Mobile Discharge Handbook	£1-35
BP48	Electronic Projects for Beginners	£1-35
BP49	Popular Electronic Projects	£1-45
BP50	IC LM3900 Projects	£1-35
BP51	Radio Station Guide	£1-45
BP60	Call Design & Construction Manual	85p
BP202	Handbook of Integrated Circuits	75p
BP205	1st Book Hi-Fi Speaker Enclosures	75p
BP213	Circuits for Model Railways	85p
BP215	Shortwave Cables & Gear for Experiments & Radio Hobbies	85p
BP216	Electronic Gadgets & Games	85p
BP217	Solid State Power Supply Handbook	85p
BP221	28 Tested Transistor Projects	85p
BP222	Short-wave Receivers for Beginners	85p
BP223	50 Projects in Digital IC's	85p
BP224	50 CMOS IC Projects	85p
BP225	A Practical Introduction to Digital IC's	85p
BP226	Build Advanced Short-wave Receivers	£1-20
BP227	Beginners Guide to Building Electronic Projects	£1-25

REGULATORS

Positive	Price	SILICON 1 amp		Price
1A7805 T0220	£0-85	Type	No.	
1A7812 T0220	£0-85	50v RMS	BR1/50	£0-23
1A7815 T0220	£0-85	100v RMS	BR1/100	£0-28
1A7824 T0220	£0-85	200v RMS	BR1/200	£0-29
1A7818 T0220	£0-85	400v RMS	BR1/400	£0-41

Negative					
1A7905 T0220	£0-92	SILICON 2 amp			
1A7912 T0220	£0-92	Type	No.	Price	
1A7915 T0220	£0-92	50v RMS	BR2/50	£0-52	
1A7924 T0220	£0-92	100v RMS	BR2/100	£0-55	
1A7818 T0220	£0-92	200v RMS	BR2/200	£0-60	
17223 14 pin ON	£0-52	400v RMS	BR2/400	£0-67	
1A723C T089	£0-52	1000v RMS	BR2/1000	£0-78	
1A7200V T033	£0-52				

CASSETTES

/no. 3193		30 min lettertape	Type		No.	Price
		EO-38	50v RMS		BR10/50	£1-50
/no. 301		Dindy C60 tape	200v RMS		BR10/200	£1-70
		EO-41				
/no. 302		Dindy C90 tape	SILICON 25 amp			
		EO-52	Type		No.	Price
/no. 303		Dindy C120 tape	50v RMS		BR25/50	£1-80
		EO-75	200v RMS		BR25/200	£2-20

TRIACS

2 amp	T05 case		10 amp		
volts	No.	Price	volts		
100	TR12A/100	£0-36	100	TR110A/100	£0-88
200	TR12A/200	£0-59	200	TR110A/200	£1-06
400	TR12A/400	£0-82	400	TR110A/400	£1-29

6 amp			10 amp		
vols			vols		
100	TR16A/100	£0-89	400	TR110A/400P	£1-29
200	TR16A/200	£0-70		DIACS	
400	TR16A/400	£0-88		BR100	£0-23 D32 £0-23

ZENER DIODES

400 mw (BY88) D007. Glass encapsulated range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v.

1w-1.5w Plastic and metal encapsulated. Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 56v, 62v, 68v, 75v, 82v, 91v, 100v.

10w Metal stud type S010 case. Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 56v, 62v, 68v, 75v, 82v, 91v, 100v.

METAL FOIL CAPACITOR PAKS

16204 - Containing 50 metal foil capacitor leaf Mullard C280 series - Mixed values ranging from 0.1uf - 2.2uf. Complete with identification sheet. **£1-38**



EDITOR

F. E. BENNETT

ASSISTANT EDITOR

B. W. TERRELL B.Sc.

PRODUCTION EDITOR

D. G. BARRINGTON

TECHNICAL SUB-EDITOR

S. E. DOLLIN B.Sc.

ART EDITOR

R. F. PALMER

ASSISTANT ART EDITOR

P. A. LOATES

TECHNICAL ILLUSTRATOR

D. J. GOODING

EDITORIAL OFFICES

Kings Reach Tower,
Stamford Street,
London SE1 9LS
Phone: 01-261 6873

ADVERTISEMENT MANAGER

R. SMITH
Phone: 01-261 6671

REPRESENTATIVE

N. BELLWOOD
Phone: 01-261 6865

CLASSIFIED MANAGER

C. R. BROWN
Phone: 01-261 5762

MAKE-UP AND COPY DEPARTMENT

Phone 01-261 6615

ADVERTISEMENT OFFICES

Kings Reach Tower
Stamford Street,
London SE1 9LS

Projects... Theory... and Popular Features ...

No doubt some rueful remembrances of last winter will be awakened by this month's cover picture. Hopefully we shall not suffer the same severe and treacherous conditions in the opening months of '80. But there's no knowing, so it will be prudent to emulate the Boy Scouts and be prepared. Which leads us to the *Loft Alert*.

Apart from fire, flooding is probably the most frightening and damaging catastrophe that can happen to our homes. Extensive flooding can occur because quite small defects such as bursts in pipes or frozen ball cocks are undetected in sufficient time to take remedial action.

To be forewarned is to be forearmed. Hence the importance of our *Loft Alert*. The wise householder will build and instal this monitoring system without delay. Then regardless of the severity of the winter, the occupants can at least be relieved of anxiety concerning the state of things up a'loft.

As will be immediately apparent, the usefulness of this device is by no means limited to the winter months. Any time of the year defects or malfunctioning of parts in the water system can occur, which could lead to a disastrous situation.

A further reassuring feature provided by our *Loft Alert* is an instant "system check" facility. And being

battery operated it is entirely independent of the mains supply.

As from next month the price of EVERYDAY ELECTRONICS will be increased to 50p. Considering that you could pay this sum for a mere Christmas or birthday card, there can be no question that EE is value for money. Nevertheless we realise any increase could be a serious blow to the younger reader. If so, we suggest an approach to Dad for a subsidy. It should not be difficult to convince him that his investment will be returned with interest in the form of useful projects for the home in the course of the coming year.

As we leave '79 and enter '80, all of us on EVERYDAY ELECTRONICS thank our readers for your support and encouragement as often expressed in your letters to us.

Best wishes for the New Year.

Fred Bennett

Our February issue will be published on Friday, January 18. See page 27 for details.

Readers' Enquiries


We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

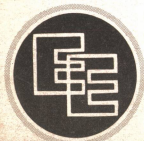All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



Everyday ELECTRONICS

VOL. 9 NO. 1

JANUARY 1980

CONSTRUCTIONAL PROJECTS

EE LOFT ALERT	Early warning of leaks, bursts and frosts by S. E. Dollin B.Sc.	12
UNIBOARD: 3—9V POWER SUPPLY	Designed specifically for Uniboard projects by A. R. Winstanley	20
MAINS ON/OFF TIMER	Up to 12 hours delay by A. R. Winstanley	28
EE RADIO CONTROL SYSTEM	Part 3: The Receiver by L. Armstrong, H. Dickinson and W. Wilkinson	34
SPRING-LINE REVERB UNIT	An exciting sound effect by R. A. Penfold	46

GENERAL FEATURES

EDITORIAL		10
SHOPTALK	Retail news, products and component buying by Dave Barrington	19
TEACH-IN 80	Part 4: The diode and rectification by S. R. Lewis B.Sc.	22
CROSSWORD NO. 23	by D. P. Newton	26
JACK PLUG AND FAMILY	Cartoon by Doug Baker	40
SCHOOL REPORT	Electronics in schools'	41
COUNTER INTELLIGENCE	A retailer comments by Paul Young	42
THE ADVENTURES OF TANTY BEAD	Cartoon by Matthew Read	42
EVERYDAY NEWS	What's happening in the world of electronics	44
FOR YOUR ENTERTAINMENT	Singing lights, frozen picture and Queen's English	52
SYNTHESISERS EXPLAINED—2	Filters and phasing	54
READERS' LETTERS	Your news and views	60
SQUARE ONE	Beginners Page: Components	61
PROFESSOR ERNEST EVERSURE	The Extraordinary Experiments of. by Anthony J. Bassett	62
RADIO WORLD	A commentary by Pat Hawker	64

Back Issues

Certain back issues* of EVERYDAY ELECTRONICS are available worldwide price 70p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

* Not available: October 1978 to July 1979.

Binders

Binders to hold one volume (12 issues) are available from the above address for £3.75 (home and overseas) inclusive of postage and packing. Please state which Volume.

Subscriptions

Annual subscription for delivery direct to any address in the UK: £8.50, overseas: £25.50. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613 Kings Reach Tower, Stamford Street, London SE1 9LS.

©IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

**OUR
REGULAR
FEATURE
FOR
BEGINNERS**

Is on page 61

SQUARE
one

FREEZE-UPS • FLOODS • BURSTS



AVOID THESE HAZARDS WITH OUR EE LOFT ALERT

By S. E. Dollin, B.Sc.

THE Loft Alert is an electronic warning system designed to warn the householder of an overflowing water tank, burst or leaking water pipes, and also the approach of freezing conditions. It consists of three sensing circuits which, when activated, give a visible and audible warning and shows which channel has been activated so that remedial action may be taken quickly before great damage is done.

An important feature of this unit is the fact that it is battery operated making it immune from the mains power failures that are possible during the winter months when this sys-

tem will be most needed. This also makes installation very much easier and safer. Provision is made for an extension warning device or lamp which can be mains or battery operated.

PRINCIPLE OF OPERATION

The system can be broken up into several distinct stages. When a fault, say a burst pipe, is detected, this produces a voltage which is fed to the appropriate latching circuit. This has the effect of lighting an l.e.d. and applying a "high" input to the on gate which results in its output going

high. This arrangement is necessary to prevent sensor circuits interacting and interfering with each other.

The output of the on gate is fed via a voltage clamp circuit to the alarm circuit.

This voltage clamp (TR1) is designed to keep the output from the on gate firmly at 0V when in the off condition. This is necessary as pin 4 of the following astable multivibrator must be kept at 0V to prevent it turning on when no alarm signal is present, since the output from the on gate is a little above 0V in its low state.

When the astable is running (pin 4 high) the associated l.e.d. flashes until the alarm condition is removed and the latch reset.

The alarm signal (stepping clamp voltage) is also processed to produce a trigger pulse for the monostable which energises a relay. The relay contacts supply power to an audible warning device for a length of time. This alarm is muted when the monostable times out.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Loft Alert is shown in Fig. 1. The sensors for water overflow and leakage are identical in principle. Water bridges two contacts and causes a signal voltage to be applied via resistors R1 (R9) to the gate of thyristors CSR1 (CSR5). When this happens the thyristor conducts and the cathode rises to a little below battery voltage thus illuminating D1 (D5).

The operation of the freezing detector is slightly different but the effect is to produce a voltage at the thyristor gate when the temperature drops to, or approaches freezing.

The resistor R2, potentiometer VR1 and thermistor RTH1 form a potential divider chain. At room temperature the thermistor has a low resistance of about 1 kilohm. This means that the voltage on the gate of CSR2 is near to zero. However as the temperature falls the resistance of thermistor RTH1 rises causing the voltage across it to rise. At a certain thermistor resistance the voltage across the thermistor is sufficient to turn on the thyristor thus causing the voltage on the cathode to rise to just below battery voltage which lights up D2.

The thyristor cathodes are all wired into a discrete 3 input or gate made up of D3, D4, D6 and R5, R6, R8, R10.

ALARM CIRCUITS

The output of the or gate is fed via R8 to the base of TR1. This stage is the voltage clamp and is simply a transistor switch. The emitter is at 0V until a high from the or gate


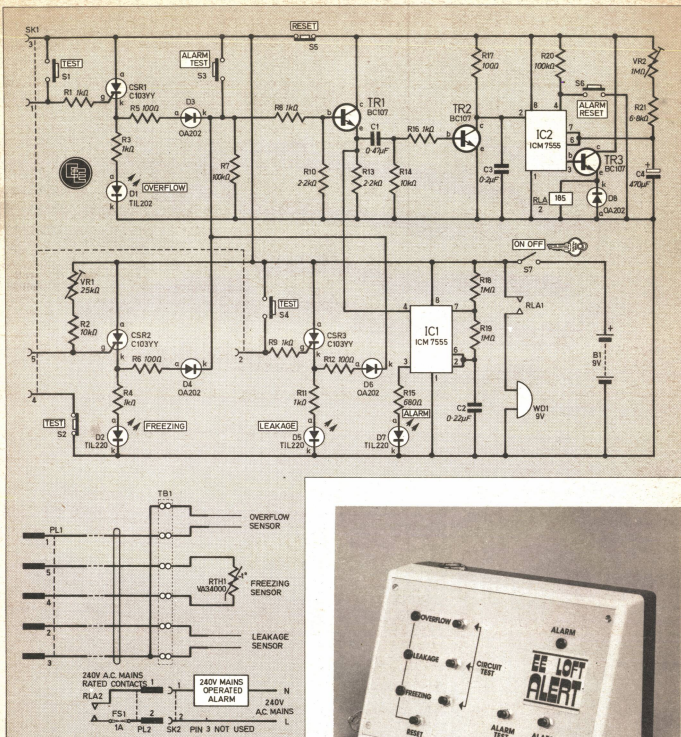


Fig. 1. Complete circuit diagram of the Loft Alert.

appears on the base whereupon the transistor switches on and the emitter voltage rises to just below the positive rail voltage.

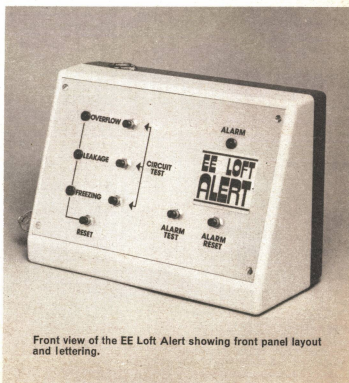At this point the signal takes two paths. The first is to the reset pin of IC1 (pin 4) wired as an astable multivibrator. Pin 4 is used here as an inhibit input.




Front view of the EE Loft Alert showing front panel layout and lettering.

HOW IT WORKS

The presence of water is detected by simple probes made up of a closely spaced pair of uninsulated conductors.

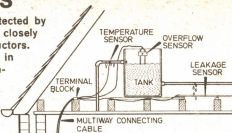To sense overflow conditions in the main tank a pair of fixed conductors is hung over the side such that their ends are just above the normal water level. Any abnormal rise in this level (caused by a faulty ball




cock for instance) will immerse the ends of these probes providing a conducting path between them. This will enable an electrical signal to be passed to the electronic circuitry thus actuating the alarm systems.

To sense burst pipes or other leakage in the plumbing, a sensor consisting of two closely spaced wires is run directly beneath the pipe work. Dripping water falls on these wires completing the circuit and setting off the alarm.

Loft temperature, or more precisely the temperature of the water pipe, is monitored by a thermistor. When the temperature falls to near 0 degrees Centigrade the alarm circuit is triggered.

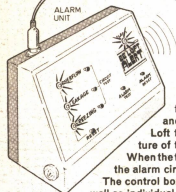The control box features both visible and audible alarms as well as individual monitoring of all circuits. This unit is installed in some convenient position in the house such as on the landing.



As soon as the voltage on this pin rises above about 0.4V the i.c. turns on and stays on so long as the "high" voltage to pin 4 is maintained. This causes the l.e.d. attached to pin 3 to flash on and off until the alarm is reset.

The other signal path is to IC2, another 555 i.c., this time wired as a monostable. This activates the relay coil for a certain time period after which the coil is deactivated. The in-built audible alarm (and extension alarm) is on for this time period (t) which is governed by the formula:


$$t = 1.1 \times (VR2 + R1) \times C4 \text{ seconds}$$

where the resistance is in ohms and capacitance in farads. The maximum time period obtainable is about 8 minutes which can be altered by VR2.

To trigger this arrangement pin 2 needs to be grounded momentarily. When the alarm is triggered TR1 emitter goes to and remains at a level of about 8V. This voltage step is applied to the RC network R14 and C1 which produces a positive-going voltage spike at the base of TR2. The transistor momentarily switches on and its collector drops to 0V. This negative-going voltage spike is applied to pin 2 of IC2 causing it to trigger and energise the relay via buffer amplifier TR3 for time t.

Circuit test switches S1, S2 and S4 simulate an alarm condition by causing a voltage to be applied to the thyristor gates. The alarm test switch

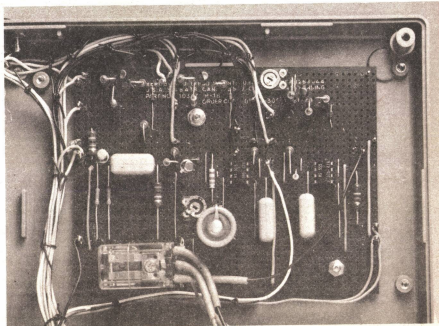S3 when operated applies a voltage to R8 thus simulating alarm conditions. Switch S6 grounds pin 4 of IC2 thus resetting it and S5 breaks the supply to reset the thyristors.



The completed circuit board mounted in position on the inside back panel of the case.

CONSTRUCTION

starts here

CIRCUIT BOARD

Construction should start with the circuit board. This consists of a piece of 0.1 inch matrix stripboard size 50 holes by 36 strips. It is advisable to make the breaks in the copper strips and drill the mounting holes before mounting components. Assembly is quite straightforward, although it is advisable to start with the resistors, then larger passive components and finally the transistors (see Fig. 2).

The i.c.s are mounted in sockets and the relay is mounted straight on to the board. It should be secured by glueing or by tightly wrapping a loop of insulated wire around the body and securing under the board well away from any copper strips used for electrical connections.

Veropins have been placed in locations on the board where connections to panel-mounted components are made. This makes interwiring and testing very much easier.

CASE

The prototype unit is housed in a Verobox type 202-21032D.

EE LOFT ALERT

COMPONENTS

Resistors

R1	1k Ω
R2	10k Ω
R3	1k Ω
R4	1k Ω
R5	100 Ω
R6	100k Ω
R7	100k Ω
R8	1k Ω
R9	1k Ω
R10	2.2k Ω
R11	1k Ω
R12	100 Ω
R13	2.2k Ω
R14	10k Ω
R15	680 Ω
R16	1k Ω
R17	100 Ω
R18	1M Ω
R19	1M Ω
R20	100k Ω
R21	6.8k Ω
All $\frac{1}{4}$ W carbon $\pm 5\%$	

Potentiometers

VR1	25k Ω horizontal miniature preset
VR2	1M Ω horizontal miniature preset

Capacitors

C1	0.47 μ F ceramic or plastic
C2	0.22 μ F ceramic or plastic
C3	0.2 μ F ceramic or plastic
C4	470 μ F 25V elect.

Semiconductors

IC1,2	555 CMOS timer i.c. (2 off)
TR1,2,3	BC107 npn silicon (3 off)
CSR1,2,3	C103YY or MCR102 thyristor (3 off)
D1,2,5,7	TIL220 I.e.d. or similar (two red, one yellow, one green)
D3,4,6,8	OA202 or similar small signal silicon diode (4 off)

Miscellaneous

S1,3,4,6	miniature push-to-make single pole switch (4 off)
S2,5	miniature push-to-break single pole switch (2 off)
S7	single-pole key operated on/off switch
SK1	5-pin DIN socket
SK2	miniature mains cable socket
PL1	3-pin miniature mains chassis plug
PL2	5-pin DIN plug
RLA	miniature 12V relay, 185 ohm coil resistance with two sets mains rated normally open contacts
WD1	miniature 9V audible warning device
RTH1	GM102 or VA3400 glass bead type thermistor
TB1	6 way screw terminal block
B1	9V type PP9

Stripboard: 0.1 inch matrix 36 strips $\times$ 50 holes; 5-way multi-core cable (or ribbon cable); connecting wire; twin-core 3A mains cable (for extension alarm); case (Verobox 202-21032D or similar); Battery connector clips; hardboard, panel pins, tinned copper wire, 2 pin plug and cable (for sensors).

See
**Shop
Talk**
page 19

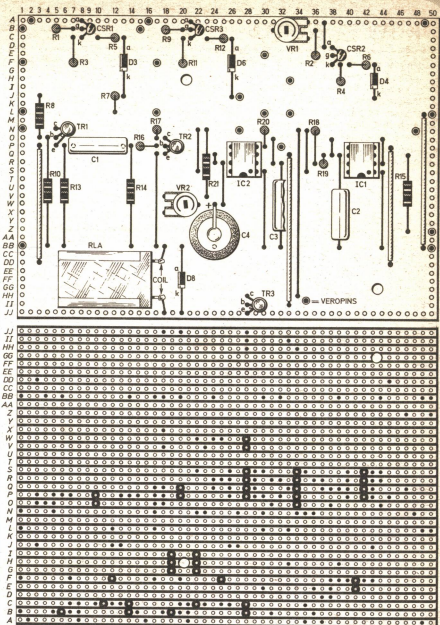


Fig. 2. Stripboard layout. Note that connections to off-board components are made via Veropins situated at appropriate locations on the stripboard. For wiring details of the relay see Fig. 3.

COMPONENTS
approximate
cost £20
excluding case and sensors


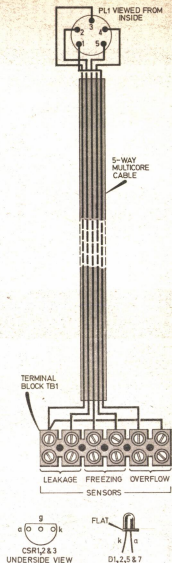
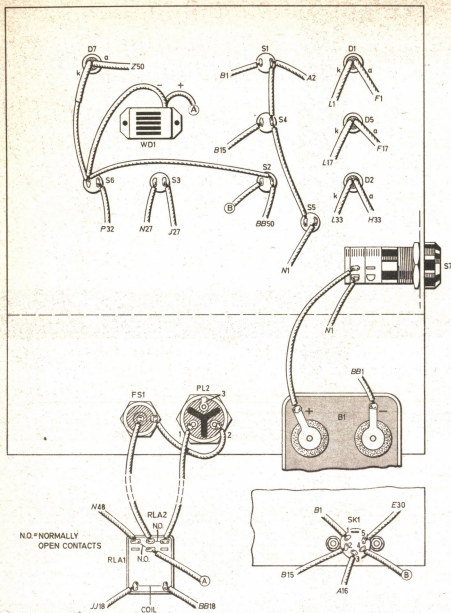
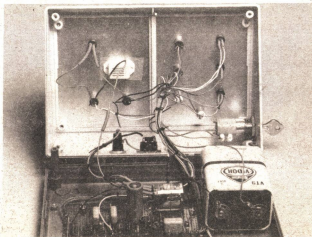



Fig. 3. Internal layout. Note that all letter/number combinations refer to Veropin locations. Fig. 4. Wiring of the interlinking cable on the main circuit board and single letters to other locations. SK1 is mounted on the from the unit to the sensors and its connectors.

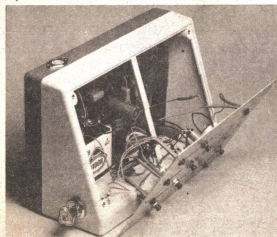



EE LOFT ALERT

SENSOR CONSTRUCTION & INSTALLATION


OVERFLOW SENSOR

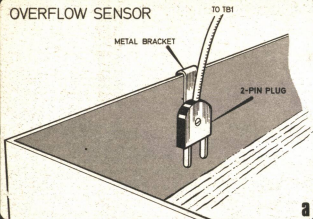


OVERFLOW SENSOR

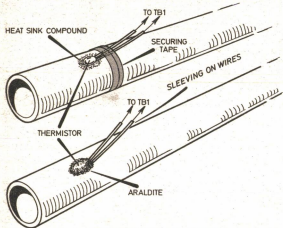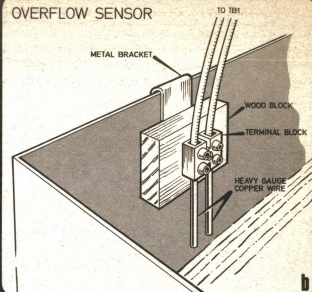

FREEZING SENSOR

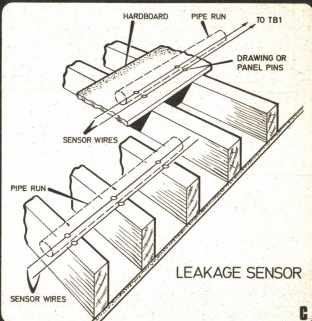

LEAKAGE SENSOR

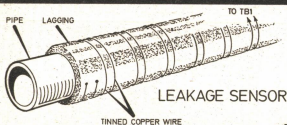

LEAKAGE SENSOR

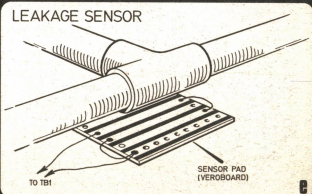


Fig. 6. Some suggested ideas for the sensors. Remember that if there is more than one sensor for any one circuit then these must be wired in parallel. For those whose pipes run along the top of the joists, leakage detection can be made easier by fastening the detector wires to short lengths of hardboard which are placed between the joists and under the pipe in question.

Assembly can begin by mounting the mains chassis plug PL2, fuse holder FS1 and 5-pin DIN socket SK1 in the case. Next the completed circuit board is bolted to the back of the case using 6BA countersunk bolts and nuts. The front panel is next marked out and drilled to accommodate the panel-mounted components.

Finally the internal wiring is completed as shown in Fig. 3. Although this layout is by no means critical, care should be taken to make sure front panel components do not foul internal parts if another layout or case are used.

A 5-pin DIN socket is used as the termination for the sensor inputs and the spare set of relay contacts are wired via a 1A fuse to a miniature mains chassis plug PL1 to act as an on/off switch for the extension alarm. Great care must be taken with this especially if it is likely to be used for switching mains voltage.

It is possible to connect any sort of mains device to this plug, for example a lamp, bell or buzzer, up to a maximum power rating of 250 watts for the relay specified.

The battery simply sits in the space next to the circuit board and a simple clamp is fitted to hold it in position.

Finally to secure the device against accidental switch-off, a key switch is used as the master on/off switch. This is not vital and can readily be replaced by any other on/off switch to reduce the overall cost of the system.

THE SENSORS

The sensor input to the unit is via a 5-pin DIN plug, hence it is necessary to run a length of 5-way cable from the unit to the loft. This is then connected to a 6-way screw terminal block as shown in Fig. 4.

Basically there are three types of sensor—one for overflow, one for leakage and one to detect freezing conditions. Various ideas for the sensor are shown in Fig. 5.

The overflow sensor is very simple, and consists of two electrodes mounted in the cold water tanks above the usual water level. See Fig. 5(a) and (b). A convenient ready-made sensor is available in the form of a 2-pin razor plug. This is robust with pins far enough apart so that when the level subsides there isn't any moisture left behind bridging the gap.

The other method uses a 2-way screw terminal block with short wires forming the probe. Care should also be taken to site this sensor far enough above the water level so that it isn't accidentally triggered by rushing water as the tank fills.

LEAKAGE DETECTOR

The leakage detector in practise is a little more complicated. One method

is to have twin runs of tinned copper wire about 2mm apart beneath all pipes at risk fitted to the joists vertically beneath the pipe run.

Alternatively the wire can be fastened onto hardboard in a straight line using panel pins. This assembly can then be laid underneath the pipe-work, perhaps on a slight slant so any dripping water will run down on to the wires and set off the alarm.

If the pipes are lagged then two parallel lengths of tinned copper wire could be wrapped around the length of the lagging. See Fig. 5 (c) and (d) for details.

If complete pipe-run monitoring is not considered essential a number of small sensors consisting of stripboard with alternate strips bridged and placed under particularly risky spots could be tried. All of these sensors would of course be wired in parallel. This is shown in Fig. 6 (e).

FREEZING SENSOR

The freezing detector is straightforward as it consists simply of a miniature bead thermistor. This is attached to either the tank ballcock or pipe most susceptible to freezing. For a permanent arrangement, the thermistor can be glued to the pipe using Araldite. Alternatively the thermistor can be coated in a heatsink compound and taped to the pipe, see Fig. 5 (f).

Readers will no doubt be able to adapt these ideas to their own circumstances or even invent better ideas of their own. In any event if more than one sensor is used for a particular channel, they should all be wired in parallel.

All the sensors are terminated in the loft at a 6-way screw terminal block TB1 to which the 5-way cable to the unit is attached.

SETTING UP

Once the unit has been assembled its function can be tested using the built-in test buttons. When any of the CIRCUIT TEST buttons is pressed the relay coil should be activated causing WD1 to sound, diode D7 should flash and the l.e.d. associated with the particular circuit should light up. Pressing ALARM RESET will mute WD1 and pressing RESET will reset the whole device.

Similarly the alarm devices alone can be tested by pressing ALARM TEST and reset by pressing ALARM RESET.

Having built and tested the unit the freezing circuit should be set up next. To do this, the thermistor should be temporarily attached to the unit via the 5-pin DIN socket, and fastened to the side of a metal container with adhesive tape. A mixture of water and ice is then poured into the container and the temperature of the

container is allowed to stabilise. The potentiometer VR1 is then adjusted until the alarm just triggers under these conditions.

At this point the sensors in the loft can be installed and the 5-way cable run down to the unit. Extension warning devices can be attached via PL2, the battery checked and the device is ready for use.

USING THE DEVICE

The Loft Alert has been designed to have a very low quiescent current consumption in the standby condition (typically less than 0.4mA), to allow the unit to be battery powered and left on continuously. Under these conditions the specified life of the PP9 battery will be close to its shelf life which is about one year.

However, should the alarm be triggered, the current consumption during the alarm period reaches about 70mA. This means that once the alarm condition has been dealt with the battery should be checked before the system is reset and left, to make sure that it was not exhausted whilst the alarm was activated.

Assuming the unit is going to be in regular use, periodic inspection and checking of the sensors and battery is a good idea and a half-yearly overhaul is certainly recommended.

Bind it

It's so easy and tidy with the Easybind to file your copies away. Each binder is designed to hold approximately 12 issues and is bound and blocked with the Everyday Electronics logo. Gold leaf set supplied for self blocking of volume numbers and years.

Price £3.75 including postage, packing and V.A.T.. Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd, Post Sales Dept, Lavington House, 25 Lavington St, London SE1 0PF

it's easy with **EASyBND**

Order Form

Everyday ELECTRONICS

I enclose p.o./cheque value


for binders. Years required

(BLOCK LETTERS PLEASE)

Name

Address

Date

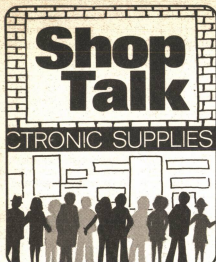

By Dave Barrington

Light Controller

It would seem that Discos do not have the monopoly on special effects this year. We are reliably informed that the measure of a good festive party this season will be its lighting effects—what's happened to stimulating conversation and good food?

Aimed more at the disco market with a price tag of £99, including VAT, the latest "light controller" from TUAC should create a stir.

The Starchaser 4000 is an extremely versatile four-channel (750W per channel) lighting control console offering 16 distinctive and varied lighting patterns. Basic light effects are selected by four switches, but by using another five switches it is claimed that the operator has a possible 1000 different patterns and effects at his finger tips.

Use of automatic gain control (a.g.c.) is a standard feature, and zero reference triac firing circuitry is incorporated to minimise r.f. interference. Also featured are two audio control modes giving a single shot and an audio controlled sequencing facility. Both audio control modes are designed to be "bass sensitive" being triggered by instruments such as drums and bass guitar.

A master dimmer allows all channels to be faded simultaneously. A crossfade facility enables each channel light to be brightened and dimmed at a controlled rate, producing a merging effect.

The crossfade switch also has a short on or "flash" position which reduces the lamp on time of any channel during sequencing to produce a simulated "strobe" effect.

The Starchaser 4000 is available direct from Tuac Ltd, or from selected stockists. Further information and addresses of stockists can be obtained from Tuac Ltd, Dept EE, 121 Charlmont Road, London SW17 9AB.

Link-up

Readers embarking on our new *Teach-In 80* beginners series may like to investigate the latest link-wire kit for breadboards from Lektrokit for possible use with the *EE Tutor Deck*.

Although intended for their own range of breadboard systems they

will fit most commercial matrix boards. Each kit contains 350 wires and comes in a plastic compartmentalised box. All of the wires are of solid tinned 22 a.w.g. with p.v.c. insulation sleeving.

Fourteen different lengths are included ranging from 0.1in, for linking adjacent holes on a 0.1in matrix board, to wires with a 5in span. All wires have both ends stripped and bent to 90 degrees and each group of wires has a different coloured sleeving for easy identification of individual link wires.


For more information and addresses of local stockists, readers should write to Lektrokit Ltd., Dept. EE, Sutton Industrial Park, London Road, Earley, Reading, RG6 1AZ.

Good Trading

Due to remarkable trading response during 1978/9, Newbear Computing Store recently decided to reorganise its operations for 1980 under three divisions.

Catering for business, industrial and educational requirements, Newbear Systems will be supplying microcomputers built to professional standards with matching peripherals and software.

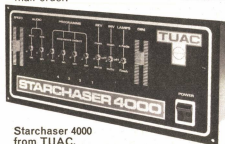The growth of the demand for technical books has meant the forming of Newbear Books. Several hundred titles are available "off-the-shelf" and services offered include, a claimed, 24 hour turnaround on mail order.



Starchaser 4000 from TUAC.

The Components Division holds very large stocks and includes a wide range of microcomputer components, including kits from Acorn, Nascom and Bearbag 77-68 series. A comprehensive range of integrated circuits are also stocked.

A further result of their good trading figures, has been the opening of a new 1500 sq. ft. Northern branch store at Mersey House, 220 Stockport Road, Cheadle Hulme, Cheshire.


The latest piece of information we have received from Newbear is the announcement of a Christmas Sale.

A number of ex-demo microcomputers and peripherals are being offered to callers at the Newbury (40 Batholomew Street, Newbury RG14 5LL) and Northern showrooms. A large range of components, keyboards and other small items will also be available at reduced prices.

Small Orders

Another well established company who have long recognised the enormous potential of the amateur electronic constructors' market is Neosid Ltd.

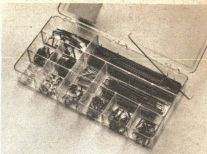A major supplier of ferrite components, coil assemblies and plastics coil formers, this company has now formed a Small



Lektrokit Link-wire pack.

Order Division to cater for the amateur's special needs.

A Small Order Catalogue is available from Neosid Small Orders, Dept EE, P.O. Box 86, Welwyn Garden City, Herts, AL7 1AS. Send a large self stamped addressed envelope.

Constructional Projects

As the *EE Loft Alert* is likely to be our most popular project, and be tackled by the less experienced as well as the more advanced constructor, we recommend that only first grade components be used.

The thyristor type C103YY is available from R.S. retail outlets. A type MCR102 from Maplin and the 2N5060, 2N5061 from Watford Electronics can be used.

If any other type of bead thermistor than that specified is used it will obviously mean circuit "tuning". The type used in our unit was an RS Components miniature bead type (stock No. 151-136) equivalent for the VA3400.

Any relay may be used provided the coil resistance is above 100 ohms and will operate with a voltage of 6 to 9V. A suitable type is the Keyswitch SM2P/12/185 which is a nominal 12V type but works down to 5V. Another two types which seem suitable are the Maplin FX27E and the Watford RL.

Part three of the *EE Radio Control System* this month deals with the Receiver.

We understand that designer approved parts for the complete *EE System* are available from Cheshire Model Supplies Ltd, 55 Cheadle Road, Cheadle Hulme, Cheshire.

Because of the small size of the receiver, and the "dense packing" of components on the printed circuit board it is essential that the specified types of capacitors and resistors are used. Resistors rated at up to $\frac{1}{2}$ W should be suitable, but $\frac{1}{4}$ W types (as available from Electrovalue Ltd) are recommended.

The firm S.L.M. (Model) Engineers Ltd., Chiltern Road, Prestbury, Cheltenham, Glos., can supply control pots, cases and those other items specifically indicated "SLM" in our components lists. They do not however supply standard circuit components.

The short spring-line module called-up in the *Spring-Line Reverb Unit* is only available from Maplin Electronic Supplies, stock No. XL08J. All other components for this project are readily available from most distributors.

The ZN1034E timer i.c. for the *Mains On/Off Timer* is listed by C. N. Stevenson, T.K. Electronics, Technomatic and Watford Electronics.

No buying problems are envisaged for the *Unibord 9V Power Supply* project.

UNIBOARDS

SIMPLE
TRANSISTOR
DESIGNS

By A.R. Winstanley

3

9V POWER SUPPLY

WITH one exception, all projects described in this series have been designed to operate from a 9 volt rail. In certain instances, however, it would be considerably more convenient to power the project from the domestic mains supply.

The 9 Volt Power Supply was designed with economy in mind. It was to be built as cheaply as possible, and as such it should eventually pay for itself in terms of the cost of dry batteries. Although the circuit is rather basic (and is not transistorised) the unit has proven quite adequate to operate the projects in this series.

CIRCUIT DESCRIPTION

The circuit diagram is shown in Fig. 1. Transformer T1 is a valve heater transformer with a mains primary and a 6.3V a.c. 300mA secondary. Mains voltage is applied to the primary and stepped down to

6.3V. This low a.c. voltage is presented to D1—D4.


The diagram illustrates four separate rectifiers but in fact a single encapsulated unit, containing four rectifiers, called a "bridge rectifier", is used.

The bridge rectifier converts the a.c. into a pulsating d.c. voltage. Capacitor C1, being a very large value electrolytic capacitor, smooths out the pulses to give a nominal d.c. voltage of about 9V with a reasonably low ripple content sufficient for our purposes here.

Finally, a light-emitting diode, D5, together with its associated current-limiting resistor R1, forms a "power on" indicator. A further bonus is that if for some reason, the output of the p.s.u. is shorted, the l.e.d. will extinguish, so indicating a fault present.

A 3.5mm jack socket SK1 is used as the outlet for the 9V supply. The tip of the plug inserted in SK1 is connected to +9 volts.

Fig. 1. Circuit diagram for the 9V Power Supply. The output connecting lead is terminated with jack plugs PL1 and PL2. The jack tips carry the positive (+9V) supply.

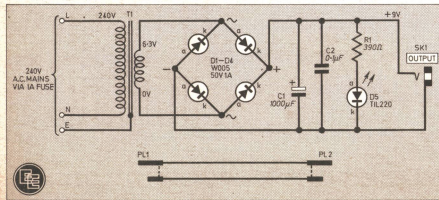

CONSTRUCTION
starts here

The prototype unit was housed comfortably in a readily-available PB1 type plastic box, measuring 115 x 75 x 35mm. It is recommended however that the heater transformer is acquired first, and then a plastic box of appropriate dimensions chosen to house it.

The circuit is built on 0.1 inch matrix stripboard measuring 10 strips x 24 holes as shown in Fig. 2. There are no problems with this aspect of construction, but it is extremely important that both the p.c.b. mounting electrolytic capacitor and the bridge rectifier are correctly orientated.

The completed board is mounted on the inside face of the end opposite main cable exit by means of 6BA spacers, nuts and bolts.

The interwiring is as shown. A cable retaining clamp should be fitted to the main cable to prevent it from pulling out. Also, note how the earth input of the mains cable is connected by means of a solder tag to the transformer mounting frame, using one of the mounting bolts.

The l.e.d. can be positioned and secured using the special-purpose plastic clip normally provided. Finally, a 1 amp fuse must be fitted in the mains plug.

VENTILATION

It was found that the transformer itself did tend to get rather warm during normal operation. To counter this a series of ventilation holes have been drilled in the case. If necessary, a piece of aluminium mesh, or perforated zinc, should be glued behind the holes to prevent any objects poking through the holes and possibly touching mains wiring inside.


Jack sockets have been used in the individual projects to facilitate the connection of the 9 Volt Power Supply. A common audio lead, terminated with a 3.5mm jack plug each end, is all that is required to make the connection.

Note that the audio lead must be connected up before the p.s.u. is switched on: if the p.s.u. is switched on first and then plugged into the project, it is possible that the jack plug can temporarily short out the power supply, perhaps having a detrimental effect.


Next Month: Touch Switch



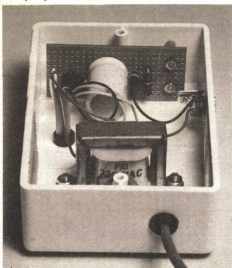The finished power supply showing the small ventilating holes and the 9V output jack socket.



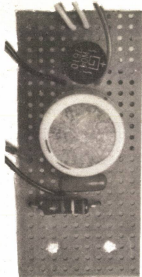Layout of components inside the case. The circuit board is mounted on the side of the case using 6BA spacers.



Completed circuit board.

COMPONENTS

Resistors

R1 390Ω ½W carbon ±5%

Capacitors

C1 1000µF 25V radial elect.

C2 0.1µF polyester type C280

Semiconductors

D1—D4 50V 1A diode bridge type

W005 or similar

D5 TIL220 i.e.d. or similar

Miscellaneous

T1 mains primary/6.3V 300mA secondary

SK1 3.5mm jack socket

PL1,2 3.5mm jack plug (2 off)

Stripboard: 0.1 inch matrix size 10 strips × 24 holes; mounting bush for D5; case type PB1, see text; cable retaining clip/grommet; p.v.c. insulated connecting wire; 3-core mains cable; 6BA fixings, nuts bolts, washers, stand-off spacers, solder tag;

Approx. cost Guidance only

£3.25

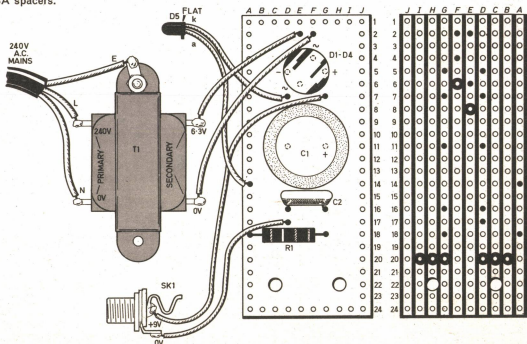


Fig. 2. Layout of components on the topside of the stripboard, breaks to be made on the copper strips on the underside and interwiring details to the mains transformer, light emitting diode (D5) and output jack socket (SK1).

TEACH-IN 80

ENTER THE EXCITING
WORLD OF ELECTRONICS

Part 4
By S. R. Lewis,
B.Sc.

THE success of electronics as we know it today is based entirely on the growth of the semiconductor industry. Whilst electronics was certainly thriving in the valve era the real potential of electronics could only be realised by producing a small, cheap, low-power alternative to the valve.

Investigation and development just after the last war led to the production of the first **transistor**. It was apparent that the basic components of the transistor—**semiconductor junctions**—could also be used to build a range of devices each with special characteristics.

In this part of the series we will look at the simplest semiconductor junction device—the **diode**. Understanding the operation of this relatively simple two-terminal device will aid the understanding of the more complex three-terminal transistors.

ONE-WAY CURRENT

The major point to understand concerning diodes is that whilst they have two terminals just like a resistor the two ends are not identical. Looking at an actual diode the two ends appear the same with the exception that the body of the diode has a ring at one end, so just what is the difference?

The answer to this is that the diode is a device sensitive to the *direction* of flow of current through it. It does not matter which way round a resistor is put in a circuit, it will still behave in the same way. A diode, on the other hand, appears like two different devices depending on which way round it is connected.

We obviously need to be able to refer to the two ends of a diode

using separate names and Fig. 4.1 shows the circuit symbol for a diode next to an actual diode with the terminals marked with their commonly accepted names—**anode** and **cathode** (the latter usually abbreviated to "k"!). The symbol for a diode is an arrow and this gives a clue to its properties.

When current flows through the diode from anode to cathode (in the direction of the arrow) the diode presents very little resistance to that current—it is a good conductor. If we try to pass current from the cathode to the anode (against the arrow) we will have great difficulty. In fact, the diode will break down under the voltage before it will pass any appreciable current.

We can liken the diode to an electronic switch which is either open or closed depending on the direction of the current. It behaves very like a valve (mechanical not electronic) in a tyre which allows air in but not out (Fig. 4.2).

When a diode has a voltage across it such that current tends to flow from anode to cathode we say the diode is **forward biased**. If the voltage is in the opposite direction then the diode is **reverse biased**.

RECTIFICATION

The widespread use of diodes has mainly come about because the majority of electronic equipment

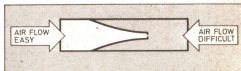
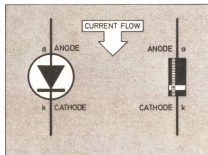


Fig. 4.1 (left). Circuit symbol and names of the two terminals of a diode. Current can only flow in the direction of the arrow.

Fig. 4.2 (above). A tyre valve provides a mechanical analogy of the diode.

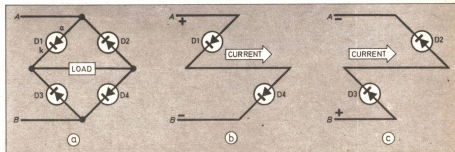


Fig. 4.3. (a) Four diodes connected as a "bridge". The "load" represents either a single component or a whole circuit. (b) shows the path of the current when A is positive with respect to B and (c) the path when B is positive with respect to A.

will only operate when supplied with a steady voltage which does not change direction or value with time.

Power as supplied by the electricity generating stations is the opposite to this; it is constantly changing value and direction—in fact doing this 100 times a second.

Diodes are the easiest way (though not the only way) of converting this constantly reversing voltage into one which is in one direction only. In fact four diodes are needed, the arrangement being shown in Fig. 4.3 and usually referred to as a **diode bridge**.

DIODE BRIDGE

When point A is positive with respect to point B, diodes D2 and D3 are reverse biased; so little current flows through them that they are virtually open circuit. Diodes D1 and D4 on the other hand are forward biased presenting very little resistance to current. The flow of current is thus as shown in Fig. 4.3b.

When the voltage is reversed, that is B positive with respect to A, diodes D1 and D4 are reverse biased while D3 and D2 are forward biased so that the current flows as in Fig. 4.3c. We thus have a circuit where the voltage across the load is the same no matter what the polarity of the power source.

We could use this circuit for protecting a circuit which could be damaged if the battery were connected the wrong way round.

SINUSOIDAL

If the voltage across A and B is from the mains it will be varying regularly from positive to negative as shown in Fig. 4.4(b). We call this type of waveform **sinusoidal**.

The positive-going half-cycle will be passed by D1 and D4. The negative-going half-cycle will be passed by D2 and D3. After passing through the diode bridge circuit the waveform appears as at (c). Notice that while it is still varying, it is always of the same polarity (the way in which this "pulsating" voltage is converted into a steady d.c. voltage will be described later in this series).

The process of converting an alternating voltage into a single polarity voltage is referred to as **rectification**. Very often the four

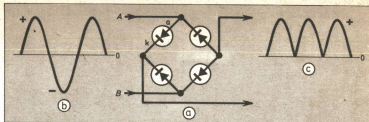


Fig. 4.4. (a) Mains voltage being rectified by a diode bridge. The bidirectional voltage (b) has been converted into a voltage of a single direction (c)

diodes needed are supplied in a single package with four leads. This is known as a **bridge rectifier**.

NON-LINEARITY

It was stated earlier that a forward-biased diode presents very little resistance to current flow but this statement needs some elaboration.

It is found that, in the forward direction, the diode has a **non-linear** relationship between applied voltage and current. In other words, if the current is 1mA with a forward voltage of 0.5V it is not true that 2mA will flow with an applied voltage of 1V.

A graph of current plotted against voltage for a typical silicon low-current diode is shown in Fig. 4.5. Two points concerning the graph are of particular interest.

The first is that the voltage range of the graph is very small, only going from 0 to 1V. If we look at the graph near the point where 0.7V is applied to the diode we see that a very small change in voltage is needed to produce a large change in current. Alternatively this may be stated as large changes in current produce small changes in diode voltage drop.

It turns out that this voltage is mainly dependent on the materials from which the diode is made. Silicon diodes have a constant voltage characteristic around 0.7V and germanium diodes (now rather uncommon) at 0.2V.

The second point is that at low applied voltages the current is very small, that is the diode has high resistance.

What conclusions can be drawn from the graph? Firstly we can deduce that even when passing a high current the diode will be dropping about 0.7V. In order for the diode to be an efficient rectifier, this voltage should be small with respect to the voltage to be rectified.

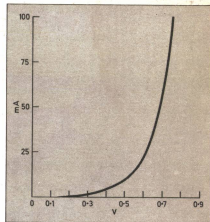


Fig. 4.5. Current plotted against voltage for a typical low-current silicon diode.

The fact that the voltage across the diode is relatively stable and predictable leads to another use of the diode: as a **constant voltage source**. Audio amplifiers often use forward biased diodes to derive stable bias voltages for output stages.

SEMICONDUCTOR JUNCTIONS

Whilst understanding how diodes behave in a circuit is fairly simple, understanding how they are made and how they actually work is far more difficult. One really needs a thorough knowledge of physics to appreciate semiconductor operation but the general principles are as follows.

Diodes nowadays are made from a single piece (or chip) of silicon which is specially treated when in its molten state. The two halves of the diode are exposed to two types of gas which give each half distinct properties.

The process of introducing tiny amounts of impurities into the silicon in this way is known as **doping**.

One half of the diode-to-be is "doped" with a carefully chosen material whose atoms have one

more electron than the basic silicon—it is like creating a surfeit of electrons. The other half is doped with a material whose atoms have one less electron than silicon—this is like creating a deficit of electrons.

Where the two forms meet, a field appears which tends to oppose any electrons which try to cross from one side to the other; we call this a **potential barrier**.

A forward bias on the diode tends to reduce the "height" of the barrier allowing more electrons to flow, hence conduction in this direction is easy. Applying a reverse bias however tends to increase the size of the barrier so very little conduction takes place (until the field is so high that the barrier breaks down). See Fig. 4.6.

This description obviously raises a lot of questions but it should give a feel for the sort of processes occurring in a diode.

LIGHT EMITTING DIODES

When electrons cross the potential barrier in a forward biased diode they change from a high energy state to a lower energy state. The energy that they lose can appear either as heat or as light.

The materials from which diodes are made determines in which form the energy appears. By making a diode out of gallium, arsenic and phosphorus it is possible to produce a diode which releases a high proportion of the energy change of the electrons as visible light. When these diodes are placed in special translucent packages we have **light emitting diodes (L.e.d.s)** which are becoming so familiar today. The symbol is shown in Fig. 4.7a.

Light emitting diodes usually require a forward current of about 10 to 20mA for efficient light generation. At these sort of currents the voltage drop across the diode is around 1.6V although it may be up to 2V for some types of L.e.d. At the present time the colours available are red, through orange and yellow to green. Blue has proved a very difficult colour to produce although it was recently announced that a blue diode has been manufactured albeit very inefficient.

As well as single light emitting diodes, arrays of diodes can be

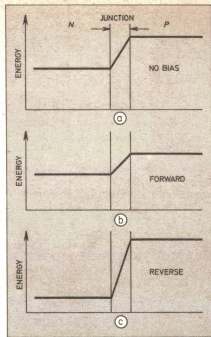


Fig. 4.6. The potential barrier in (a) an unbiased junction (b) a forward-biased junction and (c) a reverse-biased junction.

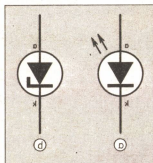


Fig. 4.7. (a) Circuit symbol of a light emitting diode (b) circuit symbol of a Zener diode.

combined to form **seven-segment L.e.d. displays** so familiar in calculators and digital clocks and watches.

ZENER DIODES

As the reverse voltage across a diode is steadily increased there comes a point where the diode "breaks down" and suddenly becomes a good conductor. If the current is controlled so that the diode does not burn itself out we have a very useful component: the **Zener or reference voltage diode**.

By controlling the geometry of their diodes, manufacturers have been able to produce diodes with a huge range of **breakdown or Zener voltages**.

The useful thing about the breakdown characteristic is that the current can be varied over a large range with hardly any change in voltage. A typical Zener diode can produce voltages stable to a few tens of millivolts at a voltage of 10V.

Zener diode specifications usually refer to both the Zener voltage and the maximum power dissipation of the diode. The maximum current that must be allowed to pass through the diode is the maximum power dissipation divided by the Zener voltage. Thus a 4.7V 400mW diode must not carry more than 400/4.7 or about 85mA. The symbol for a Zener diode is shown in Fig. 4.7b.

DIODE SPECIFICATIONS

Diodes come in a variety of shapes and sizes. Manufacturers specify two main properties of their diodes: the **maximum forward current (I_{max})** and the **peak inverse voltage (p.i.v.)**, that is the maximum safe voltage that can be placed across the diode in the reverse direction that will not cause breakdown.

A diode in a transistor radio may have a p.i.v. of 50V and an I_{max} of 100mA. One in a power supply could have a p.i.v. of 600V and an I_{max} of 5A.

When large currents flow through a diode heat is generated so the packages of heavy current diodes are usually designed to bolt onto a piece of metal (a **heatsink**) to help keep the diode cool.

DIODE GATES

We have seen how diodes are similar to switches, having two states one high resistance and the other low resistance, the "switch" being controlled by the direction of the current flow.

The principle can be put to further use in what is known as the **diode gate**.

A "gate" as the name implies can be either open or shut. In real terms this means that a voltage is used to control the flow of current into another part of the circuit.

The circuit of a simple diode gate is shown in Fig. 4.8. The controlling voltage is applied at point A, the voltage to be controlled being that at point B.

EXPERIMENT 4.1: DIODE BRIDGE RECTIFICATION

Components needed: 1k Ω resistor, 100k Ω resistor, 1N4148 diodes (4 off)

The circuit diagram for an experiment to investigate diode bridge rectification is shown in Fig.4.10(a), with the layout of the components on the Tutor-Deck in Fig.4.10(b). Note these additional connections on right hand panel of Tutor Deck: link S1(a) to B1 +9V; link S1(c) to B2 -9V.

Switch S1 is used to produce either +9V or -9V at point A. Since the meter can only indicate 100 μ A or so, a resistor R1 is used as the main current path, with the meter (in series with R1) used to indicate the polarity of the voltage across R2.

It will be found that whatever the setting of S1, the polarity of the voltage across R2 will be the same.

For identification of Tutor Deck components and their associated sockets refer to Fig. 2.8.

EXPERIMENT 4.2: DIODE "AND" GATE

Components needed: 1k Ω resistor, 1N4148 diodes (2 off)

The circuit diagram for the simple two diode AND gate is shown in Fig.4.11(a) with the layout of the components in Fig.4.11(b).

The l.e.d. D1 serves a dual purpose; it forms both the output diode and the load. When either input A or input B is taken to 0V the l.e.d. will be off, since all the current through R1 will flow through D3 or D4. Only when both inputs are taken to 9V (or left open-circuit) will the l.e.d. light. We say the input A AND input B must be at logic "1" before the output is at logic "1".

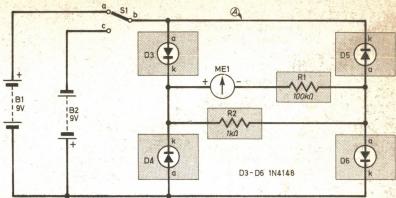
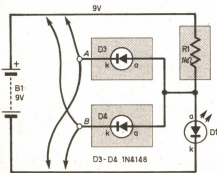


Fig. 4.10 (a) Circuit diagram showing the diode as a rectifier with (b) showing the component layout on the Tutor Deck.

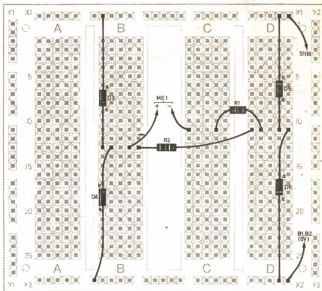


Fig.4.10b

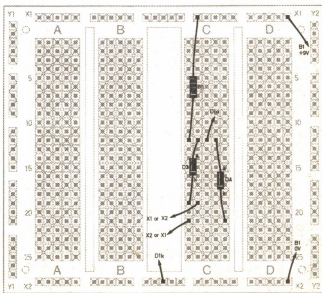


Fig.4.11b

Fig. 4.11 (a) Circuit diagram of a simple two-input diode AND gate. (b) shows the layout on the Tutor Deck.

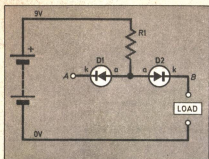


Fig. 4.8. Circuit of a simple diode gate. The voltage at A is used to control that at B.

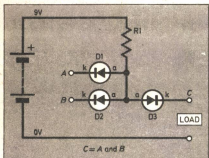


Fig. 4.9. A diode AND gate. All inputs must be at logic "1" (9V) for the output to be high.

Consider what happens when A is taken to 0V. Diode D1 will be forward biased, current flowing through R1. The voltage drop across D1 will be about 0.7V (assuming it is silicon). A load connected from the cathode of D2 to 0V will therefore have no voltage across it.

PART 4 QUESTIONS

4.1. A diode with its cathode more positive than its anode is said to be

- forward biased
- reverse biased
- neither

4.2. A diode in a circuit is found to have a voltage drop from anode to cathode of 0.2V. Is the diode most likely to be

- silicon
- germanium
- gallium arsenide

4.3. A 10V 1.3 watt Zener diode should not be allowed to pass more than

- 1.3A
- 130mA
- 13mA
- 1.3mA

4.4. An AND gate output will only be at logic "1" when

- all
- none or
- some of its input are at logic "1".

4.5. The stripe on an 1N4148 diode indicates

- the anode
- the cathode
- the emitter

PART 3 ANSWERS

3.1. c) 3.2. a) and c) 3.3. b) 3.4. c)

If A is now taken to 9V diode D1 will have zero voltage across it. Now all the current will flow through R1, D2 and into the load.

If the usefulness of this circuit is not apparent, consider the case when, instead of just a single diode, two or more diodes are used in place of D1. Now connecting any input diode to 0V will cause zero voltage to appear across the load. What we have is the basis of

a simple logic gate, in fact an AND gate, see Fig. 4.9.

Logic is a whole subject on its own and we will not go into further detail at this stage. However, from these simple beginnings quite elaborate logic circuits were developed leading to the immensely complicated logic circuits used in today's computers.

Next month we will look at capacitors.

EE CROSSWORD No 23

BY D. P. NEWTON


ACROSS

- A kind of biscuit found with chips (5).
- Complete temperature scale (8).
- Conducts into kidnapping (7).
- Grille makes sick (3).
- Metallic ion form expressing the perverse timing of Fate (6).
- Would another revolution make the i.c. so antique? (5).
- Short beats give sustaining activity (3).
- Those heartily felt surges (6).
- A switch that's a bit shaky (8).
- Free electricity? (2, 6).
- Sea with icy connections (6).
- Phoney part of 25 down (3).
- Characteristic curves are seldom so perfect (5).
- Often a cause of an open-circuit but has a capacity to be useful (3, 3).
- We couldn't solder on with it (3).
- A stratum characteristic of the i.c. (7).

- To put down interference (8).
- Measuring term (5).

DOWN

- It avoids mis-match at the terminal (7).
- Aged solder partly but more personal (5).
- We all must have them to make any start at all (5, 10).
- Sound tone clipped to place above (4).
- The fishy part of electricity (3).
- When 10 down cools off, do we get these? (4).
- Type of network (7).
- Nothing like 18 across in part (2, 4).
- Early galvanometer (7).
- Bulb cooler tails off to immersion heater (6).
- One electrode turned cooker (7).
- All brain but no eye for food (4).

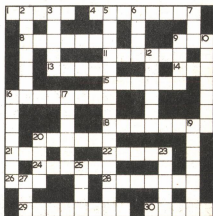

23 Glare makes it big (Anag.) (5).

25 Cog (4).

27 They are common to the electronics of 13 and 28 across (3).

Solution on page 60

next month



SLIDE/TAPE SYNCHRONISER

A compact unit that enables the amateur photographer to give the professional touch to his slide presentation. A simple, cheap and effective design giving fully automatic slide changing with optional manual override. For use with any slide projector fitted with a remote control socket.

MICRO MUSIC BOX

A touch operated music box using a microprocessor. From a total repertoire of 24 tunes, it plays a selected bank of 8 tunes in rotation by automatic sequencing when operated.

MORSE PRACTICE OSCILLATOR

A very simple project to aid those learning and teaching Morse Code. Contains complete list of Morse alpha-numerics.

SIMPLE SHORT WAVE RECEIVER

This t.r.f. type receiver is designed to combine both simplicity and good performance. Suitable for both Amateur Band and Broadcasting Band listening. Frequency coverage of 1.67 to 31.5MHz in three ranges with c.w. and s.s.b. as well as a.m. resolution.

**special
offer**
FOR EE READERS
**Mini 20
Multimeter**


- ★ A 27-range instrument
 - ★ Ideal for the constructor and experimenter
- Full details in February issue

Everyday ELECTRONICS

FEBRUARY 1980

ISSUE ON SALE
FRIDAY, JANUARY 18

Price 50p

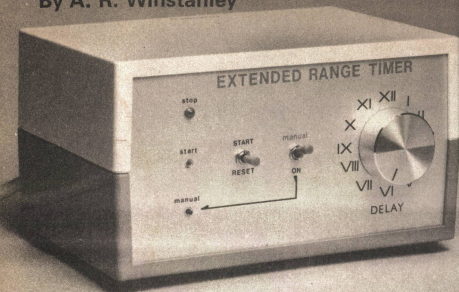

Mains On/Off Timer

PERHAPS one of the less pleasant ways of starting a day is to be awoken to the nerve-shattering jangling of one very large and very loud alarm clock! There must be better ways of being roused from sleep, and this project would seem to make life a little easier in this respect.

TIMED DELAYS

The Mains On/Off Timer is a versatile unit which will generate timed delays of up to twelve hours in one-hour increments. Once this period is up the Timer will switch on or switch off any mains load connected to its output sockets, and this load can have a power rating of up to 1800 watts; therefore the unit is suitable for driving many appliances.

Thus by connecting a mains radio to the Timer and setting the appropriate delay, one can be awoken to the more acceptable strains of Terry Wogan.

The Timer utilises the Ferranti ZN1034 precision timer i.c. to produce very accurate timing periods using low value timing components when compared with typical component values used with, for example, the NE555 timer.

Also, the ZN1034 is equally at home producing delays of one second or one week—compare this with the maximum one hour delay generated by the 555. Indeed, by using two ZN1034 timers a delay of up to one year is attainable.

THE TIMER I.C.

The internal circuitry of the ZN1034E (the 'E' denotes a 14-pin d.i.l. package) is very simply illustrated in Fig. 1. The i.c. features an on-chip oscillator and twelve-stage divider. The frequency of oscillation is determined by an external RC circuit. When the oscillator has cycled 4095 times the control logic switches over the complementary outputs at pins 2 and 3.

The internal RC circuit therefore determines the delay period which the i.c. will generate. The use of an oscillator and counter in this manner enables an RC circuit with a relatively low time constant to be utilised to deliver relatively long delays.

The timing period is given by the formula

$$t = k \times B \times C$$

where t is the delay (seconds)

R is the external timing

resistor (ohms)

C is the external timing

capacitor (Farads)

and k is a multiplying constant.

The constant, k , is determined by the value of a "calibration resistor." With pins 11 and 12 of the i.c. linked, an internal 100 kilohm resistor is selected, and $k = 2736$.

If pins 11 and 12 are linked by a 50 kilohm resistor then the calibration resistor is increased to 150 kilohms and $k = 4095$. If instead a 300 kilohm resistor is connected between pin 12 and ground then k becomes 7500, and in this mode the i.c. is able to produce its longest delay periods. If the internal resistor is used, this will give the best coefficient of temperature, but whatever method is chosen, the calibration resistor should not exceed 300 kilohms.

When choosing values of R and C , the following limits apply:

$$5k\Omega \leq R \leq 5M\Omega$$

$$C > 3300pF$$

The timing period commences when the device is triggered by grounding pin 1. Two complementary outputs are available at pins 2 and 3; pin 2 ($\bar{Q}$) is normally high and goes low during timing; the opposite is true of pin 3 (Q).

COMPONENTS
approximate
cost £25


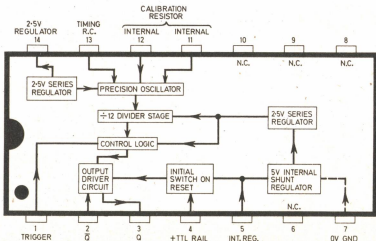


Fig. 1. Block diagram of the internal circuitry of the ZN1034 i.c.

29

HOW IT WORKS

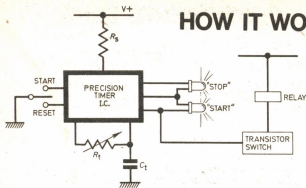

A precision timer i.c. forms the basis of this design. An external RC network (R_1 and C_1) alters the frequency of an internal oscillator. When the oscillator has cycled 4095 times, the internal i.c. logic detects this and causes a transistor to switch off, thereby removing power from the relay coil and turning off the mains load.

Two complementary outputs are available on the i.c., and both are utilised to provide a visual indication by means of two l.e.d.s to signal whether the timer has "started" or "stopped."

The i.c. is both triggered and reset with one switch. Timing resistor R_1 is varied in steps by means of a rotary switch to allow different delays to be obtained. The Timer generates delays of between 1 and 12 hours, but in theory the i.c. can deliver delays of between about 15 microseconds and about 3 weeks.

The relay contacts switch the mains load off after the delay is up, but in this design by utilising both sets of changeover contacts, the load can be switched on or off after the delay.

supply to the i.c. with a normally-closed switch. Instead, however, a reset function was derived by grounding pins 4 and 5 with S2—this grounds the i.c. and resets it. Resistor R1 ensures that there is no danger of shorting out the supply, and R2 limits the peak current caused by C3 and C4 discharging to 0V.

By resetting the i.c. in this manner it was possible to incorporate the trigger (START) and RESET functions into one switch.

I.C. OUTPUT

Both of the i.c. outputs are used. When the i.c. is not timing, then pin 2 is high and pin 3 low. Therefore output current flows out of pin 2 and sinks into pin 3, illuminating D5 to indicate the timer has stopped. Light emitting diode D6 cannot illuminate because it is reverse-biased by about two volts. Resistor R15 limits the current flowing in the l.e.d. to less than 10mA—generally enough to cause an easily visible glow.

Upon commencement of the timing period (IC1 being triggered by S2), pin 3 goes high and pin 2 low—D5 must therefore extinguish and D6 illuminates to indicate that the timer has started timing. Also, TR1 switches on with pin 3 going high. This completes the circuit to RLA which now operates. Resistor R17 is a series dropping resistor and is necessary to

enable the 12V 110 ohm relay to be used with a 17V supply. A transistor

is required because the i.c. cannot possibly supply the 110mA or so required by the relay.


Switch S4 has been incorporated to allow a MANUAL operation of the relay independently of the Timer which switches on the relay itself and illuminates D8 to indicate the manual function.

RELAY

The relay used in the prototype was an R.S. Open Type 348-835 which is equipped with a pair of 10A 250V a.c. changeover contacts. Socket SK1 is connected to the mains through the normally-closed contacts. When the relay operates, these contacts open and switch off the load connected to SK1 which switches on again when the Timer is reset or times out.

The opposite is true of SK2. When the unit is timing, SK2 switches on and switches off when the unit times out. The use of these "complementary" sockets means that any load can be turned on or turned off when the Timer has completed its cycle.

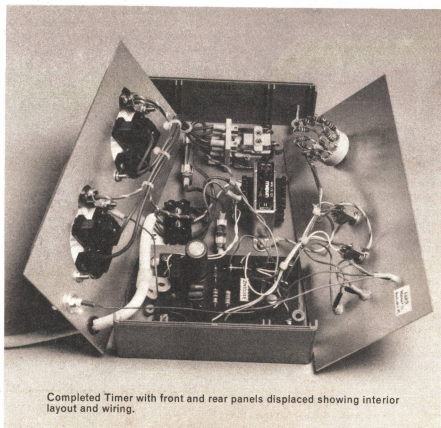In the final design, the relay contacts have been derated to 7.5A by means of FS1 so that neither the relay contacts or the mains interwiring can be operated at their absolute maximum ratings. Fuse FS2 protects the transformer in case a fault should develop.



Completed Timer with front and rear panels displaced showing interior layout and wiring.

CONSTRUCTION starts here

CIRCUIT BOARD

The circuit is built on a glass fibre printed circuit board for high reliability and strength. The foil layout and component overlay is shown actual size in Fig. 3. The prototype was made using etch-resistant transfers for the tracks and resist ink for the larger areas of copper foil.

There are several points which must be observed when soldering the components to the p.c.b. Firstly make absolutely certain of the polarity of C1. Also ensure the correct orientation of D7. Finally, whilst an i.c. socket was not used on the prototype, it is recommended that one is used to prevent thermal damage to the rather expensive i.c. during soldering. Complete the p.c.b. in accordance with Fig. 3 and then move on to the case-work.

CASE DETAILS

The prototype was housed neatly in a plastic Verobox type 75-1412K which has aluminium front and rear panels. The front panel should be drilled to take the three switches and three light-emitting diodes. Take care to ensure that the front panel is not scratched during this operation as this would greatly detract from its final appearance.

Letter the front panel as necessary and give it several light coats of lacquer for protection. A solid machine-turned aluminium knob and two different-coloured end caps for the miniature toggle switches completes the front panel and gives a very professional finish.

REAR PANEL

The rear panel must be punched or cut to take the two main sockets, mains cable inlet, and also SK3 if used. There will not be much room left on the rear fascia after the two mains sockets are in place, and so this stage of the construction needs to be planned with care.

If flush-fitting sockets are used, then two large cut-outs will be required; on the prototype this was very easily accomplished with a tank cutter and hand brace. Other methods include drilling a ring of holes, punching out the centre and then filing till smooth.

COMPONENTS

Resistors

R1	1-2k Ω
R2	10k Ω
R3-R14	390k Ω (12 off)
R15	220k Ω
R16	680k Ω
R17	47k Ω 1W
R18	1-5k Ω
All $\frac{1}{2}$ W carbon $\pm$ 5% carbon except R17 (1W)	

Capacitors

C1	1000 μ F 25V p.c.b. elect.
C2	0-1 μ F polyester
C3	1 μ F 35V tantalum
C4	0-1 μ F polyester
C5	3-3 μ F 35V tantalum

Semiconductors

D1-D4	BY164 60V 1-4A bridge rectifier
D5, 6, 8	TIL220 or similar i.e.d. with mounting clip (3 off)
D7	1N4001 or similar silicon diode
TR1	BFY52 silicon <i>n</i> p <i>n</i>
IC1	ZN1034E precision timer i.c. 14 pin d.i.l.

Miscellaneous

T1	Mains primary/12V 500mA secondary transformer
RLA	12V 110 ohm coil with two sets of changeover contacts rated at 250V 10A

S1	d.p.d.t. 10A mains toggle
S2	s.p.d.t. miniature toggle, centre biased
S3	1-pole 12-way rotary switch
S4	d.p.d.t. miniature toggle
SK1, SK2	13A 250V flat pin flush mains socket (2 off)
SK3	See text
FS1	1A 20mm
FS2	7-5A $\frac{1}{2}$ inch

Chassis fuse holders for FS1 and FS2; case, Verobox 75-1412-K; glass fibre p.c.b.; 14 pin d.i.l. socket; control knob; 13A cable and plug; p.v.c. insulated interconnecting wire; 10A mains interconnecting wire; 10A connecting block; coloured caps for S2 and S4 (one red and one green); p.c.b. mounting pillars.

See
**Shop
Talk**
page 19



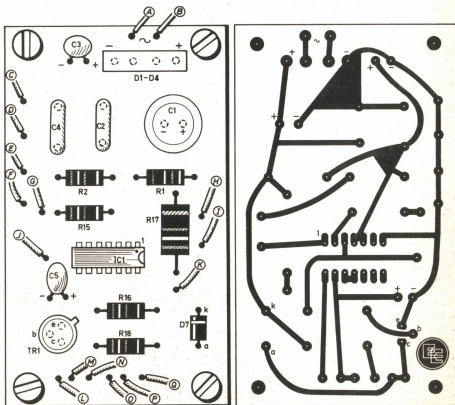
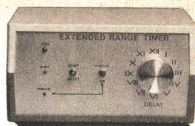
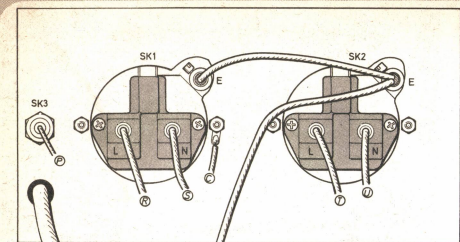
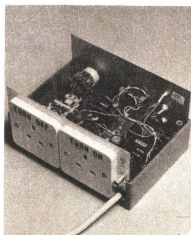
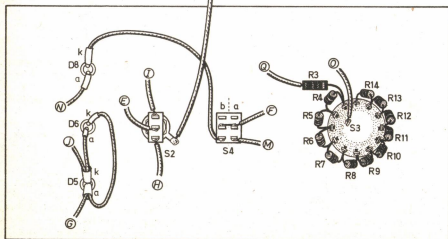


Fig. 3. Printed circuit board component layout and underside foil pattern (actual size).

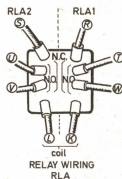

Mains On/Off Timer

Fig. 4. The case opened out to show the position of the internal components and the internal wiring. All cables carrying a.c. mains must be rated at 240V 13A. This includes the wiring to SK1, SK2, RLA, FS1 and T1 primary. The relay connections are shown below. These may differ if the specified relay is not used. Connections to locations on the p.c.b. are made using veropins.

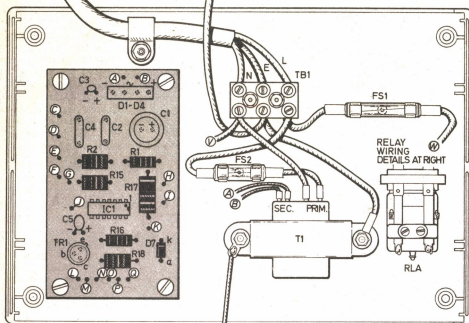

The resulting large holes were then slightly modified with an Abrafile to take the shape of the earth terminals of the mains sockets.

It will be seen that as the mains inlet hole must be very near the right hand edge of the panel, then an adjacent hollow pillar moulded into the base needs to be trimmed right down to allow the mains cable to pass through unhindered. This pillar must be cut with a hacksaw, making quite sure that you don't cut into the edge of the case itself.

A hole (or two holes, depending on the type of socket used) will be required for SK3, if used. If a BNC socket is used, as in the case of the prototype, then one hole only is needed, the 0V connection being made through the earth. If, for example, two 4mm sockets are used then provision has been made on the p.c.b. for a 0V connection to be extended to one of the sockets.

Fit the sockets to the rear panel and fit a grommet to the mains cable inlet hole. Letter SK1 and SK2 "turn on" and "turn off" respectively.

INTERNAL WIRING

The dark grey chassis is drilled to take the p.c.b. mountings, two fuse-holders, transformer, terminal block, relay and mains cable clamp. The positioning of these holes should be carefully marked out so that the holes do not foul with the pre-moulded pillars in the base. The mains cable clamp is a nylon "P" clip which prevents the cable from being pulled out.


There is quite a lot of interwiring to be carried out but if Fig. 4 is followed carefully then no problems should arise.

All mains-voltage joints must be neatly soldered and insulated with p.v.c. sleeving, and all of this wiring is carried out with 10A (or greater) mains cable coloured blue, brown or green/yellow to coincide with the standard mains colour code. The transformer and FS2 can, however, be wired with normal 6A mains cable. The mains inlet must be rated at 13A. All other wiring can be carried out with lightweight hook-up wire, preferably stranded.

The relay connections shown in the diagram are for the specified relay only, and may differ if other makes of open relay are used.

EARTHING

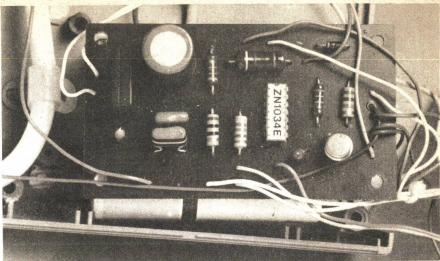Concerning the earthing arrangements, the front panel must be earthed using a very large earthing tag placed under one of the miniature toggle switches. An alternative here would be to solder the earth wire directly to the metal body of one of the switches. The rear panel is earthed



Close up view of the top of the p.c.b. showing component positioning and wiring.

with a 4BA solder tag under one of the mains socket mounting bolts. The 0V line of the p.c.b., and the transformer mounting bracket, are earthed in a similar fashion.

The wiring can be tidied up using nylon ties. The wires are arranged into looms, the tie is threaded around the loom and pulled tight. The excess is then snipped off. When forming the looms, keep mains cables away from low voltage wiring.

CHECKING AND SETTING UP

With all of the wiring completed, check carefully all aspects of your work. Check the p.c.b. for errors like reversed components or dry joints, etc. Recheck the mains wiring for quality and make sure that this is in order. Check the polarities of the l.e.d.s are correct.

If a multimeter is available, select a low ohms range and test for a low resistance between the earth pin of the mains plug and the front and rear panels. Test for infinite resistances between the earth pin and live and neutral pins of the plug.

If you are satisfied, fix down the top cover of the case, plug in and switch on. The STOP l.e.d. should be alight. Move S1 to START and allow it to return to centre off. The STOP indicator should extinguish and the START l.e.d. glow. The relay should also be heard switching in. Reset the timer at S1 and the relay should click out and the l.e.d.s switch over again.

Check now that the manual switch operates the relay and MANUAL l.e.d. when moved down. Set the knob for a one hour delay and start the timer; check that roughly a one hour delay is achieved. This last test will give a good indication of the accuracy to be expected with other delay settings. The prototype gave exactly 58 minutes delay on a one hour setting—this is

exactly the period calculated with the formula given earlier.

If a c.r.o. is available, then the basic oscillator period can be measured (up to a maximum three hour delay) and the expected time delay computed with the formula given previously.

If everything seems in order then try the timer on a very long delay setting to confirm its accuracy. Here again the prototype was less than ten minutes out on an eleven-hour setting.


USING THE TIMER

Someone will possibly want to use a cassette recorder with the device. This is in order provided that the cassette recorder is not allowed somehow to remain for long periods in the "play" position with the power removed. Otherwise the rubber pinch-wheel may possibly become physically distorted if it is kept "pinching" the tape against the capstan spindle for too long.

The timer can quite successfully be used with "auto stop" recorders to turn the power off altogether after the tape mechanism has stopped automatically at the end of a tape.

Finally it was discovered that in spite of the decoupling incorporated in the circuit, spurious noise generated by other appliances sharing the same socket being switched on and off sometimes reset the Timer. The Timer will not however start timing when a transient appears on the line.

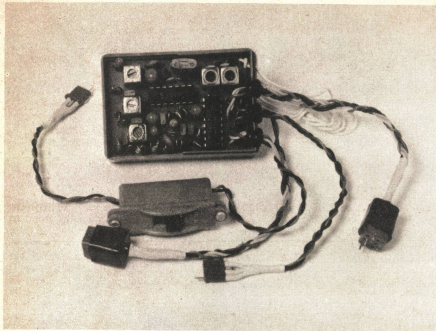The only way round this it seems is to use the timer and nothing else off one mains outlet, or plug into a suitable mains "suppression unit". It can be noted that the timer is not susceptible to transients generated by appliances in other parts of the building, and it is in order to share a mains wall socket with loads that are always on all of the time, like digital clocks, for example. □



By L. ARMSTRONG • H. DICKINSON • W. WILKINSON

PART THREE

EE RADIO CONTROL SYSTEM

RECEIVER DESCRIPTION AND CONSTRUCTION

This third part of the series deals with the receiver, its construction and the tuning-up procedure.

This receiver is as sensitive as most commercial receivers and is capable of working in the 25kHz spaced split frequencies provided reasonable care is taken to ensure that the adjacent channel transmitter is not nearer to the model than the control transmitter.

The receiver is housed in a small plastics case. External connections to the servos and the battery are made either by floating connectors attached to the ends of flexible leads, or via a connector block mounted directly on the p.c.b.

FLEXIBILITY

Any number of channels from one to seven may be used, the only difference being in the number of leads brought out. Individual sockets may be used for each channel if so required, or a mixture of single sockets and blocks as shown in the diagrams.

Any servo may be plugged into any receiver output channel provided that particular channel has a control stick on the transmitter. It is not necessary to use the control channels in any set order and the servos should be plugged into the channels required.

Once again i.c.s are used where advantageous, such as in the r.f. amplifier/oscillator stages and the decoder. This also helps to reduce constructional errors in these areas.

RECEIVER IN OUTLINE

A typical 27MHz receiver is shown in block diagram form in Fig. 3.1.

The transmitter signal is received by the aerial and passed on to a tuned circuit which has a high impedance to 27MHz signals but has a low impedance to signals of other frequencies. This ensures that a maximum 27MHz signal is passed to the radio frequency (r.f.) stage for amplification.

The crystal oscillator, which is usually of the third overtone type, runs at a frequency of 455kHz less than that of the transmitted signal.

When the oscillator signal and the output of the r.f. stage are fed into the mixer stage, the sum and difference frequencies of the two input signals are available at the output of the mixer. The output of the mixer is fed into a tuned amplifier which is tuned to 455kHz thus ensuring that only the signals spaced 455kHz away from the crystal oscillator frequency are amplified. This stage is called the intermediate frequency amplifier (i.f.).

The i.f. amplifier output is then fed into a detector stage which effectively removes the 455kHz signal and leaves only the modulation, the modulation in this case being the pulses necessary to drive the decoder circuitry which in turn drives the servos.

It can be seen that the first three stages of the block diagram Fig. 3.1 are contained in one integrated circuit IC1. This i.c. gives a reliable mixer stage which is necessary if repeatability of performance is to be obtained amongst receivers built by different constructors.

A conventional i.f. amplifier using transistors and transformers is used, this then feeds a transistor detector. It was considered whether to use ceramic filters to obtain a better selectivity, but suitable filters cost a few pounds and were not generally available, hence the choice of standard circuitry.

The rest of the receiver consists of the pulse amplifier, sync pulse detector stage and the decade counter decoder IC2 which decodes the pulses suitably for driving the servos.

CIRCUIT DESCRIPTION

In the full circuit diagram (Fig. 3.2) it can be seen that the aerial is connected to the primary of a double-

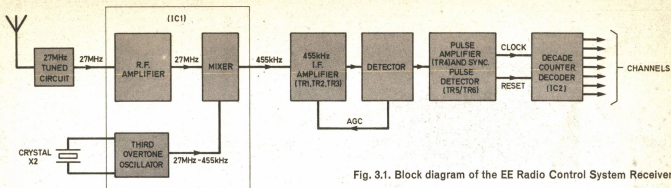


Fig. 3.1. Block diagram of the EE Radio Control System Receiver.

tuned r.f. circuit comprising inductance L1 and capacitor C2. A small capacitor C3 couples the primary tuned circuit to the resonant secondary circuit L2, C4. These two tuned circuits form a highly selective tuned input stage.

Impedance matching into the r.f. stage of IC1 is achieved by using the secondary of L2.

The crystal oscillator discrete components are the crystal X2 and three capacitors, C7, C8, C9; the remainder of the oscillator circuit being in IC1 itself.

MIXER STAGE

The r.f. stage output and the oscillator output are mixed internally, the output of the mixer stage (pin 2)

being fed into the primary of the first i.f. transformer T1 which is tuned to the difference frequency of 455kHz by its internal capacitor and adjustable ferrite potcore. The output of the untuned secondary drives the first i.f. amplifier TR1, the collector currents of TR1 and TR2 being determined by the emitter resistors and the base voltages.

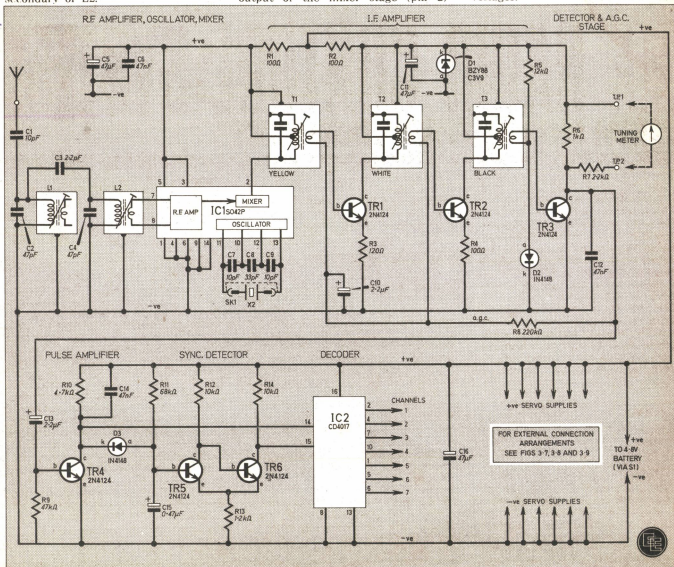


Fig. 3.2. Circuit of the EE Radio Control System Receiver.

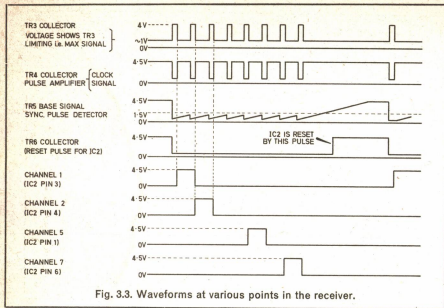


Fig. 3.3. Waveforms at various points in the receiver.

The second i.f. transformer T2 couples the signal into the second i.f. amplifier TR2 which in turn feeds i.f. transformer T3.

The secondary of T3 is connected between a forward biased diode D2 and the base of detector transistor TR3. The forward voltage of 0.5V across D2 is insufficient to turn on TR3 which needs approximately 0.65V base voltage for this purpose. It can be seen therefore if the secondary of T3 supplies a 300mV peak-to-peak i.f. signal, the positive peaks will add to the 0.5V thus supplying the base voltage needed and so turn on TR3.

The larger the signal, the larger the voltage swing at TR3 collector until the maximum swing of (supply voltage—0.4V) is reached. Smoothing capacitor C12 has the effect of changing the 455kHz peaks into a mean d.c. voltage whose d.c. level varies with signal strength, the larger the signal the lower the d.c. voltage at TR3 collector.

When a 200µsec "interruption" in signal occurs (which constitutes a channel gap from the transmitter), TR3 has insufficient base voltage and turns off, capacitor C12 charging swiftly up to positive rail via R6. When the signal resumes, TR3 turns on again discharging C12 and the "interruption" becomes a "pulse". In this way the transmitted pulses are reconstituted at TR3 collector.

AUTOMATIC GAIN CONTROL

Since the d.c. level at TR3 collector is dependent upon signal strength, it is fed via R8 to the bases of the two i.f. amplifier transistors TR1, TR2, the pulse interruptions in signal being "smoothed out" by capacitor C10. In this way the gain of the i.f. amplifier is controlled by the incoming signal strength, since the mean d.c. vol-

tage at TR3 collector drops with large signals thus decreasing the base voltages of TR1, TR2, hence their gain.

The signal from TR3 collector is fed via C13 to the pulse amplifier TR4 which has no bias and hence requires 0.6V pulse to trigger it thus giving a measure of noise immunity. The output at TR4 collector is approximately a 4.5V peak-to-peak signal and is used to "clock" the decoder IC2.

DETECTION OF SYNC PULSE

In order that "Channel 1" always appears at the same output pin of IC2 it is necessary to detect the end of a block of pulses and reset the counter IC2. It is for this purpose that the sync pulse was inserted into the pulse train and this is now detected by D3, R11, C15.

Under no-signal conditions the collector of TR4 is high and hence C15 charges up via R11. When the pulses appear, C15 is discharged to approximately 0.7V via D3, TR4.

The time constant of C15, R11 is such that C15 cannot recharge between channel pulses, but only in the sync pulse period which is relatively long. The voltage across C15 is therefore fed into a level detector TR5, TR6 which has a high output when C15 is charged up and vice versa. Hence under no-signal conditions, or during sync pulse, C15 is charged up and TR6 collector is high thus resetting the decoder IC2 ready for the next pulse train.

DECADE COUNTER AND DECODER

The decoder IC2 is a CMOS five-stage Johnson decade counter with built-in code converter. The ten decoded outputs, of which only seven

are used, are normally low and only go high at their appropriate decimal time period. The output changes occur on the positive-going edge of the clock pulse and the outputs appear in rotation as shown in the waveform diagram, Fig. 3.3.

The sequence of events is therefore as follows:

Assuming sync pulse time, TR6 collector is high thus resetting IC2. The negative-going edge of the first clock pulse takes TR6 collector low thus removing the reset from IC2.

When the positive edge of the first pulse occurs, output 1 of IC2 goes high and remains high until the positive edge of the second block pulse, whereupon output 1 returns to the low state and output 2 goes high. This remains high until the positive edge of the third clock pulse when output 2 returns low and output 3 goes high.

This sequence carries on for each clock pulse up to 7 when the sync pulse occurs and resets IC2. All the outputs are set low again ready for the next pulse train.

Hence it can be seen each output goes high for the period between two adjacent clock pulses thus reconstituting the original pulse from the transmitter for that particular channel.

CONSTRUCTION
starts here

The receiver is built on a small printed circuit board, Fig. 3.4. Location of components is given in Fig. 3.5.

As with the transmitter, the importance of using a good soldering iron with a small bit must be stressed.

Good joints are most essential here as it is the receiver that will be taking all the knocks and bumps in your model, so any dry and loose joints will be a hazard to its survival. A skilled and practised hand in soldering miniature components is demanded. This is NOT a task for a novice to undertake.

CIRCUIT BOARD

Construction is started with the insertion on to the p.c.b. (plain side) of wire links.

"Link A" goes from IC2 pin 6 to "Channel 7" pad.

Link "B" goes from IC2 pin 12 to position shown. This is for an optional "fail-safe" facility, to be described later.

The r.f. tuned circuits can now be inserted, then the i.f. cans making sure in the case of the latter that

EE RADIO CONTROL RECEIVER

COMPONENTS RECEIVER

Resistors

- R1 100 Ω
- R2 100 Ω
- R3 120 Ω
- R4 100 Ω
- R5 12k Ω
- R6 1k Ω
- R7 2-2k Ω
- R8 220k Ω
- R9 47k Ω
- R10 4-7k Ω
- R11 68k Ω
- R12 10k Ω
- R13 1-2k Ω
- R14 10k Ω

All $\frac{1}{2}$ W carbon $\pm 5\%$

Capacitors

- C1 10pF ceramic plate
- C2 47pF ceramic plate
- C3 2-2pF ceramic plate
- C4 47pF ceramic plate
- C5 47 μ F tantalum bead 6-3V
- C6 47nF ceramic disc 12V
- C7 10pF ceramic plate
- C8 33pF ceramic plate
- C9 10pF ceramic plate
- C10 2-2 μ F tantalum bead 35V
- C11 47 μ F tantalum bead 6-3V
- C12 47nF ceramic disc 12V
- C13 2-2 μ F tantalum bead 35V
- C14 47nF ceramic disc 12V
- C15 0-47 μ F tantalum bead 35V
- C16 47 μ F tantalum bead 6-3V

Semiconductors

- TRI-6 2N4124 npn silicon (6 off)
- D1 BZY88C3V9 Zener diode 3-9V
- D2, 3 1N4148 silicon diode (2 off)
- IC1 SO42P R.F. amplifier, tuner & oscillator (Siemens)
- IC2 CD4017 CMOS decade counter

Inductors

- L1, 2 Tuned r.f. coil Toko 113CN-2K159 (2 off)
- T1 i.f. transformer, yellow Toko 4827
- T2 i.f. transformer, white Toko L238
- T3 i.f. transformer, black Toko 4825

Miscellaneous

- Receiver case (SLM)
- $\frac{1}{4}$ inch grommets (3 off)
- Printed circuit board
- Connectors—as required, see text (SLM)
- Connecting wire (10 strand), various colours. Heat shrinkable plastic tubing.
- Nicad battery box, 4 $\times$ HP7, (SLM)
- S1 Noble slide switch d.p.d.t., with box (SLM)
- SK1 crystal socket, low profile (SLM)
- X2 Crystal (see Part 2)

See
**Shop
Talk**
page 19

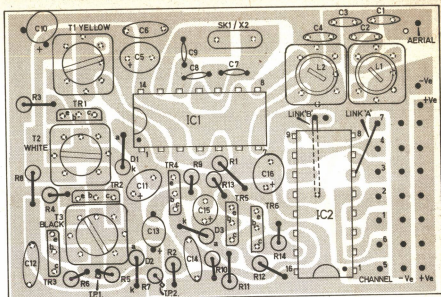


Fig. 3.5. Top view of the printed circuit board with all components in situ. The pattern on the other side of the board is shown in grey to assist when fitting components. Note the two links "A" and "B" which must be fitted before any components are mounted. T.P.1 and T.P.2 are "tuning points"—for connection of multimeter.

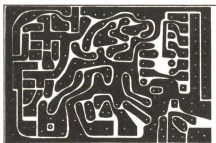


Fig. 3.4. Printed circuit board for the EE Radio Control Receiver, actual size.


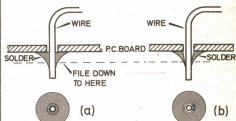


Fig. 3.6. (a) Good joint, any filing shows just solder and wire; (b) Bad joint; filing reveals wire with ring of solder and air gap between the two.

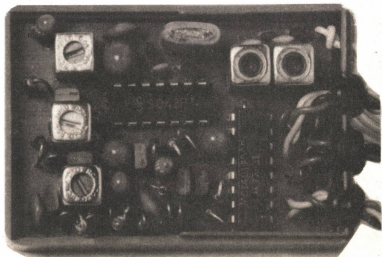

they are inserted in the correct place (identified by their coloured tuning core).

The integrated circuits IC1 and IC2 are inserted next. Take care with IC2 as this is one of those CMOS devices. If in doubt follow the precautions suggested in the transmitter construction section.

The order of placement for the remaining components is not critical, however a suggestion is to insert the physically smaller components first. Make sure that the diodes, tantalum capacitors and the transistors are all inserted the correct way round.

The uppermost leads of R5 and R7 should be bent to form tuning points.

When mounting the crystal socket take care no solder gets down the leads as this will ruin it.

PLUGS AND SOCKETS

The choice of plugs and sockets for connecting between the receiver and servos is left entirely to the constructor as it is dependent upon whether it is to be compatible with parts of an existing system. In the case of the "first time" constructor then Figs. 3.7 and 3.8 show how to connect to the connector block, in this case the SLM 7-way 3-pin type.

This block can be used either as a floating connector on the end of flexible leads, or mounted directly on to the p.c.b.

The writer's preference is to use floating connectors rather than a p.c.b.-mounted block connector, since as the receiver is invariably wrapped in sponge rubber the servos may be plugged or changed in at will without disturbing it. Hence a suggested wiring scheme if more than four channels are required could be as follows:

A single 3-pin socket on a flying lead is used for the first channel since this is invariably the aileron channel and the servo is mounted in the wing of the plane. The remaining channels are wired to the connector block as shown, the battery supply feeding into the plug on the block. When ordering the connector block specify 7-way block and cover (6 sockets plus 1 plug).

The power pins on the blocks are wired in parallel as shown. Two or three strands from the hook-up wire are twisted together and tinned. The wire is then wound round the pins and soldered.

After all the leads are connected, check them *very carefully*. Then cover the back of the block and the joints with 5-minute epoxy and slip the cover on to the back of the block. The epoxy when set fixes the pins and wires into a solid block and prevents any single connector from pulling out of the block.

AERIAL

The aerial should be a 30-inch length of light flexible cable similar to that used for the leads.

FINAL EXAMINATION

When all the wiring is completed (including the servo leads), the bottom of the board should be cleaned to remove any flux. The board should be scrutinised for any solder bridges between tracks and these removed.

Another trick is to file the heads off all the joints and then clean the board again. This usually shows up any dry joints since these *cannot* be tolerated. Think of the model and your time mending it!! See Fig. 3.6.

CHECKING AND TUNING-UP

Measure the resistance between the battery supply leads with a multimeter on the ohms range. It should read approximately 1k Ω with the leads one way round and 100 Ω the other way round. If much less check for shorts on the back of the p.c.b. and check parts placement.

If the measurements prove correct then connect the correct way round to a 4.8V supply and the following measurements should be checked with reference to the "0" volts (-ve) rail. Measurements should be done under no-signal conditions, that is with the transmitter switched off.

1. Pin 2 IC1	approx. +4.5V
2. Emitter voltages of TR1, TR2 measured at top of R3 and R4	approx. +0.25V
3. Can of i.f. transformer T3	approx. +3.9V
4. Collectors of TR1, TR2	approx. +3.9V
5. A.G.C. supply voltage (top of R8/collector of TR3)	4.5V
6. Base of TR3	0.6V
7. Collector TR4	4.8V
8. Collector TR5	1.3V
9. Collector TR6	4.8V

Should any of the above measurements be incorrect then check the placement of the components associated with them.

If the measurements are correct, then plug in the matching crystal into the socket SK1. Place the transmitter, less aerial, very close to the receiver.

Connect a multimeter (of 5k Ω /volt a.c. minimum) on the lowest a.c. voltage range nearest 1V between the tops of resistors R7 and R5 (T.P.1 and T.P.2).

Switch on transmitter. If the receiver is anywhere near in tune the meter will start to indicate. Make sure the receiver aerial is clear of any

metal work, etc.

Adjust the i.f. transformers T1, T2 and T3 for maximum voltage deflection then L1 and L2, gradually moving the transmitter further away to keep the meter reading below 0.5V (as this is the maximum deflection obtainable).

Each time the reading approaches 0.5V, progressively move the transmitter further and further away adjusting L1, L2 and T1, T2 and T3 to peak the reading. The meter may well be 10 to 15 feet away at this stage.

The receiver should now be in tune.

If a servo is available, plug it into channel 1 lead, which should be the aileron, and move the transmitter stick to get a servo movement. Typical range with one servo and with no aerial on the transmitter should be about 15 to 20 feet. If no servos are available then this test will have to await next month's issue when the servos will be described.

ALTERNATIVE TUNING METHODS

Two other tuning techniques are available, the first being to connect a crystal earphone between T.P.1 and T.P.2 where the tone of the pulse train can be heard. The same tuning sequence is used to peak the tone to its maximum loudness and clarity.

The other technique is to connect an oscilloscope to the test point T.P.1 and T.P.2 and tune-up watching the waveform. R7 should be increased to 10k Ω in this case. The waveforms are as in Fig. 3.3.

FITTING IN CASE

Depending on whether a p.c. block or flying leads are used, the appropriate holes should be cut in the lid of the receiver case with a modeller's knife or file.

The receiver aerial exits from the case via a small hole and the aerial wire should be knotted on the inside so that no strain is applied to the connection on the p.c.b. if the aerial is tugged.

The p.c.b. assembly should be fitted into the box base and a piece of sponge rubber (about $\frac{1}{4}$ inch thick) cut such that when put on top of the receiver, the crystal socket SK1 is uncovered (as is the connector block, if used). This sponge rubber prevents the receiver rattling about in the case and also stops the board lifting when the crystal is removed. The receiver case top should then be fitted and the whole sealed with tape. The receiver is now completed.

BATTERY ASSEMBLY

Fit four Nicad cells into that half of the Nicad holder with the hole in the end. See Fig. 3.11.

Fig. 3.7. The receiver wired for seven channels, using floating connectors. The slide switch S1 and the Nicad battery box are also shown.

EE RADIO CONTROL RECEIVER

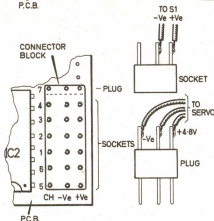
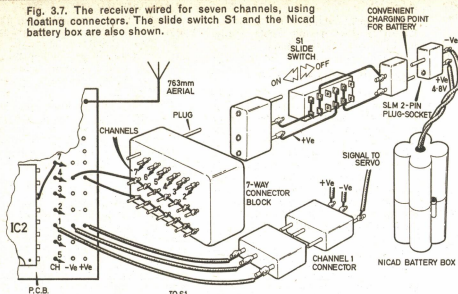


Fig. 3.8. The receiver wired for seven channels using 7-way connector block mounted directly on p.c.b. External connections are via one socket and six plugs.

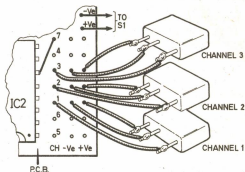


Fig. 3.9. The receiver wired for three channels using single sockets.

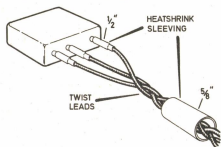


Fig. 3.10 (left). Wiring of single plugs and sockets and fitting of shrinkable plastic sleeves. Apply heat (e.g. from hair drier) and sleeves will shrink to half original diameter, thus securing the lead connections.

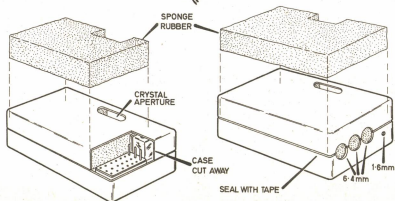


Fig. 3.12. Receiver case showing cut-outs required and sponge rubber pad.

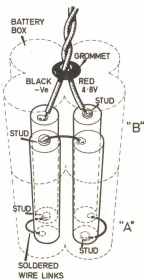


Fig. 3.11. Wiring of the four Nicad cells and their installation within the battery box.

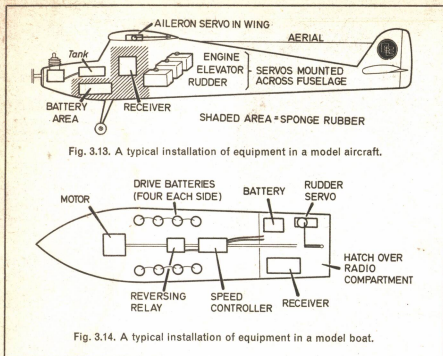


Fig. 3.13. A typical installation of equipment in a model aircraft.

Fig. 3.14. A typical installation of equipment in a model boat.

Wire the exposed ends of the cells as shown at "A". Fit other end of holder over this wired end, invert box and remove top cap. Wire this end now as "B" taking care to fit the battery supply wires through the grommet and the top before connecting to the cells. Finally screw the two halves of the Nicad box together.

INSTALLATION IN A MODEL

Arrangement of the equipment in a model is usually shown on the model plans. If such information is not available, it is suggested that a book on the particular line of modelling in question should be purchased.

These specialist publications give a lot of useful advice based on experience. In a plane for instance, a typical installation is as shown in Fig. 3.13.


Note the battery is installed at the front so that in the event of a crash the battery does not rush forward and batter the receiver to certain death.

The battery and receiver should be well packed in foam rubber. The servos can either be mounted on commercially available servo trays (which even hold the on/off switch), mounted on bearers by woodscrews and the mounting grommets supplied with each servo, or just fixed inside the model using double-sided adhesive tape.

TRANSMITTER

The transmitter circuit diagram Fig. 1.3 should be amended as follows:

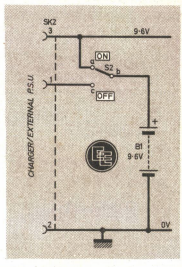- (i) To conform with Fig. 2.6 and conventional numbering of DIN sockets, renumber SK2 pins as shown below
- (ii) Add letter code to S2 contacts. (Second pole is not used, but slider contact (e) provides anchor point—as in Fig. 2.6.)



In the case of a boat it is best to waterproof all the equipment where possible. This can be easily achieved by putting the receiver battery, receiver and servos inside a plastic sandwich box. It is advisable to mount the speed controller and changeover relay near to the motor in order to cut down any voltage loss which can occur with today's powerful electric motors.


Next Month: Servos and speed controller.

JACK PLUG & FAMILY...

BY DOUG BAKER



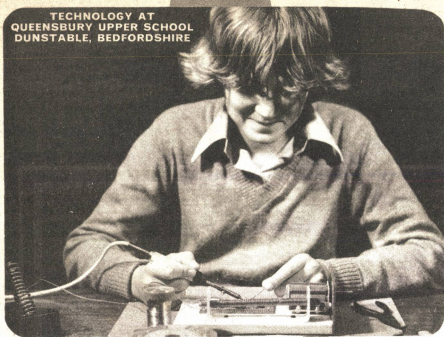TECHNOLOGY AT
QUEENSBURY UPPER SCHOOL
DUNSTABLE, BEDFORDSHIRE



School Report

By M. H. S. Higley

Electronics was introduced into Queensbury School curriculum in September 1974 and then, shortly afterwards, the subject of Design Technology. Both of these subjects are taught within the Craft, Design and Technology department, under the title of Design Technology, and satisfy the School's desire to provide a link between Mathematics/Science and Craft.

Pupils who study Design Technology find they are able to build the AND, NOT and OR gates which they encounter in Computer Studies. Likewise, the very elementary electronics knowledge the pupils obtain in Physics is extended both

in theory and practice during Design Technology lessons.

Exams

The public examinations taken by pupils, having completed the two year Technology course, are C.S.E. Electronics and, either C.S.E. or 'O' level Technology. Within the next two years it is hoped to have six former students studying at 'A' level.

Electronic components are, of course, expensive and the constructional projects undertaken by the pupils, in the main, employ discrete components as many of the integrated circuits available are far too expensive for school use. However,

the 741 op. amp and T.T. Logic (TTL), in the 7400 series, are used extensively because these are extremely useful and also inexpensive.

Projects

Recently, they have been experimenting with the ZN414 integrated circuit radio "chip" and this may become the basis of a standard receiver for the pupils. Several simple circuits are used as an introduction to the world of electronics such as, a single transistor radio receiver, a moisture detector, a light operated switch and an elementary metal detector. These are projects which ideally suit the inexperienced constructor. The more advanced pupils have in the past constructed a manual telephone exchange, a digital clock, a logic tutor box and a differential amplifier which is used to demonstrate electrocardiograph techniques.

Work now in progress includes a full-adder demonstration unit using TTL and a model high-speed commuter train driven by an air-screw. This particular project will have circuitry to start, stop and reverse the vehicle at pre-determined points along the track.

Ident-light

One pupil is investigating the possibility of identifying people using a light detector which could be employed in police work or in hospitals. His theory is that different features reflect varying amounts of light and by scanning the face with a light measuring device an electrical output can be obtained which can be stored in many ways.


With the assistance of the Computer Studies department, he will write a BASIC program to store his data in the computer and also carry out a comparison check against previously stored data.

Careers


The projects vary in their complexity but it is hoped that all the pupils gain some insight into the ever-expanding fields of electronics. Having experienced the various courses offered through the School curriculum they are better able to choose the career that is suited to their ability.

It is not the intention to produce complete electronic engineers within the school system but to enable the pupils to make the correct choice of career and thence go on to higher education. Should they find in later years they require to cross over into another field then with a good background of Mathematics, Science, English and an appreciation of Technology the transition would be that much easier.

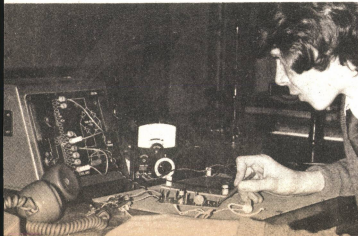A fifth year pupil taking voltage measurements on the circuit board of his Metal Detector.



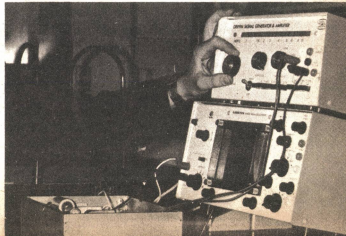A sixth former checking the frequency response of his Mullard 10W Amplifier.





Memory Lane

This being the festive season my indulgent Editor kindly allows me to wander down memory lane and rattle a few old skeletons. In the past I have related incidents in my life that I thought were interesting or amusing without any particular regard to chronological order. This year I thought I would go back in time to my earliest recollections, to see at what point I became entangled in electronics.

It all began when I was about five and was given for my birthday one of those lovely old torches. Perhaps you know the ones. They have a huge bulbous lens and take the Ever Ready 1289 battery. Perhaps they are still around, the batteries are still on sale.

It's amazing after all these years, I think Lawrence of Arabia said the streets of Mecca were lit by electricity while we were still wearing wood. I expect the Arabs used 1289 batteries!

Shock Treatment

Where was I? Oh yes the large torch. Like all small boys I soon reduced it to its component parts and found I could do things with the battery and bulb on their own. I put the bulb in a small aspirin bottle hung it over my bed and wired it up to the battery under my pillow.

So far so good, but I quickly learned that small batteries are soon exhausted, and that led to my next experiment, a more disastrous one. Having decided the battery was dead because there was no electricity in it, where should I get some more? Why of course in the light socket. I promptly removed the bulb and placed the battery contacts on the studs. The result was a violent flash and new fuses required all round.

Moving on a year or two I made the interesting discovery that if two pieces of wire were connected to a battery and joined by a short length of very thin wire it would soon get red hot. The thin wire was placed in the hole in the end of a cotton reel while the hole was filled with gunpowder.

The idea was undoubtedly to explode it from a safe distance. Unfortunately while I was busy stuffing the gunpowder into the hole the two wires somehow contrived to make contact with the battery and caused the loss of my eyebrows, the first of many times it was to happen in my chequered career.

Crystal Clear

It was shortly after that, that crystal sets began claiming my attention. My father brought home a most exquisitely made Marconi set. Rather like a small black attache case with two plated knobs at either side which slid in and out for tuning.

Inside the lid was a panel with switching arrangements for different lengths of aerial and for changing from galena crystal to carborundum. The wiring inside was fantastic, all 16 gauge square sections and every bend an exact right angle. Alas it was several years before they discovered that r.f. currents dislike going round sharp corners and tend to fly off at a tangent. My father was delighted with it and told my brother and I that "Gamages are selling them off for ten bob (50p) and they originally cost fourteen pounds". Even so, we found a simple set using a variometer worked much better.

We then made the amazing discovery that the higher the aerial the louder the sound. Each week we would buy a length

of bamboo pole and push it up another ten feet. The trouble was that each extension had to be thinner than the last until ultimately they were so thin and bent so much that the height advantage was lost.

We made another useful discovery at this time. We found we could run three pairs of earphones from the same set. My father had one pair in the living room and my brother and I each had one by the bed.

We found that to communicate with our parents, we could take off the earphones and talk into them instead of bawling at the top of our voices. This did have its drawbacks. According to my father, I cannot guarantee the veracity of the story, he said he was listening to the news which went as follows "Last night Queen Mary was seen going out with Dad!" The last word being supplied by one of his erring children probably wanting a glass of water. Mind you I have always regarded this story as highly suspect!

Enter the Valve

I had now reached the ripe old age of eleven and was staying in the house of a gentleman who owned a valve set. These had to be seen to be believed. Each valve was turned on slowly by a rheostat, to-day we would call it a variable resistor, and you really could read a newspaper from the light they gave out.


Masses of wires led to an h.t. battery that weighed half a hundredweight, an accumulator fit for a car, and a grid bias battery about a yard long. An enormous coil and slider at the top of the set and two swinging coils on the side, plus a fearsome array of dials and knobs completed the receiver, and crowning all this mammoth out-fit a tiny little horn speaker made by someone called "Brown".

We would all gather round it expectantly and after sundry howls and noises reminiscent of a cat having its tail trodden on, with any luck a squeaky voice would come out of the horn. "This is 2LO London calling in the British Isles, tonight ladies and gentlemen we have for your entertainment that well known comedian Leonard Henry". I wonder how many of my readers remember this or similar announcements.

Say what you will, it was great fun. We were all enthusiastic because we felt we were in at the beginning of a great achievement, and I am delighted to say, those of us in Electronics, to-day, are experiencing the same feelings all over again.

The Adventures of Tanty Bead

By Matthew Read

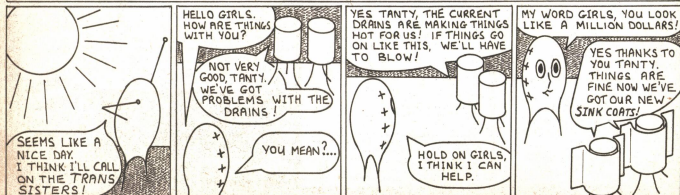

CMOS			
4001	13p	4025	13p
4002	13p	4026	90p
4003	13p	4027	28p
4009	30p	4028	40p
4011	13p	4029	80p
4012	13p	4040	55p
4013	28p	4041	55p
4015	50p	4042	55p
4016	28p	4043	55p
4017	47p	4044	55p
4018	55p	4045	55p

FULL DETAILS IN CATALOGUE!

TTL			
7400	10p	7473	20p
7401	10p	7474	22p
7402	10p	7475	20p
7404	12p	7486	20p
7406	22p	7489	13p
7408	12p	7490	25p
7410	10p	7492	30p
7413	22p	7493	25p
7414	39p	7494	45p
7420	12p	7495	35p
7427	20p	7496	45p
7430	12p	74121	25p
7432	18p	74122	35p
7442	38p	74123	38p
7447	45p	74125	35p
7448	50p	74126	35p
7454	12p	74132	35p

OPTO

LED's	0.125in, 0.2in	each	100+
Red	TIL209	TIL220	7p
Green	TIL211	TIL221	13p
Yellow	TIL213	TIL223	13p
Clips	3p	3p	
DISPLAYS			
DL704	0.3in CC	130p	120p
DL707	0.3in CC	130p	120p
FND500	0.5in CC	100p	80p

SKTS

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p
3 feed TO18 or TO9 socket	10p	each			
Solderless pins	100-500	1000-370p			

PCBS

VEROBOARD			
Size in.	0.1in, 0.15in.	Vero	Cutter 80p.
25 x 1	14p		
2.5 x 3.75	15p		
2.5 x 5	54p	Pin insertion	
3.75 x 5	64p	tool 100p	
3.75 x 17	205p	185p	
Single sided			
pins per 100	40p	40p	
Top quality fibre glass copper board. Single sided. Size 203 x 55mm. 50p each.			
'Dalo' pens. 75p each.			
Five mixed sheets of Alfac. 145p per pack.			

RESISTORS

Carbon film resistors.			
High stability.			
Low noise 8%.			
E12 series. 4.7 ohms to 10M. Any mix:			
each	100+	1000+	
0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg ohm (850 real 0.5W £7.50, 0.25W £5.70).			
METAL FILM RESISTORS			
Very high stability. Low noise rated at 1W			
1%.			
Available from 51ohms to 330k in E24 series. Any mix:			
each	100+	1000+	
0.25W	4p	3.5p	3.2p

WE WISH ALL
OUR CUSTOMERS
A MERRY CHRISTMAS
AND A
HAPPY NEW YEAR

LINEAR			
THIS IS ONLY A SELECTION!			
LF356	80p	NE531	98p
LM301AN	28p	NE556	23p
LM308	60p	NE566	60p
LM318N	75p	NE567	100p
LM324	45p	RC4136	100p
LM339	45p	SN76477	230p
LM378	230p	TBA800	70p
LM379	410p	TBA805	100p
LM380	45p	TDA1022	60p
LM390	55p	TLO81	45p
LM395	65p	TLO84	125p
CA3045	55p	2N414	80p
CA3080	70p	2N4256	390p
CM1458	32p	2N4256	390p
MM5760	590p	2N10346	200p

TRANSISTORS

BC107	17p	BCY72	14p	ZTX500	16p
BC127	17p	BD131	35p	2N697	12p
BC132	15p	BD132	35p	2N3053	18p
BC178	18p	BD139	35p	2N3054	50p
AD161	38p	BD140	35p	2N3055	100p
AD162	38p	BFY50	15p	2N3442	135p
BC107	8p	BFY51	15p	2N3702	8p
BC108	8p	BFY52	15p	2N3703	8p
BC109	8p	BFY53	15p	2N3704	8p
BC109C	10p	BFY54	15p	2N3705	8p
BC109D	10p	BFY55	15p	2N3706	8p
BC148	7p	BFY56	15p	2N3707	8p
BC177	14p	BFY57	15p	2N3708	8p
BC178	14p	BFY58	15p	2N3709	8p
BC179	14p	BFY59	15p	2N3710	8p
BC182	10p	BFY60	15p	2N3711	8p
BC182L	10p	BFY61	15p	2N3712	8p
BC182L	10p	BFY62	15p	2N3713	8p
BC184	10p	BFY63	15p	2N3714	8p
BC184L	10p	BFY64	15p	2N3715	8p
BC212	10p	BFY65	15p	2N3716	8p
BC212L	10p	BFY66	15p	2N3717	8p
BC214	10p	BFY67	15p	2N3718	8p
BC214L	10p	BFY68	15p	2N3719	8p
BC217	14p	BFY69	15p	2N3720	8p
BC278	14p	BFY70	15p	2N3721	8p
BC278L	14p	BFY71	15p	2N3722	8p
BC279	14p	BFY72	15p	2N3723	8p
BC279L	14p	BFY73	15p	2N3724	8p
BC279L	14p	BFY74	15p	2N3725	8p
BC279L	14p	BFY75	15p	2N3726	8p
BC279L	14p	BFY76	15p	2N3727	8p
BC279L	14p	BFY77	15p	2N3728	8p
BC279L	14p	BFY78	15p	2N3729	8p
BC279L	14p	BFY79	15p	2N3730	8p
BC279L	14p	BFY80	15p	2N3731	8p
BC279L	14p	BFY81	15p	2N3732	8p
BC279L	14p	BFY82	15p	2N3733	8p
BC279L	14p	BFY83	15p	2N3734	8p
BC279L	14p	BFY84	15p	2N3735	8p
BC279L	14p	BFY85	15p	2N3736	8p
BC279L	14p	BFY86	15p	2N3737	8p
BC279L	14p	BFY87	15p	2N3738	8p
BC279L	14p	BFY88	15p	2N3739	8p
BC279L	14p	BFY89	15p	2N3740	8p
BC279L	14p	BFY90	15p	2N3741	8p
BC279L	14p	BFY91	15p	2N3742	8p
BC279L	14p	BFY92	15p	2N3743	8p
BC279L	14p	BFY93	15p	2N3744	8p
BC279L	14p	BFY94	15p	2N3745	8p
BC279L	14p	BFY95	15p	2N3746	8p
BC279L	14p	BFY96	15p	2N3747	8p
BC279L	14p	BFY97	15p	2N3748	8p
BC279L	14p	BFY98	15p	2N3749	8p
BC279L	14p	BFY99	15p	2N3750	8p
BC279L	14p	BFY100	15p	2N3751	8p

DIODES

1N914	3p	1N4005	6p
1N4001	4p	1N4001	4p
1N4002	4p	1N4002	4p
1N4003	4p	1N4003	4p
1N4100	4p	1N4100	4p

CAPACITORS

TANTALUM BEAD			
0.1, 0.15, 0.22, 0.33, 0.47, 0.68,			
1 & 2.2uF @ 35V			
4.7, 6.8, 10uF @ 25V			
22 @ 16V, 47 @ 6V, 100 @ 3V			
MYLAR FILM			
0.001, 0.01, 0.022, 0.033, 0.047			
0.068, 0.1			
POLYESTER			
Multilayer C280 series			
0.001, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 5p			
0.15, 0.22			
0.33, 0.47			
0.68			
1.0uF			

Everyday News

A MICRO LASHING FOR INDUSTRY

Judging from the many stories published in these pages over the last year, we find it hard to believe a statement and report from the Minister of State for Industry that less than a third of Britain's top 1,000 companies are applying microelectronics in their business.

This is the finding of a MORI survey conducted for the Department of Industry and revealed recently by Lord Trenchard, Minister of State for Industry.

Brief extracts of a speech he made at a recent London seminar on "Technology and Organised Labour" are given below:

"The lack of British microelectronic applications is reinforcing the huge productivity gap between the UK and our major competitors and provides an explanation as to why UK unit labour costs are so high while our wage levels remain so low."

"In 1978-79 unit labour costs were increasing at a rate of 10 per cent in the UK, twice as fast as in the USA and almost five times as fast as in Germany. Japanese unit labour costs were actually declining at over 3 per cent."

Viewdata Boost

A promise to build thousands a month of viewdata TVs during 1980 has been made by ITT and they will be able to receive the Post Office Prestel Service.

This will go a long way towards remedying Post Office complaints that Britain's TV industry has been producing too few sets, therefore retarding wider use of Prestel. ITT forecast that by 1985 there will be over a million business users of Prestel and 600,000 domestic users.

GOLDEN AGE

This year's President of the Institution of Electrical and Radio Engineers, Professor William Gosling, called his inaugural address "Electronics—a profession in its golden age".

He pointed out that for the first time in human history we can create artefacts of more than biological complexity and from materials that are as common as dirt.

"I have just returned from Japan whose post-War performance is outstanding. I believe that there are two secrets in the Japanese miracle. First, they really accept that the foundation for a high standard and quality of life must be industrial success and expansion. Secondly, within their companies, they all work together for efficiency and profit. Negotiation of entirely dependable agreements with one union only, in no way conflicts with the drive of all employees towards constant change and greater efficiency."

"With regard to the absolute dependability of agreements and the freedom, indeed requirement, for management to introduce constant change and improvement in Japan, it is not generally realised that even with well ordered industrial relations, it is quite difficult for a factory manager to 'spare up' more than 20 per cent of his time for the introduction of new methods and new sys-

tems to move his company forward. Eighty per cent of his time is already mortgaged in carrying out essential routine duties. If he has to spend up to 50 per cent of his time in constant negotiation at many levels the show moves backwards and not forwards."

"The challenge before us today is whether we can, by combining will with technology right across our industrial and commercial operations, lift ourselves off the lower rungs of the productivity ladder in order to generate the wealth we all need to improve the quality of life for all our people."

"Microelectronics provides us with a means to meet this challenge."

"Why then is it that less than a third of Britain's top 1,000 companies are already applying microelectronics to their production processes, purchasing, design, quality control, and products? This was a finding in a MORI survey commissioned by the

Department of Industry to monitor our national microelectronics awareness campaign."

"The answer is that effective application of microelectronics requires a radical change in work habits and attitudes from the boardroom to the factory floor. The whole company has to learn a new way of operating."

"The MORI survey disclosed that some 5 per cent of the top 1,000 British companies reckon that they have already lost market share because of failure to apply microelectronics and another 9 per cent expect to suffer losses for the same reason."

"In the United States, over 750,000 new jobs have been created during the last three years in California, the home of 'Silicon Valley', while over 5 million new jobs have been generated over the last four years in the USA as a whole. Of even greater significance was the finding of the Birch Report that small firms in the USA employing 20 or fewer people generated 66 per cent of all new jobs. Many of these small firms have come forward on the wave of microelectronic inventions and applications that have been sweeping through the USA."

"There is no reason why we in the UK should not seize our share of these new opportunities, if we turn our attention as a nation away from the sterile internal debates between 'we' and 'they' on whichever side of the fence we are and focus all our energies on acquiring the skills necessary to exploit the new technology whatever our current status or job functions."

The finance may be there, but the millions of pounds investment needed at the new interest rate could make the final unit cost too high for the purchaser?

No doubt readers will have their own views?

A big future for video discs for home entertainment is expected by RCA following a signing with Paramount and Rank for the supply of feature films.

By 1990, RCA estimate that video disc players will have captured as much as 50 per cent penetration of all homes with colour TV with possibly 40 million units in service.

SAFETY IN THE HOME

Originally published to give guide-lines for safety in domestic radios, successive editions of the British Standards Institution safety requirements has had to take in more and more household electronic equipment. The latest edition, now entitled "BS 415 Safety requirements for mains-operated electronic and related apparatus for household and similar general use", specifies safety requirements for a whole range of mains electronic equipment now available for use in the home. It includes monochrome and colour television receivers, radio receivers, clock radios; stereo amplifiers, tuners and turntables; record players, music centres, tape recorders, video cassette recorders, and electronic musical instruments.

Auxiliary equipment provided for use with this apparatus is also covered, e.g. microphones, loudspeakers, cable connected remote control devices and battery eliminators.



... from the World of Electronics

ANALYSIS

THE MIRACLE INGREDIENT

System X sounds as if it ought to be one of those new formula consumer products promising better action with less effort at lower cost. But System X is no soap substitute. It is the new generation of digital electronic telephone exchanges which are now being constructed and will be installed in ever-increasing numbers in the 1980s. The first large System X exchanges being installed in 1980 and operational in 1981.

If all goes well it certainly promises better action with less effort for the consumer though whether at lower cost remains problematical. And System X also has a miracle ingredient.

The advantage of going all-digital is that a digital network can handle any type of information without discrimination. The system sees no difference between digitized speech or data or facsimile or telephone answering machines or automatic diallers or teleconferencing or wake-you-up calls or radiopaging or Prestel terminals. Once you change everything into digits you get a complete communications and information system on one network.

A digital system also has a big money-saving spin-off in management statistical information, automatic billing to the customer, automatic self-testing and fault diagnosis, and overload control which at busy periods will hopefully solve queuing and rerouting problems.

A small miracle had to happen in the first place to make this mammoth project feasible. This was to get the equipment manufacturers talking to each other and to the British Post Office with everyone, so to speak, on the same wavelength instead of competing with each other as in the past. GEC, STC and Plessey needed to reveal their engineering secrets to each other as well as to the Post Office. And it actually happened, although not without difficulty.

A central theme of System X is that it is not only good for the UK but for the rest of the world as well. The world telephone network of 400 million lines today is expected to grow to a staggering 1,400 million lines by the end of the century and System X could capture 10 per cent of the world market.

It raised a lot of interest at the recent international Telecom '79 show at Geneva where it was the only large scale digital system shown in actual operation as distinct from wall diagrams and glossy pamphlets from other countries.

The first-ever public demonstration was a triumph but it raises the spectre, ever-present with high technology, of being before its time, of already being obsolescent before getting into service.

But have we not forgotten the miracle ingredient? The modular architecture of System X in both hardware and software is such that it can always be up-dated to take advantage of new components and technology. Moreover, it can be tailored to interface with any existing equipment anywhere in the world and can be expanded at will to accommodate more or different services as they become demanded by the user.

Brian G. Peck

THE ELECTRONIC OFFICE

The electronic office was a big feature of the International Business Show at Birmingham where 430 exhibitors reported a good attendance. But, as one observer reported, the huge display of electronic equipment for the office of the 80s was not matched by the mass

of new office furniture, very little of which was designed to accommodate the electronics.

The beginning of a Japanese low-cost invasion was spearheaded by the first UK showing of the Sharp desk-top personal computer priced at from £520 plus VAT.

Britain's Airborne Early Warning (AEW) system is running to schedule. The tactical communications system comprising 120 different electronic units has been ground-tested and is now being air-tested in a special trials aircraft. Main contractor for both the airborne radar and communications is Marconi Avionics Ltd.

The Rank Organisation expects to sell 5,000 colour TVs a year in Israel following the recent introduction of colour TV. The Rank sets will be distributed through Electra of Israel.

VIDEO AWARD

The Sony Corporation has been awarded its third Emmy by the National Academy of Television Arts and Sciences for its role in developing the one-inch Videotape recorder for broadcast production.

Sony developed its one-inch BVH series of recorders in 1976. Since then, one-inch VTRs have been rapidly replacing the two-inch format equipment in television stations around the world.

PERSON-to-PERSON

The chance to speak person-to-person to Post Office telephone subscribers anywhere in the country from the privacy of their own vehicle is now possible through the Network radiophone service.


Believed to be the first time an independent message-handling contractor has been granted a licence to break the Post Office's monopoly on telephone communications, the new service is now operational throughout the Greater Manchester area.

Through the Network service's transmitter at Salford, the motoring businessmen can now be "plugged" directly into the Post Office telephone system making it possible to make and receive calls to and from anywhere in Britain or abroad.

Subscribers to the system are charged £60 a month for the rental of the equipment and service, and allowed up to 40 free local telephone calls a month made or received over the Post Office telephone lines. They are only charged for incoming calls if they agree to accept them from the operator.

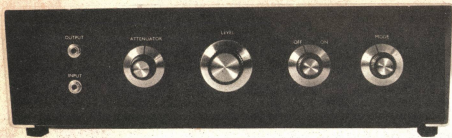Perhaps, when radiophones become standard fittings in new vehicles the sight of vandalised public call boxes and long queues will be a thing of the past.—A commercial venture here for the "new" Post Office?





SPRING-LINE REVERB UNIT

BY R. A. PENFOLD

REVERBERATION is caused by sounds bouncing around the floor, ceiling and walls of a room, and tends, to a certain extent, to sustain sounds and merge them into one another.

Many types of music benefit from a suitable amount of reverberation and sound rather "flat" if it is absent. This can be something of a problem for the home-recording enthusiast because the carpets, curtains and furniture of most homes tend to have good sound absorbing properties, giving very little reverberation.

Fortunately it is possible to artificially add reverberation to a signal using a unit such as the one described in this article, and very realistic results can be obtained in this way. There are several ways of producing the reverberation artificially, but using a spring-line unit is probably the best low-cost method, and is the one employed here.

The unit can also be used with an electric guitar or an electronic organ or other electronic instrument as an effects unit, and can produce very interesting results.

BLOCK DIAGRAM

The block diagram seen in Fig. 1 shows the basic stages in the circuit of the reverberation unit. The input signal is taken to a buffer stage which gives a reasonably high input impedance of about 100 kilohm. Some of the output from this stage is taken to a mixer, and then to the output by way of an output level control.

The rest of the output from the buffer stage is coupled to an audio power amplifier via a volume control type attenuator. The output from the power amplifier is used to drive the spring-line unit.

A spring-line basically consists of a long coiled wire spring having a

transducer at each end. One transducer is fed with the output from the power amplifier, and it converts this signal into sound waves which travel down the spring comparatively slowly due to its inertia. The transducer at the other end of the spring picks up these sound waves after a short delay, and converts them back into electrical signals.

The sound waves are not totally absorbed, however, and are reflected backwards and forwards along the spring numerous times before they die away to an insignificant level. These reflected waves are picked up by the output transducer each time they reach the appropriate end of the spring, and this gives the required reverberation signal.

The reverberation signal is mixed with the main signal, and the attenuator at the input of the power amplifier controls the level of reverberation signal that is added to the ordinary signal. A switch is used to disconnect the ordinary signal from the mixer when only the reverberation signal is required.

The reverberation time, i.e. the time taken for the reverberation to decay to an insignificant level (-60dB), depends upon the type of spring-line

utilised in the project, but is approximately 2.5 to 3 seconds if the specified unit is used. This is ideal for most applications.

THE CIRCUIT

The circuit diagram of the reverberation unit is shown in Fig. 2. TR1 and its associated components form the input buffer amplifier connected in the emitter follower mode so that it provides the necessary fairly high input impedance, and a low output impedance to drive the following circuit with little loss of signal level due to loading.

Capacitor C3 couples some of the output from the buffer stage to the reverberation level control, VR1. From here the signal is coupled direct into the non-inverting input of the audio power amplifier which uses a LM380N device (IC1). The inverting input of IC1 (pin 6) is earthed to the negative rail in order to prevent stray pick up here. Capacitor C5 decouples the supply to the input stages of IC1, and this helps to improve the low-frequency stability of the circuit.

The output from IC1 is coupled to the input transducer of the spring-line unit by way of d.c. blocking

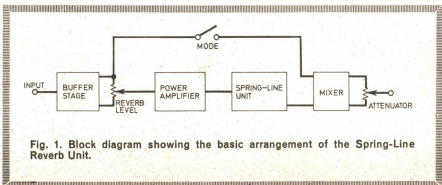


Fig. 1. Block diagram showing the basic arrangement of the Spring-Line Reverb Unit.

KITS FOR SOUND EFFECTS AND OTHER PROJECTS

PHONOSONICS

DEPT EE9D, 22 HIGH STREET,
SIDCUP, KENT DA14 6EH

P.E. GUITAR EFFECTS PEDAL

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls. Basic parts with foot switches

KIT 451 £8.45
KIT 45-2 £5.95
PCB 42A £1.57
Text photocopy 78

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit including variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Can be used with other electronic instruments.

Set of basic components KIT 56-1 £7.57
PCB & layout chart PCB 56A £1.78
Text photocopy 78

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit. Set of basic components, PCB & chart

KIT 74-1 £4.97
Text photocopy 39

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration. Basic comp., foot switches, PCB & chart

KIT 75-1 £5.64
Basic comp., panel switches, PCB & chart KIT 75-2 £4.98
Text photocopy 38

P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control. Set of basic components, PCB & chart

KIT 91-1 £3.99
Text photocopy 38

P.E. AUTO-WAH UNIT

Automatically Wah or Swell sounds with each note played. Basic comp., foot switches, PCB & chart

KIT 75-1 £5.64
Basic comp., panel switches, PCB & chart KIT 75-2 £4.98
Text photocopy 38

P.E. THREE-CHANNEL SOUND-TO-LIGHT

A simple sound-to-light controller. Set of basic components, PCB & chart

KIT 52-1 £14.16
Text photocopy 24

COMPONENT SETS include all necessary res., caps., pots, t/fomers. Hardware such as cases, skis, knobs, hds, etc. are not incl., but most can be bought separately. Fuller details in lists.

ADD: POST & HANDLING

U.K. orders: under £5 add 25p, over £20 add 50p, over £20 add 75p. Recommended insurances against postal mishaps: add

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

P.E. PHASER

An automatic 6-stage phasing unit with integrator. Set of basic comp., PCB & chart

KIT 59-1 £19.14
KIT 59-2 £19.14
Text photocopy 68

ELEKOR PHASING & VIBRATO UNIT

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 3-input mixer stage.

Set of basic components KIT 70-1 £19.11
PCB & layout chart KIT 70A £2.56
Text photocopy 67

P.E. PHASING UNIT

A simple but effective manually controlled phasing unit. Set of basic components, PCB & chart

KIT 25-1 £3.52
Text photocopy 28

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses. Set of basic components, PCB & chart

KIT 59-1 £19.11
Text photocopy 68

P.E. SMOOTH FUZZ

Set of basic components, PCB & chart

KIT 91-1 £3.99
Text photocopy 38

TREMOLO UNIT

A slightly modified version of the simple P.E. unit. Set of basic components, PCB & chart

KIT 54-1 £4.97
A slightly modified version of the original P.E. unit. Set of basic components, PCB & chart

KIT 28-1 £4.98
Text photocopy 38

P.E. MICROPHONE PRE-AMP

Includes preset gain control to match most microphones, bass roll-off, treble lift, master gain control.

Set of basic components, PCB & chart

KIT 61-1 £4.20
Text photocopy 38

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic comp., PCB & chart KIT 46-1 £16.42
Power Supply comp., PCB & chart KIT 46-2 £4.99
Text photocopy 97

P.E. TUNING INDICATOR

A simple 4-active frequency comparator for use with synthesizers and other instruments where the full versatility of KIT 46 is not required.

Basic comp., PCB & chart, but excl. sw. KIT 60-1 £8.19
Text photocopy 58

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels. Set of basic components, PCB & chart

KIT 60-1 £8.19
Text photocopy 58

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 3-digit counter for 1Hz to 999kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Set of basic components KIT 79-1 £38.45
PCB (as published) PCB 79A £3.33
Text photocopy 78

TAPE NOISE LIMITER

Effectively reduces tape-recording hiss. Set of basic components, PCB & chart

KIT 6-3 £4.13
Power Supply comp., PCB & chart KIT 6-2 £3.15
Text photocopy 19

P.E. DISCOSTROBE

4-channel sound-to-light controller also giving sequential, random or strobe modes of control. Set of basic components

KIT 57-1 £29.80
PCB 57A £3.79
Text photocopy 78

MANY MORE KITS

for synthesizers, Rhythm Generators, Electronic Pianos and other projects, big, small, simple or complex, are available, plus a range of keyboards, separate components and accessories. Details in our lists.

TERMS: C.W.O. MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL: 01-362 6164)





Random Electronic

EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box & descriptive instructions.

Complete or Kit

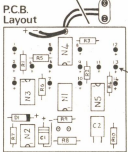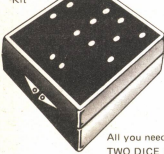

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

a *Self Assemble Dice

£3.95 + P&P 25p

b *Ready built Dice

£4.75 + P&P 25p

Order now from: **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk IP473-210151

Amount enclosed £

Name

Address

please state amount required in appropriate box ☐ a ☐ b

TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course—or refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

Courses in
C & G Elect. Technicians
C & G Elect. Installations
Telecoms. Technicians Exams
Television Servicing
Radio Maint. & Repairs (BIET)
Pract. Radio & Electronics
Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept. TEES1 Reading RG7 4PF.

NAME (Block capitals please)

ADDRESS

POSTCODE

Other Subjects

AGE

Accredited by CACC

Member of ABCC

CONSTRUCTION

starts here

The layout of the unit is not critical, and the arrangement used for the prototype can be seen from the illustrations.

will be required if insulated case jack sockets are used.

USING THE UNIT

The unit is intended to be used in a high-level signal path, with an input level of about 50 to 1000mV r.m.s. It is unlikely that really good results will be obtained operating the unit from a low-level source such as a dynamic microphone, since the signal to noise ratio will inevitably be effectively reduced. Far better results would be obtained by interposing a suitable pre-amplifier between the source and the reverberation unit.

Except with input levels of about 50mV r.m.s. or less, full reverberation will be reached before VR1 is advanced to its fully clockwise setting. Taking it beyond the point at which full reverberation is achieved would simply cause the signal at the output of IC1 to clip, producing severe distortion on the output signal.

With S2 switched to the position where the ordinary signal is muted and only the reverberation signal is obtained the unit will act as an interesting effects unit for an electronic instrument. It is particularly effective with instruments that provide a glissando signal, as it then gives a weird but not unmusical wailing sound.

INTERIOR WIRING

All the point-to-point wiring of the unit is illustrated in Fig. 3. S1 and S2 are rotary types on the prototype (S2 being one pole of a 4-way 3-pole type having an adjustable end stop set for 2-way operation), but toggle or slider types can be used if preferred.


The input and output terminals of the spring-line unit are clearly marked, and the leads to the input transducer can be connected with either polarity. One of the output terminals is connected to the metal casing of the spring-line by a solder-tag which is ready wired into place by the spring-line manufacturer.

Assuming a metal case is used there is no need to make a connection to this terminal since it will be earthed to the negative supply rail through the cabinet, which is in turn earthed by the negative supply connection to SK2. Using a separate connecting wire would probably produce an earth loop with consequent instability. Socket SK1 also receives its earth connection via the metal case. However, an earth wire to each socket

THE CASE



A suitable component layout for the unit using a stripboard having 36 holes by 17 strips is shown in Fig. 3. Drill the two 6BA or M3 clearance mounting holes and make the 10 breaks in the copper strips before soldering in the components and three link wires. The semiconductor devices should be the last components to be soldered into circuit.

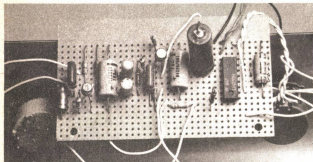The case needs to be a fairly large type in order to accommodate all the components, and in particular the spring-line unit which is a little over 200mm in length. The largest size Vero "G range" case makes a very attractive housing for the project and is used as the cabinet for the prototype unit, but any case of about the same size should also be perfectly suitable.




The finished circuit board removed from the chassis.

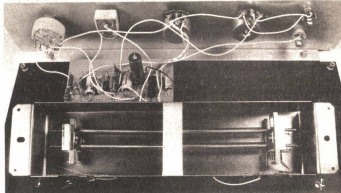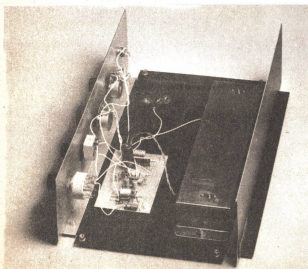The case "surround" removed showing positioning of circuit board and Spring-Line module.



Interwiring to the front panel controls and detail of the Spring-Line module.

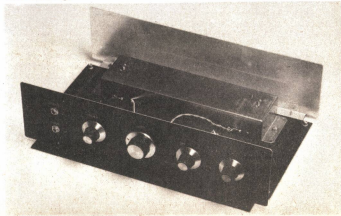The completed Spring-Line Reverb showing front panel controls and lettering.




Now, the complete MK 14 micro-computer system from Science of Cambridge

VDU MODULE. £33.75

(£26.85 without character generator) inc. p & p.

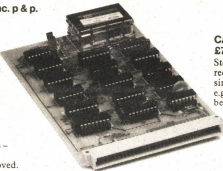Display up to ½K memory (32 lines x 16 chars, with character generator; or 4096 spot positions in graphics mode) on UHF domestic TV. Eurocard-sized module includes UHF modulator, runs on single 5 V supply. Complete ascii upper-case character set can be mixed with graphics.





POWER SUPPLY. £6.10 inc. p & p.

Delivers 8 V at 600 mA from 220/240 V mains – sufficient to drive all modules shown here simultaneously. Sealed plastic case, BS-approved.



CASSETTE INTERFACE MODULE. £7.25, inc. p & p.

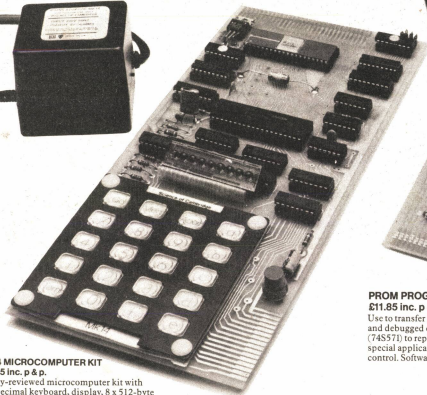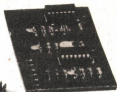Store and retrieve programs on any cassette recorder. Use for serial transmission down single line at up to 110 baud (teletype speed), e.g. over telephone line, and to communicate between two or more MK 14s.



MK 14 MICROCOMPUTER KIT

£46.55 inc. p & p.


Widely-reviewed microcomputer kit with hexadecimal keyboard, display, 8 x 512-byte PROM, 256-byte RAM, and optional 16-lines I/O plus further 128 bytes of RAM.

Supplied with free manual to cover operations of all types – from games to basic maths to electronics design. Manual contains programs plus instructions for creating valuable personal programs. Also a superb education and training aid – an ideal introduction to computer technology.

Designed for fast, easy assembly; supplied with step-by-step instructions.

PROM PROGRAMMER. £11.85 inc. p & p.

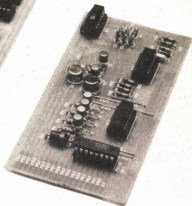Use to transfer your own program developed and debugged on the MK 14 RAM to PROM (745571) to replace SCIOS monitor for special applications, e.g. model railway control. Software allows editing and verifying.



To order, complete coupon and post to Science of Cambridge
Return as received within 14 days for full money refund if not completely satisfied.

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs, CB2 1SN.

Please send me:

- ☐ MK 14 standard kit @ £46.55.
- ☐ Extra RAM @ £4.14 per pair.
- ☐ RAM I/O device @ £8.97.
- ☐ VDU module including character generator @ £33.75.
- ☐ VDU module without character generator @ £26.85.

- ☐ Cassette interface module @ £7.25.
- ☐ PROM programmer @ £11.85.
- ☐ Power supply @ £6.10.
- ☐ Full technical details of the MK 14 System, with order form.

All prices include p & p and VAT.

I enclose cheque/MO/PO for £ _____ (total).


Name _____

Address (please print) _____

Science of Cambridge Ltd

6 Kings Parade, Cambridge, CAMBS, CB2 1SN.
Tel: 0223 311488.

EE/1/80

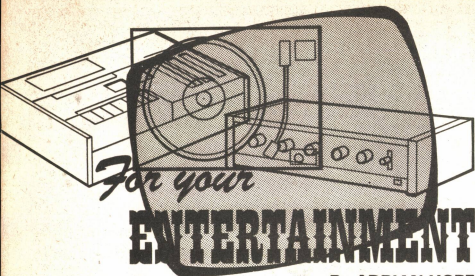

By ADRIAN HOPE

Singing Lights

Have you ever noticed how electric light bulbs, especially of high wattage "sing" when run off a thyristor dimmer switch? The singing is usually most pronounced when the switch is set at a half-way position.

The reason for this seems pretty clear. The thyristor dimmer works by biting chunks out of the 50Hz mains sine waveform and they are taken out so sharply that the waveform ends up with squared edges. These square edges generate high frequency harmonics which cause interference on medium and long wave radio sets.

It also seems reasonable to deduce that some of the lower frequency harmonics fall in the audible range. By electro-magnetic induction these set the coils of the lamp filament vibrating at an audible pitch. In other words the coils of the lamps behave just like the coils and laminations, which can emit mechanical buzzes and hums of an infuriating level.

Given the fact that the use of a dimmer will vibrate the coiled filament mechanically, an interesting thought now arises. Surely this continual mechanical vibration of the lamp filament can't exactly lengthen the lamp's life.

It has become a factoid (Norman Mailer's delightful term for an unsubstantiated fact that finds its way into the folklore) that the use of a dimmer prolongs lamp life because it cuts down on cold current surge and consistently under-runs the lamp. But over the years I have been led to the reluctant conclusion that lamps run on dimmers need replacing at least as often as lamps run on simple on/off switches.

Could it be that the disadvantage of mechanical vibration outweighs the advantage of limited current surge, so that the use of a dimmer actually shortens, rather than lengthens, lamp life?

Frozen picture

A low dosage X-ray machine produced by EMI Pantak and International Aeradio is being installed at Gatwick and Heathrow airports for airline security baggage inspections. The new RapideX X100 machines will not fog film and development of X100 represents an interesting change in policy by EMI Pantak.

The company had previously supplied Heathrow with RapideX high dose machines which fog passenger's film, even when shielded by protective lead bags. The original machines generated an X-ray dose of at least 17 milliroentgens per second and as the inspection process takes up to ten or twelve seconds (for instance if the operator looks closely at a suspicious object) the baggage under inspection may receive a total of up to 200 milliroentgens.

The advantage of the old machines is a very clear picture which reveals the presence of any metallic weapon, however carefully concealed. The disadvantage is a very unhappy passenger who has forgotten to remove all cameras and film beforehand, or relied on shielding by a protective lead bag.

Low dose X-ray systems, as already used by many airports around the world, expose the baggage only briefly to low level radiation. The resultant X-ray picture is then frozen on a fluorescent screen and artificially brightened by an image intensifier.

Low dose systems do not fog film and will not penetrate the lead shield. If the operator sees the opaque outline of a lead bag the passenger is asked to open it for visual inspection. Public pressure has now forced the London airports to follow the rest of the world and install low dose systems.

The new RapideX X100 uses a similar strength of radiation to the original machine but for just one hundredth of a second. The picture is then frozen on a memory tube.

There is certainly no noticeable effect on photographic film. Pictures taken on even very fast colour stock, rated at 400ASA, and exposed thirty times to the X100 radiation dose, show barely noticeable fogging.

Airline passengers passing through London will thus no longer need to

remember to remove all unexposed film from their baggage for pre-flight security checks.

Queen's English

The Texas Instruments Speak and Spell toy (previously mentioned in this column) is now available in a version which speaks something approaching the Queen's English. The basic three-chip synthesiser circuitry includes a ROM which can be programmed to speak any words in any language.

But the original Speak and Spell was modelled on an American voice, with American pronunciation and the visual display shows American spelling. So anomalies like "color" for "colour" and "skedule" for "schedule" are buried in the ROM to confuse British-speaking users.

Although it is an expensive business to completely reprogramme the ROM, and change the speech accent, Texas has now altered the programme sufficiently to eradicate the most obvious "Americanese" anomalies. Unfortunately, both original and re-programmed models are on sale virtually side by side and it is very hard to distinguish one from the other.

The circuitry synthesizes words from the ROM in purely random fashion and a potential customer might have to test the toy for hours before hitting by chance on a tell-tale word like "honor". Fortunately, there is a very simple way to distinguish the two models.

The Z key on the British version has been re-programmed to say "zed" whereas the American version still says "zee". So anyone buying a Speak and Spell to help their children's education would be well advised to press the "Z" key before parting with their money.

Speak and Spells are already available for under £40 and the price, especially of now obsolete Americanese versions, will probably drop further. Texas is using the basic 3-chip circuitry for a whole range of new applications, for instance a language translator which speaks in a foreign language.

Without doubt there will be all kinds of new speaking gadgetry on the market from Texas and other firms over the next year or so and their prices will fall just as calculator prices have plummeted over recent years. So think twice before buying at current prices.

Is it a Mental Breakdown?

That said, I have to admit to finding Speak and Spell a fascinating gadget, and while playing with one on loan for a week discovered a delightful trick which you can play on it.

In order to expand the Speak and Spell's vocabulary, there is provision for an extra ROM in the form of a plug-in module. A "module" key on the keyboard makes the content of the new memory accessible to the synthesizer circuit.

If you press the "module" key, but fail to insert the module, the synthesizer circuitry makes its usual random search for instructions and will sooner or later try to delve into the non-existent ROM. When this happens the synthesizer goes haywire, asking the operator to spell non-existent words, phrases and sounds. So pathetic is the garbled sound that only the hardest heart can fail to feel sorry for the confused electronics burling as if in final, demented death throes.

SAXON ENTERTAINMENTS

P.A. & DISCOTHEQUE
EQUIPMENT AT
INCOMPARABLE PRICES

STANDARD CENTAUR 100W

£309 incl. of carr & VAT Deposit **£62.00**
12 months @ **£24.47** or 24 months @ **£14.19**

SUPER CENTAUR 200W

£366 incl. of carr. & VAT Deposit **£74.00**
12 months @ **£28.94** or months @ **£16.78**

GXL 200W With Twin 200 Watt Cabinets

£470 + Carr £15 & VAT £32.32 Deposit **£94.00**
12 months @ **£37.27** or 24 months @ **£21.40**

GXL WITH PDF BINS (illus.)

£502 + Carr £15 & VAT £34.56 Deposit **£102.00**
12 months @ **£39.44** or 24 months @ **£23.00**

CUSTOM CENTAUR 400/600W

WITH FOUR PDF 100A BINS

£833 incl. of carr & VAT Deposit **£167.00**
12 months @ **£66.03** or 24 months @ **£38.28**

CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY
TWIN LOUDSPEAKERS & LEADS
100W-600W

20% DEPOSIT CREDIT TERMS



GXL + PDF BINS

- ★ 2 Year warranty
- ★ Full Mixing + Crossfade + Mic/Tape Inputs
- ★ Headphone & Cue Light Monitoring
- ★ Full Range Bass/Treble Controls + Mic Tone
- ★ 4 Channel Soundlight + Display

JUST PLUG IN AND GO !!
SEND TODAY FOR YOUR FREE BROCHURE

MINI DISCO 100 WATT

MONO SYSTEM WITH LOUDSPEAKERS

£229 incl. of Carr & VAT Deposit **£46.00**
12 months @ **£18.13** or 24 months @ **£10.52**

P.A. SYSTEMS

2 YEAR GUARANTEE
100 WATT

£207.00 incl. of carr & VAT Deposit **£42**

- 12 months @ **£16.35** or 24 months @ **£9.49**
- ★ Four Mixing Inputs
- ★ Bass & Treble Controls
- ★ Twin Piezo Horn Columns
- 200 WATT incl. of carr & VAT **£309.00**

12 months @ **£24.19** or 24 months @ **£14.19** Deposit **£62**

AMPLIFIER UNITS ONLY

AP100 AMPLIFIER

£56.92 + Carr £1.50 incl. of VAT

- ★ 4 mixed Inputs
- ★ Bass/Treble Controls
- ★ Vynide Case
- ★ 100 Watts Outout

AP200 AMPLIFIER

£102.92 + Carr £1.50 incl. of VAT

- ★ Six Mixed Inputs
- ★ Three Sets Bass/Treble
- ★ 200 Watts Outout
- ★ Slave Socket



NEW SAXON KLAXON

UK Police Hawaii 5.0 Destroyer

Four Sirens in one package incl. of VAT **£20.12**

Individual Sirens **£8.62**

NEW SAXON SMASH

ALIEN VOICE SIMULATOR

Add a new dimension to your disco with this press button effect unit. Insert between mic & amp **£8.62**

PLUTO PROJECTORS

P140 **£44.27**
150 WATT
INC WHEEL

P5000 **£102.92** incl. of VAT
250 watt .Q.I. inc Cassette/Wheel
(Full range of wheels - ask for list)



ELECTRET MIC D1501 **£21.27**

TOP QUALITY UNIT incl. of VAT

ECM105 LOW COST ELECTRET

CONDENSER MIC incl. of VAT **£5.75**

MELOS CASSETTE ECHO-REVERB UNIT-Twin input **£74.75**

VARIABLE SPEED & DEPTH incl. of VAT

AMPLIFIER MODULES

- ☐ 30Hz-20kHz
- ☐ Short/open circuit proof
- ☐ Top grade components
- ☐ Suit most mixers



SA308 8 ohms 30W 45V **£12.36**
Supply for 2 modules **£13.49**


SA604 4 ohms 50V **£16.47**
Supply for 1 or 2 modules **£17.19**

SA608 8 ohms 60W 65V **£17.42**
Supply for 1 or 2 modules **£17.19**

SA1204 4 ohms 120W 75V **£20.12**
Supply for 1 module **£17.19**

SA1208 8 ohms 120W 95V **£24.15**
Supply for 2 modules **£28.46**

DISCO MIXERS - COMPLETE OR MODULAR

 

MONO OR STEREO WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

FEATURES INCLUDE

- Twin Deck - Mic & Tape Inputs
- Wide range bass & treble controls
- Full headphone monitoring
- Crossfade - Professional standard performance.

COMPLETE MIXERS (with case)

Mono mains **£32.41**

Stereo mains **£73.31**

MODULES

Mono module **-31.62**

Stereo module **£45.12**
Panel **£4.54**
Kit of knobs/sockets etc **£8.32**

D.I.Y. MODULES FOR P.A. SYSTEMS MONO/STEREO

Input Modules

Mono PCB only **£7.47**

Stereo PCB only **£12.07**

Mono C/W Front panel **£10.92**

Stereo C/W Front panel **£15.81**

Mixer/Monitor Modules

Mono PCB only **£7.47**

Stereo PCB only **£12.07**

Mono C/W Front panel **£10.92**

Stereo C/W Front panel **£15.81**

Power supply to suit **£10.92**

send for full details.



make your own mixer Mono! Stereo up to 20 channels accept all inputs available as PCB only for complete on front panels

SOUND-TO-LIGHT UNITS



3 CHANNEL - 3kW **£33.92** incl. of VAT

Operator from 1W upwards

Bass/mid/treble/master + £1 carr complete

Module only **£22.71**

Panel **£3.39**

4 kW SOUNDLIGHT SEQUENCER (illus) **£46.57** incl. of VAT

NOT THE CARD

Dimmer on each channel

Automatic sound light level

Logic circuitry throughout

Module only **£20.76** Panel **£3.39**

MOTOROLA PIEZO HORNS £5.46 YES!!

FUZZ LIGHTS Red, Yellow, Green **£26.22**

HEAVY DUTY SPOT BANKS - MATCHES LOUDSPEAKERS

3 way 600W **£40.82** 4 way 800W **£47.72**

100W SPOTS

Red - Blue - Amber - Green **£1.72**

CABINET FITTINGS

- ICI Vynide 50" wide **£4.02m**
- Kick-res grille 50" wide **£4.02m**
- Netlon kick proof 24" wide **£4.02m**
- Cornet/feet/ress plates 17p
- Recess handle **£2p**
- Bar handles **£2.87**
- Bar plugs/sockets 29p

LOUDSPEAKER CABINETS - COMPLETE WITH LEADS

- ☐ Fitted with 100W 17,000 Gauss drivers
- ☐ Rugged cabinets with aluminium trim-black vinyl etc.
- ☐ Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24) **£50.60**

Large 100W 1 x 12 (65 x 48 x 24) **£62.67**

P.A. 1 x 12 (+2 Piezos) (80 x 38 x 24) **£82.22**

P.A. 2 x 12 200W (100 x 38 x 24) **£119.60**

Disco 2 x 12 200W (80 x 63 x 24) **£103.50**

PDF reflex bin (80 x 40 x 41) **£115.00**

PDF100 Reflex Bin - Twin Horns - Integrated Slave Amplifier - Accepts mono or stereo signals

- ☐ Use with all types of mixer
- ☐ Pan and volume controls
- ☐ Send for details **£155.25** Deposit **£31.25**

All inclusive of carr & VAT

ALL PRICES ARE INCLUSIVE OF 15% VAT.
Shop premises open Tues to Sat 9 am - 5 pm
Lunch 12.30 - 1.30 pm Mail order dept open
Mon to Fri 10 am - 4 pm Ring 01-484 6385

TO ORDER


By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclaycard Number

By Phone. You may order COD, Access or Barclaycard. Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS

327 Whitehouse Road, Croydon, Surrey.
All enquiries. Large SAE Please. Brochure on request

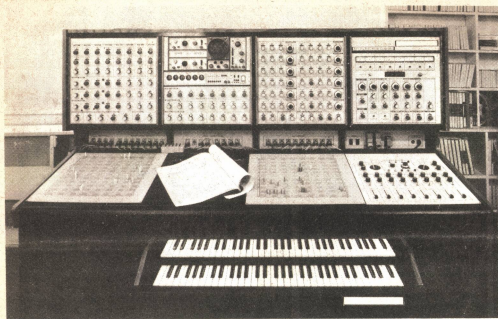MANCHESTER DISCO CENTRE, 237 DEANS-GATE, MANCHESTER. CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY



By B. H. Baily

Synthesisers

EXPLAINED PART 2

IN PART 1 we dealt with the basic principles of tone generation and envelope shaping in both electronic organs and synthesisers. We saw how the organ uses a set of oscillators and dividers to produce all the required notes or pitches for the entire organ, and the keyboard selects these when keys are pressed, but that in the monophonic synthesiser only one, two or three oscillators are normally used, and these are made such that each can produce a wide range of pitch, and can thus be called upon to produce any note over the whole keyboard, by applying a suitable voltage to its voltage control input.

We also saw how easy it is to memorise any such pitch by arranging for the voltage applied to be "stored" in a special sample/hold circuit, using a simple capacitor.

Already, the principle of voltage control has shown to be very valuable. But it does not stop at that. Just think of the numerous effects pedals you can now buy for guitars alone. Each of these contains a circuit which can be varied by mechanical means to give such effects as waa, waa, phase, etc. The circuits are designed such that the effect is modified by the rotation of a potentiometer, which changes the resistance in a

certain part of the circuit to give the change in effect. The rotation of the potentiometer is produced by movement up and down of the foot-operated pedal, and is what is termed manually operated.

Manual operation is all very well, and essential in some cases, but in a synthesiser it is often convenient that such changes in effect be done automatically, usually at a preset frequency of repetition. Of course, little motors could be devised to drive the shafts of potentiometers, but this has obvious disadvantages.

VOLTAGE VARIATION

Instead, the circuits which require a variable resistance to work them are modified so that they will produce the effect by a variation of voltage on a special voltage control input as with the voltage controlled oscillator mentioned earlier. The actual pattern of voltage applied to control such circuits can be generated internally in the synthesiser by other special circuits, or, where required, manually, by either the keyboard, as in tone generation using the v.c.o.s, or even by a special two-function voltage source potentiometer known as a joy-

stick. This device uses two potentiometers arranged such that the movement of a control stick in one direction produces a variable voltage output from one output terminal, whilst movement in a direction at 90 degrees to this, varies a second voltage output. In this way, two separate voltage controlled circuits may be varied using only one hand.

Another source of manually-operated voltage control is the ribbon controller which is rather like a long potentiometer operated by a finger pressed on to a foil strip which is pressed to make contact on a strip of resistive element underneath it. The output is taken from the foil, and a voltage is connected across the ends of the resistive element, so that the foil picks off whatever voltage is present at its point of contact with the element.

AUTOMATIC SOURCES OF V/C VOLTAGES

A repetitively-changing voltage is relatively simple to produce. After all, this is what we have coming from our v.c.o.s, except that the repetition rate is too fast for most of our purposes. So, a slower oscillator is required, whose frequency can be

MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current: 0-150 mA. Resistance: 0-100,000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges, $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE


£6.95



6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is ± 3 ppm at 25°C or less then ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity: 30 mV up to 30 MHz. Reg. 9V battery. 22-351. REG. PRICE

£79.95

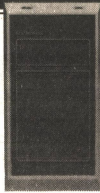

MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts: 0-1-3-10-30-100-300-1000. DC current 0-100 μ A. 0-3-30-300 milliamp. Resistance 0-30-300-3k-301C-1 megohm. 0-100-1k-101C-100k-3 megohms. Reg. 9V battery. 22-209.

REG. PRICE
£29.95



TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.


REG. PRICE **£9.95**



DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE **£19.95**

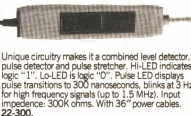

SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE **£2.79**



AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**

REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.

REG. PRICE **£229.95**



DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.


REG. PRICE
£9.95



VARIABLE POWER SUPPLY

Power project boards. IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**

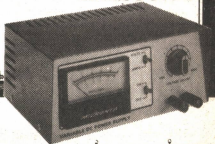

You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80.

TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.

Everyday Electronics, January 1980



TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Across, Barclaycard and Trustcard welcome.

Prices may vary at individual stores.

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all...

... our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.C.s, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.


Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including I.C.s, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

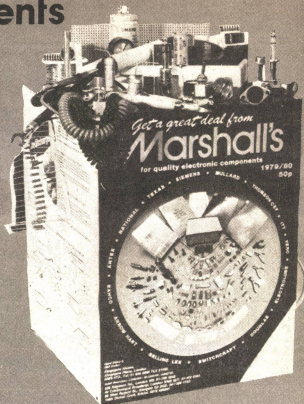
Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

FASTER THAN A SCOPE— SAFER THAN A VOLTMETER

LOGIC MONITOR LM-1

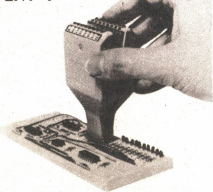

ONLY £28.70

plus 15% VAT, plus post and packing
Total **£34.44** including box and
instruction manual.

CONTINENTAL SPECIALTIES CORPORATION
CSC

Europe, Africa, Mid-East: CSC UK LTD. Dept. 4S.
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: SAFFRON WALDEN 21682.
Telex: 817477.

Instant - simultaneous monitoring of the logic state of all IC nodes

Just clip it over your IC.

LM-1 Instantly and accurately shows both static
and dynamic logic states on a bright 16 LED
display.

LM-1 finds its own power.

LM-1 cuts out guesswork, saves time, and eliminates
the risk of short circuits.

LM-1 is suitable for all dual-in-line logic ICs.

LED on = logic state 1 (high), LED off = logic state
0 (low), and each LED is clearly numbered 1 to 16
in the conventional IC pattern.

CONTINENTAL SPECIALTIES CORPORATION
CSC
CONTINENTAL SPECIALTIES CORPORATION, DEPT. 4S.
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.
Name.....

Address.....

QUANTITY
REQUIRED

FREE catalogue
Tick box ☐

I enclose cheque/PO for

LM1. £34.44

inc. p & p and VAT

£.....

Phone your order with Access, Barclaycard or American Express
Card No. Expiry date.

varied at will to suit the type of music being played, and whose effect or intensity can also be varied.

A suitable frequency range would be from 1Hz (i.e. one cycle per second) to about 7Hz. Such an oscillator is termed a low-frequency oscillator (l.f.o.) to distinguish it from the v.c.o. used to produce the tones. Whilst the l.f.o. is used to vary voltage-controlled circuits, it is not normally itself voltage controlled, but is varied manually.

Similarly, its output is manually variable, by means of a potentiometer, which results in the change of intensity of the effect being controlled by the l.f.o.

VIBRATO

The vibrato effect is popular in organs and synthesisers. In both cases it is created by modifying the pitch of the tone generators slightly by applying a low-amplitude sine wave of about 6Hz to the tone generator(s) so that the pitch is varied about six times a second upwards and downwards around the natural frequency of the note(s) being sounded.

In the synthesiser there is no need to apply the l.f.o. signal to each v.c.o. separately, since each oscillator is controlled by the same source, i.e. the resistor ladder of the keyboard and the subsequent sample/hold circuit. So the l.f.o. signal may be applied to either of these.

If it was applied to the keyboard resistor ladder, however, it would be effective only while the keyboard was in actual use. Once a key was released, i.e. during the sustain period, the sample/hold circuit would be disconnected from the ladder, and, of course, the sample/hold could not memorise the changing voltage from the l.f.o.

The effect of vibrato during the held portion of a note, and not during the decay period of the sustain has its uses, but it is more common for the vibrato to be present throughout the entire length of a note. This can be done by applying the l.f.o. signal to the sample/hold circuit, where the stored voltage on its capacitor could be modified at the frequency of the l.f.o., 6Hz.

The variation that the l.f.o. produces in pitch of the v.c.o. is of the order of a quarter-tone in each direction for normal vibrato supplied on organs, but in the synthesiser we can vary our intensity control so that the l.f.o. sweeps the frequency over many full tones, or even a full octave! Such an effect is in great demand in space-type musical effects.

PRODUCING CHORDS

Before we drift too far away from the v.c.o. it is relevant to cover the use of more than one v.c.o.

As stated already, the monophonic synthesiser allows one key of the keyboard to be played at a time. So far, it is easy to understand how a single pitch can be created, as a single v.c.o. is scaled by the voltage control selection on its input. Imagine a second oscillator connected the same as the first. If this were identical, the two v.c.o.s would both produce the same pitch, e.g. middle C, when the keyboard key of middle C is pressed. But if we equip one oscillator with an independent pitch-modifying control, and turn this control on the second oscillator such that it changes the pitch of the second oscillator to, say, G below middle C, we find we have a chord of two notes.

The G is, in fact, five semitones below C. When the oscillator is so adjusted for G, and the key pressed is, say, D, the second oscillator sounds a note still five semitones below D, i.e. the note of A below middle C. So, although the secondary pitch control of the second v.c.o. has been changed, the change is constant, so that we can depend upon the fact that if we offset the second v.c.o. to produce a certain difference in pitch as measured on the musical scale, then that same difference in pitch will be maintained for whatever key is pressed on the keyboard. Where more than two v.c.o.s are used, the number of notes sounded in a single-key chord can be increased proportionally.

MULTIPLE-STRING EFFECT

It is not always to produce chords, however, that more than one v.c.o. may be used. You will remember that it was mentioned in Part 1 that a piano hammer strikes more than one string when a key is pressed. There is more than one reason for the use of multiple-strings, and increased volume of sound is only one.

In a piano, it is practically impossible to set two strings such that their frequencies are exactly identical, and certainly quite out of the question to rely on them staying in perfect tune with one another for any length of time afterwards. No, an integral part of the quality of a piano note is actually the very slight difference in pitch produced by the strings of any note played. In fact, the strings are sometimes deliberately offset by a noticeable degree to enhance the "honky-tonk" sound of a piano in a bar-room.

Similarly, in synthesisers, we can use more than one v.c.o., each set basically to the same pitch, yet not quite. The effect is a curious phasing quality as the pitches come together to reinforce one another and gradually drift out of phase so that one tends toward cancelling another out. The change may be very slow, taking

a second or two to repeat, or it may be faster, depending on the discrepancy of tuning between the v.c.o.s.

PHASING

The previous paragraphs have introduced an effect which can be produced by two oscillators slightly out of tune to one another; known as phasing. However, there is another way of producing this effect without resorting to two oscillators.

The reader will probably be familiar with the small units available for guitar use, which give a continuously varying phasing sound. The effect is created by selecting a narrow band of frequencies in the audio spectrum and suppressing these frequencies. The band selected is then slowly moved up and down the spectrum, so that it covers and re-covers the whole range of its ability. The result is the familiar effect known as phasing. It operates by suppressing the harmonics of the notes played.

So far, we have dealt with individual notes only, but now we shall look closer at such notes and see exactly what they consist of.

Many books have been written on this sort of study alone, so it must be understood that the look we take at it can only be very brief and basic, sufficient to understand the operation of the phaser and filters, to be described later.

HARMONIC CONTENT

In Fig. 1.2 there are three output waveforms available from the v.c.o. One is a truly wavelike form, smooth and flowing, with no sharp corners or points on it, shaped like the ripples on a pond when a stone is thrown into the water. The waveform is known as a sine wave. It is technically pure, i.e. it consists of one frequency, its natural frequency, or *fundamental*.

If we look at a sine wave of a note of say, middle C, on an oscilloscope, we are looking at the actual shape of the pure signal of middle C frequency. The straight portions and the rounded portions are all part of the pure and fundamental frequency. This means that any shape slightly different from the sine shape is impure, and contains an element of another frequency.

Difficult to understand? Well, consider the following.

If we take the sine wave of middle C, and modify its shape slightly, such that although its peaks are the same distance apart, the "bend" is made sharper instead of being so smooth. The bent portion will then be narrower, and the sharper law of bend will therefore correspond to the law of bend of a frequency whose peaks are closer together, i.e. a higher frequency. So our modified waveform

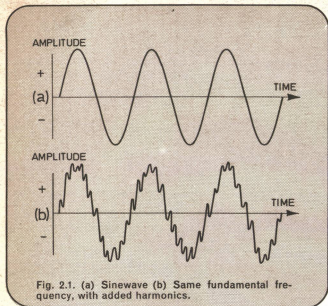


Fig. 2.1. (a) Sinewave (b) Same fundamental frequency, with added harmonics.

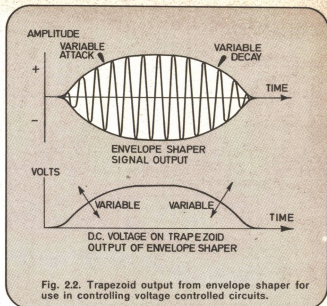


Fig. 2.2. Trapezoid output from envelope shaper for use in controlling voltage controlled circuits.

will still have the same fundamental, i.e. number of peaks per second, but will also contain a characteristic of another higher frequency within it!

This second frequency content is termed a *harmonic*. The more a signal departs from the pure shape of a sine wave, the more harmonics it contains. In fact, the squarewave contains many harmonics, chiefly because its vertical edges are so sharp, but it has a clear-cut fundamental, i.e. repetition rate. Violin music is also rich in harmonics, and a single violin note has a host of harmonics (overtones) contained within it.

WHITE NOISE

A pure sine wave is shown in Fig. 2.1a, to be compared to Fig. 2.1b, a waveform very rich in harmonics, but having the same fundamental frequency as that in Fig. 2.1a.

It is these harmonics which the phaser and later-to-be-described filter operate upon. For this reason, the application of these circuits to pure sine wave signals is largely ineffective, and the more harmonics a signal has the more effective the phaser or filter is found to be.

Sometimes, a deliberate quantity of white noise is added to a signal to enrich it and make use of a filter or phaser more noticeable. White noise sounds like the rush of steam from a locomotive, or similar to waves breaking on a sea shore. It contains a vast number of harmonics, with no regular or constant fundamental to bias the sound. So, it is analogous to white light, and contains all the colours of the spectrum of sound within it. It is easy to see now why a signal containing white noise is so effectively phased.

FILTERS

Filters take three main forms, bandpass, highpass and lowpass. Like the phaser, filters in synthesisers are made voltage controlled for full flexibility.

The bandpass filter is basically opposite in function to the phaser. Instead of suppressing a narrow band of frequencies or harmonics it is designed to suppress all but this narrow band. The effect is as if it were amplifying the narrow band over all other frequencies.

As in the phaser, the narrow band is moveable, up and down the audio spectrum by means of a voltage control frequency. On some filters, the actual band is adjustable by means of a panel control, so that the band may be narrowed or broadened at will.

The effect of a simple bandpass filter is that of the familiar waa-waa circuit which is really a simple form of bandpass filter.

The highpass filter suppresses frequencies below a certain threshold and this threshold is adjustable by voltage control. The lowpass filter works in reverse, by suppressing frequencies above a threshold, which again can be moved up and down the spectrum by voltage control.

The effects differ in practice between the three types of filter, but their basic operation is that of filtering certain harmonic contents in composite waveforms. The actual effect of filters on specific waveforms is not easily shown in diagrammatic form, so no attempt is made here to illustrate filtered and unfiltered waveforms, mainly because filtering is not a present/absent effect, but is more a gradual onset as the threshold level is met, and changes as the voltage

control is varied, and two dimensions would prove inadequate to illustrate the whole overall picture. However, it is hoped the above description will give the reader a good idea as to the principles involved.

VOLTAGE CONTROL FROM ENVELOPE

A useful source of voltage control signal is derived from the envelope shaper circuit. Unlike the signal output, which contains the signal shaped into an envelope of variable attack and variable decay, this second output is simply a d.c. voltage, which varies in direct proportion to the form of the actual envelope at any given time. This output is known as the trapezoid output, and it can be used to control other circuits by changing the voltage on their voltage control inputs, see Fig. 2.2.

If it were applied to a bandpass filter (giving waa-waa sound), through which the final synthesiser signal is passed, the sound produced would be, perhaps, "oowwhaah". The "oow" portion being produced as the attack portion was covered, and the "whaah" part during the decay period. This effect is particularly useful when it is required to give waa-waa effects which are synchronised with the playing of the tunes.

If the waa-waa was produced by driving the filter from a l.f.o., it would be self-repetitive at the frequency of the l.f.o., and the player would have to set this frequency to synchronise with the music beat, whereas with envelope control, the envelope automatically follows the music beat, as it follows the playing of the keys themselves.

To be continued

MAPLIN

ELECTRONIC SUPPLIES



SOLDER

A high quality standard solder by Erco Multicores. Ideal for miniature components (20mg). Vtg ret. about 163 metres. Order as FY70M Price £7.87



MINIATURE TRANSFORMERS

Good quality metal transformers to BS415. 0V type: secondaries 0-9V at 500mA + 0-9V at 500mA. Order as WB90B Price £2.19
0-9V type: secondaries 0-9V at 500mA + 0-9V at 500mA. Order as WB111M Price £2.58
12V type: secondaries 0-12V at 250mA. Order as WB10M Price £2.19
250mA. Order as WB15M Price £2.19
150V type: secondaries 0-150V at 250mA + 0-150V at 250mA. Order as WB15R Price £2.15



Price £13.73

150W amp kit. Order as LW33X Price £14.99

AMP KITS

Complete box of parts with full instructions to make 6 amplifiers with excellent specifications. 6W amp kit. Order as LW36P Price £3.63
50W amp kit. Order as LW50S Price £13.73



LIQUID CRYSTAL DISPLAY

High quality 3 1/2 digit 12.7mm (1/2 inch) high figures. Display has centre color for use in 12 hour clocks and decimal points, plus and minus signs and overflow indicator for use in panel meters. Order as FY90W Price £9.89



SIREN

A small, but penetrating siren operating on 12V DC (1.2A) (15c. 700m). Order as YG25C Price £3.11



McKENZIE POWER SPEAKERS

High quality, high power speakers. 12in. 50W 16Ω. Order as XG79B Price £18.79
12in. 50W 16Ω. Order as XG80B Price £18.79
12in. 80W 8Ω. Order as XG81C Price £26.92
12in. 80W 16Ω. Order as XG82D Price £26.92
15in. 150W 8Ω. Order as XG83E Price £37.80
15in. 150W 16Ω. Order as XG84F Price £37.80



PIEZO HORN TWEETER

Very simply added to any speaker system up to 100W rms. No crossover required. Distortion < 1%. Order as WP98K Price £5.27



20,000 OHM/VOLT MULTIMETER

A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to +20dB. Complete with test leads, battery and instruction booklet. Order as YB35E Price £13.79



MIC STAND

Quality microphone stand extends to 1.5m. Boom arm long adjustable. Stand Order as XG46A Price £11.25



SOLDERING IRONS & KITS

Arteson CX iron. 17W minimum. Order as FY65B Price £4.85
Arteson CX iron. 25W. Order as FR12N Price £4.85
CX iron with stand in presentation pack. Order as FY67B Price £9.85
CX2 iron with stand in presentation pack. Order as FY69A Price £9.85




CLOCK MODULE

Module requires only transformer and two push switches to operate 4-digit, 0.2in red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 357 of our catalogue. Order as XL14Q Price £8.41



QUICK CHARGE RECHARGEABLE CELL

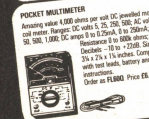1.2V. Size AA/AAA. Fully recharged in 5 hours with 150mA. Capacity: 450mAh. Will last for at least 500 full charge/discharge cycles. Charge in quick charge cells now! Order as LY04R Price £1.49



POCKET MULTIMETER

Amazing value 1,000 ohms per volt DC (200k) moving coil meter. Ranges: DC volts 0.5, 2.5, 25, 500; AC volts 10, 50, 500, 1,000; DC amps 0 to 0.25mA, 0 to 250mA; Resistance 0 to 600 ohms; Decibels -10 to +22dB. Size only 3 1/2 x 2 1/4 x 1 1/8 inches. Complete with test leads, battery and instructions. Order as FL300 Price £5.75



REVERBERATION SYSTEM

The 'concert hall' sound in your living room. Driver module. Order as XG85B Price £8.14
Requiem + and - 15W 200mA power supply (ready built) suitable for Driver Module. Order as YL17T Price £4.73
Spring line with 3 sec. reverse timer. Order as XL84A Price £4.93
Spring line with 7 sec. reverse timer. Order as XG84F Price £11.13



KEYBOARDS

High quality keyboards with hard wearing sloping twisted plastic keys. With keys mounted on nylon bristled steel levers 48note C to C. Order as XG16S Price £23.90
61note C to C. Order as XG16S Price £23.90
With keys protected on a hard wearing moulded falcon. 48note C to C. Order as XG17T Price £19.93




MULTIMETER & TRANSISTOR TESTER

Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt. DC Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA; 10A; AC current 0.5, 5, 50, 500mA; Resistance 5k, 50k, 500k, 5M, 50M ohms; Decibels -10dB to +60dB. Complete with test leads, three leads for transistor tester batteries and instruction booklet. Order as YB70T Price £29.30



TURNTABLES

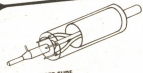Autoreverse complete with stereo ceramic cartridge and circuit to make a complete low cost record player ideal for the young pop fan. Order as XG00A Price £16.30
Single play rim drive turntable with stereo ceramic cartridge. Order as XG23A Price £24.79
Single play belt drive turntable 'S' shaped tone arm. Order as XG25C Price £26.83



LASER TUBE

A helium-neon 0.5mW laser tube. Full details on page 292 or see catalogue. Order as XL11M Price £104.35



ADJUSTABLE LAMP

Adjustable to get a bright light on miniature components. With bracket for clamping or bolting to bench or wall. On/off and dimmer fully adjustable and stable. Finished in white. Order as XY25C Price £78.96

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until February 8th 1980. Export customers deduct 13% and export postage will be charged extra at cost.
Please use order code. All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER.

MAPLIN

ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex S66 8LR. Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff on Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000.

Everyday Electronics, January 1980

SQUARE One

FOR BEGINNERS

THE COMPONENT LIST

EACH constructional article featured in **EVERDAY ELECTRONICS** contains a comprehensive and detailed component list. This lists all the electronic components and various pieces of hardware, sometimes to the last nut and bolt to complete the project. A typical list is seen on page 31.

Each component is specified in detail and this stringent specification can cause headaches for some constructors, especially the newcomers to electronics.

For convenience (yours and ours) the list has several headings under which like components are grouped in numerical order as per the circuit diagram.

RESISTORS

All fixed-value resistors will be found under the heading of **resistors**. In the majority of cases they will be collectively specified as " $\frac{1}{4}$ watt carbon ± 5 or 10 per cent". Any special types will be indicated appropriately after the value. Many newcomers can be excused for thinking that this particular type is vital for successful operation of the circuit. It is not!

A metal film, metal oxide and in some cases wirewound types may be readily substituted for just as good, if not better overall performance. Wirewound types however should be substituted with caution, their relatively high inductance could interfere with the operation of some circuits.

Carbon types are chosen for their availability and low relative cost.

WATTAGE

Now a few words on wattage. As previously said most resistors in these pages are specified as $\frac{1}{4}$ watt types. This does not exclude the use of $\frac{1}{2}$, $\frac{3}{4}$, 1 watt and even higher, except where available "board space" is limited, or on a p.c.b. design where component hole spacings have been decided with a particular component in mind.

The $\frac{1}{4}$ watt resistor is probably chosen by designers for its small, but still easy to handle size, availability

and cheapness. They are more than adequate for low-voltage, low-power battery circuits, as many of our projects are.

If someone took the time and trouble to calculate the required wattages in a circuit, it would be found that in many cases $\frac{1}{10}$, $\frac{1}{20}$ watt and less are all that are necessary. (Divide the square of the maximum possible voltage across the resistor by the resistance value. $W = V^2/R$.)

But for those not sufficiently experienced, the specified rating should be regarded as the minimum required for the circuit, allowing higher wattages to be used if at hand.

TOLERANCE

The " ± 5 or 10 per cent" seen in component lists refers to the resistor tolerance, its maximum deviation from its nominal value. For $\frac{1}{4}$ watt carbon types the constructor these days has little choice. It appears that only 5 per cent types are available. A closer tolerance type can be employed if that is all you can obtain at the time with no adverse effects on operation. Also a 10 per cent can replace a 5 per cent and in a lot of cases an even looser tolerance. Some parts of circuits will still operate in a fashion even if the value is widely different.

CAPACITORS

Both fixed-value and variable capacitors (including preset-types usually called trimmers) are found under the heading **capacitors**.

With variable types, their maximum value is given. For example, a variable capacitor specified as 365pF is continuously variable from 0pF to 365pF. A lower value than specified, e.g. 208pF if at hand could be used to initially test the circuit operation but would give reduced coverage or range. A higher value variable capacitor (e.g. 500pF) can also be used for testing purposes. The range or coverage would be increased, but the intended coverage would be cramped at one end. Similarly with trimmers.

Fixed value capacitors fall into two categories — polarised (electrolytic)

and non-polarised. The latter can be connected in circuit either way round but the former can only be connected one way.

Non-polarised capacitors are specified as value and dielectric. In many cases the latter reads "ceramic or plastic". The constructor then has a free choice from what is available to him since plastic includes polycarbonate, polyester, polystyrene and polypropylene. Polyester is the most common and cheapest.

If a particular dielectric is specified it is wise to obtain this type, as it may have been chosen for its particular properties and optimum performance. For example, a silvered mica capacitor would be chosen for its close tolerance and high stability. A particular dielectric may also be specified if it is to be mounted on a p.c.b. where the lead fixing holes have been accurately dimensioned to suit the specified type.

WORKING VOLTAGE

Working voltages of non-polarised capacitors tend to be high, certainly higher in nearly all cases than 9V which is the most popular supply voltage in our battery operated projects. If the working voltage requires mention, when it is used, say, for example, in a mains filter, it is particularly specified after the value—0.01F 400V a.c. The capacitor can have a higher working voltage but should never, in any circumstances, be less.

This is true also for electrolytic capacitors where the working voltage is always specified. With such capacitors, the physical size for a given value increases with working voltage.

In particular applications, a higher working voltage type than required may be called up. In timing circuits, where capacitors are being charged with minute currents, the leakage through the capacitors may become significant.

The leakage effect is reduced by using a higher working voltage type of the same value.

The working voltage specified for electrolytic capacitors is usually that used in the prototype and may considerably exceed the maximum requirement.


This may be due to the fact that this is the lowest working voltage available to meet the voltage requirement.

SHOP TALK

A reference to our *Shop Talk* feature appears alongside most components lists and is often overlooked by constructors. If you are building a project, it is wise to read this page. Here, among other items, any components thought likely to be difficult to get, special components, substitutions etc. are discussed, and where appropriate sources of supply and cost are given.

The Extraordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett

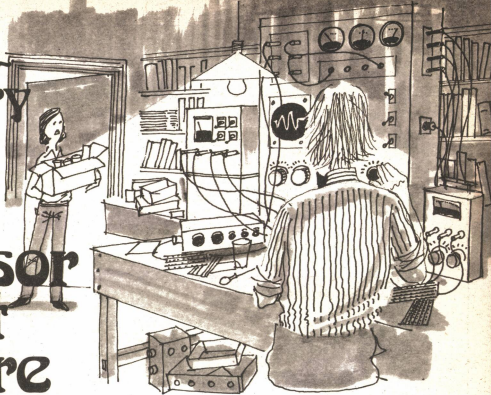

Bob, Tom and Maurice watched as the Prof. fed a few instructions into a computer which promptly printed out a large bundle of fuzz box circuits, which were simultaneously displayed on one of his large computer viewcreens. "I know you will want to take these and study them." He handed the bundle to Bob.

"Thanks, Prof. These look really interesting. I know that fuzz boxes produce their effects by various changes in the musical waveform of the instrument and it will be interesting to study a few of the different circuits and their effects. I am amazed that there are so many!"

"Yes—but although the large number of circuits may seem bewildering, they can mostly be fitted into a number of small groups according to the various principles of operation."

As the Prof. spoke his young friends saw the diagrams rearrange themselves into groups on the large computer viewscreen.

"In this group (Figs. 1-6) the fuzz is produced by operating transistors as non-linear amplifiers, which adds harmonic distortion, and intermodulation effects. An extra bonus of fuzz effects is also produced by overloading the circuit.

"Notice how in this early design fuzz circuit (Fig. 1) using germanium *pnp* transistors, the input transistor TR1 is not forward biased at all and relies upon a combination of transistor leakage together with the guitar signal itself, to bias it into conduc-

tion. This results in a highly-distorted signal at the collector, which is fed through a $0.1\mu\text{F}$ capacitor (sometimes $0.047\mu\text{F}$ or smaller) to the other two transistors where further distortion and amplification occurs. The effect is modified by adjusting VR1 'Fuzz Filter' control.

"Here is a very similar circuit using silicon transistors (Fig. 2). Because these transistors do not 'leak' as much as the older germanium types and the guitar signal itself cannot be relied upon to bias the input transistor to conduction, a bias circuit (R1, R2, R3) is used and this is decoupled by a $10\mu\text{F}$ capacitor to prevent negative feedback from correcting distortion introduced by the transistor.

"I will not comment on every circuit. You can learn a lot for yourself by studying them all and by doing a few experiments. In Fig. 4 the fuzz effect is varied by changing the bias on a transistor, whilst this circuit, Fig. 5, uses a transistor, TR3, which has been deliberately reverse-biased. This technique can be useful in reducing low-level noise and interference which is a problem with many other fuzz box designs.

"The 'overdriver' (Fig. 6) is basically a fuzz circuit which incorporates tone-controls."

DIODES IN FUZZ BOXES

"Here are some more fuzz-box circuits which use diodes to distort the waveform and produce fuzz effects,

but these circuits, unlike earlier ones which used heavy duty power diodes connected to the speaker outlet of the amplifier, use miniature diodes to distort the signal before it reaches the input of the guitar amplifier.

"Either silicon or germanium diodes may be used to produce the fuzz effects, and although the principles are the same, the effects produced are not identical and may sound different. In the first of these diode fuzz circuits (Fig. 7) an integrated-circuit pre-amplifier is used to raise the voltage level of the input signal to a value which will cause the diodes to conduct, alternately clipping away the upper parts of the signal waveform, when the fuzz control is at minimum resistance.


"As the fuzz control is adjusted to higher resistance, the clipping is reduced to give less harsh effects."

"What happens if you use germanium diodes instead of silicon ones in this circuit, Prof?" Bob enquired.


"Due to the lower forward voltage drop of the germanium diodes, they would clip at a lower voltage level, giving a lower output level which would be especially noticeable when the fuzz depth control was set to low resistance. This lower amplitude can easily be compensated by means of extra amplification. So the circuit will work equally effectively with either germanium or silicon diodes!"

To be continued

FUZZ CIRCUITS

 

DISTORTION BOOSTER

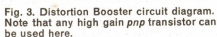



FUZZ CIRCUIT



FUZZ & TREBLE BOOSTER



DIODE FUZZ

 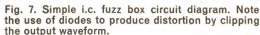

OVERDRIVER CIRCUIT

RADIO WORLD

By Pat Hawker, G3VA

Down to earth?

In announcing the engineering plans for the fourth British TV programme channel, Lady Plowden, chairman of the IBA, pointed out recently that many people think that transmitter networks on the ground are about to be overtaken by direct broadcasting to the home from space, adding: "If we were starting all over again, and there were no u.h.f. networks in the country, there might be reason to do this—always assuming that we were not working to a fixed launch date." This confirms, once again, the view that the question of broadcasting from spacecraft is now increasingly one of need, desire or choice rather than technological feasibility (which indeed is now virtually proven).

In practice, for the Fourth Channel, there could be no question of using direct broadcasting satellites, with the u.h.f. networks now firmly established and with so many viewers already having receivers and aerials and just waiting to touch or push the channel-selection button. For 12GHz transmissions from space they would need at least a new "electronic aerial" comprising a parabolic dish aerial of up to one-metre in diameter together with the circuitry of a receiver or adaptor capable of dealing with 12GHz frequency-modulated signals. Because of the electrical power limitations on spacecraft (the idea of putting a nuclear generator into space is now virtually ruled out) it is necessary for direct-broadcast satellites to use f.m. for vision as well as sound.

I would estimate that it would be some considerable time, if ever, before the extra cost to a viewer for watching programmes coming directly from a space satellite would fall below about £100-£200. This might be well worth paying for say five additional programme channels (the UK allocation) or if you are located in one of the "impossible" places for u.h.f. reception, but otherwise would not appeal to many viewers.

While France, West Germany and Luxembourg all seem anxious to push ahead with direct-broadcast satellites (the first two with an eye on industrial opportunities in those countries where the advantages of satellite systems are more real than in Europe) the major need at present would seem to be for "distribution satellites" akin to those which are already proving useful and profitable for so many American cable "subscription TV" services, for the Canadian CBC and American PBS broadcast networks.

The intention in this case is to provide a low-cost "programme feed" for transmitters spread over large areas or for small, medium and large cable networks. Currently over 1500 TV receiving terminals (mostly working on about 4GHz) are in use or being planned in North America,

and all the major American sound radio networks now distribute their programmes to affiliated transmitters by means of satellite distribution circuits (which allow improved audio up to 15kHz compared with the 5kHz of most long-haul terrestrial links).

Europe at present has only the OTS experimental satellite, apart from the high-cost *Intelsat* global system. But at least this has enabled the IBA to make some interesting use of their transportable up-link terminal, including the first space relays from the Channel Islands and Eire (for the Pope's visit).

Since most European countries operate a telecommunications monopoly, one suspects that there will be less rapid progress towards low-cost satellite distribution circuits in Europe than in the fiercely competitive situation in the USA where RCA, Western Union and now AT & T are all in the business of providing circuits in space.

What a novice needs to know

At a time when there is renewed discussion about the possibility of "novice" amateur licences in the UK, based on an appreciably simpler technical examination and a Morse test of only 5 or 6 words per minute, Graeme Scott, an Australian amateur with the call sign VK3ZR has formulated what appear to be some guidelines on the minimum technical/operating knowledge suitable for a novice examination. He considers that the candidate should be expected to show knowledge of the legal conditions imposed by the amateur licence he is seeking (i.e. how to operate legally); how to tune a transmitter; how to carry on a contact in Morse; how to put together a simple station; show an understanding of common problems (including the causes of television interference, key clicks etc); and have some basic familiarity with the terminology and equipment commonly used in radio.

These guidelines differ from the standard Radio Amateur's Examination in placing much less emphasis on the design of equipment and would limit the mathematics to such basic formulae as Ohm's Law; resistance-capacitance-inductance-frequency-wavelength relationships; value of parallel/series resistors, watts input and so on. The emphasis would be on the information needed in practice to ensure the radiation of satisfactory signals.

Interference

Recently, I was speaking to someone concerned with interference complaints in South Africa (where this is primarily the responsibility of the broadcasters rather than the Post Office). He reported that there had been a very significant increase in complaints of television interference since the start of Citizens Band radio there a couple of years ago.

Tests showed that often the CBrig when correctly tuned and operated gave no problem, even when placed on a bench beside the TV receiver. However, when used over a period of time by people with very little technical knowledge, the same rig tended to drift out of adjustment and to cause severe interference.

The most recent figures from the USA also underline the problem of the inexperienced operator: in the first quarter of 1979, the FCC received 16,401 complaints of alleged radio-frequency interference to TV reception; 13,894 related to CB stations; only 519 to amateur radio stations.

Young Ladies

A very marked change has come over the electronics trade and technical press during the past decade: today one finds that the industry's press conferences are very far from being the all-male affairs they tended to be not so many years ago. A large number of talented young ladies are now writing regularly on electronics.

Does this mean, one wonders, whether the readership is similarly changing? Mr Editor may correct me, but I would hazard the guess that the overwhelming majority of readers are still male.

This certainly applies to the field of amateur radio, where at a guess not more than about 0.25 per cent of British amateurs are "YLs" (young ladies) or "XYLs" (wives)—the former expression "OW" comparable to "OM" (old man) is never used today. Of course, even 0.25 per cent represents several hundred and this is a vast increase since the early days of amateur radio.

I was reminded of this by learning of the death a few months ago of Miss Barbara Dunn, G6YL who for five years (1927-1932) had the distinction of being Britain's first and only YL operator. Altogether she held her amateur licence for more than 50 years and, particularly in the 1930s was an extremely active and able operator.

She taught herself 20 words-per-minute operating by listening on a crystal set to the old FL time signals on 2600 metres from Paris and by listening to ships working on 600 metres and (as they did in the early days) around 2100 metres. She also had to cope with the problem, common to many of the early amateurs, of having no a.c. mains supply and having to depend on a rotary converter running from accumulators charged from 100-volt d.c. mains. Even now, it is well within memory of many of us when quite large areas of London had nothing but d.c. mains.

In 1932 Barbara Dunn was joined by another YL colleague, the late Miss Nell Corry, G2YL who also achieved great distinction in the amateur world by her work on 28MHz—on which band she became the first British amateur to work all continents in October 1935.

In fact, although the number of YLs has always been small in the UK they have contributed much to the hobby. These days I find quite a few American amateurs and also the operators on the Russian club stations turn out to be "YLs".

With my name I also encounter the problem that a number of the people I work on c.w. imagine that I am a "YL" operator and insist on sending me "88" (love and kisses)!

IT'S HAPPENNED AGAIN !

Yes, it's here at last - the all new P-Three Catalogue. Fun for all the family, and the update on all that is new, worthwhile and exciting in the world of Radio and Communications. A big section on frequency synthesis techniques covering broadcast transmitters, to communication quality transmitter systems. More new products than ever - RADIO CONTROL parts, crystal filters, ceramic filters for 455KHz, and the new range of 70MHz and 146MHz VHF/UHF transceivers. The new 8 channel FM receiver with 84dB signal to noise, and adjustable muting threshold. Radio control IC's - and an updated version of the RCMAE 8 channel FM receiver now with an Ambit designed screened front end, with 27MHz ceramic bandpass filter, LCD panel clock/time modules - the nearest and best LCD digital frequency counter yet available. And a new 100kHz HF synthesiser with five ICS - the clock is endless. Get your copy of the catalogue now. Post publication price is 60p (inc PP etc). The previous two sections are also required for a complete picture: Parts 1 & 2 £1 the pair, All 3 £1.50. And don't miss our special guide together with a quiz to see if you can spot the difference between the pictures! Yes, we still haven't learnt how to spell.)

© 1985 by Peter Dainton Publications Ltd.

- * Single IC RF/IF/Detector
 - * Single IC decoder
 - * 27MHz ceramic filter input
 - * FET RF stage with double tuned bandpass filter
 - * Dual ceramic filter IF
 - * Based on RCM&E FM system
 - * Best quality SLM servo connector block
 - * ONLY £16.10 inc VAT (kit)
- (includes new SLM case)

39.999MHz, and 10kHz
are available via diode p

Semiconductors —specializing in radio devices, Plessey SL1600, EUROPE's best selection of AM/FM and communications devices. Power MOSFETs, WORLD'S LOWEST NOISE AUDIO small signal transistors, BAR graph LED drivers for linear and log.
CD4000 series CMOS, TTL/LPSNUTL, standard linears (741, 301, 3080 etc). MPUs, memories. Small signal transistors from AEG BC237/8/9 families etc (1000 off BC239C : 5.2pA).
LEDs: AEG 3mm/5mm round, 2.5x5mm flat, red, green, orange, yellow. The best prices you will find for quality products.
MOSFETs for RF signal processing, including the BF960 UHF device, and 3SK51 for VHF. Varicap diodes for 17:1 capacity ratio tuning

Our DFM4 does, since it uses a vacuum fluorescent display for direct readout of MW/LW/FM. Basically the same as the DFM2, (LCD Version). £24.45 kit (inc VAT) Transformer with all necessary windings for DFM4 - £2.50 inc VAT.



5 tuned circuit, with image/spurii better than -80dB, buffered LO output, MOSFET RF stage, FET IF preamp, tunes with only 1% to 8% -90dBm 3rd order intercept. 1off price £12.00 inc VAT. (100off/ OA)

911225 FM IF strip with all mod cons for the HiFi tuner:
All types use 80-BB S/N Hitachi IC, with muting, AFC, AGC, meter
outputs for signal level and centre zero. IF preamp stage
'A' Dual linear phase ceramic filters, with 100% IF AGC'd IF
pass and 2nd narrow filter with DC filter selection. Dual
FM detector stage £23.95 inc VAT (built)
'B' Dual ceramic filters, single tuned detector stage £14.95 inc VAT
(all 'A' series units are set out with a spectrum analyzer for best THF)

91072 AM RADIO TUNER MODULES - DC TUNED
and DC SWITCHED Available February '80
All include buffered I.C. output, mechanical IF filter (TOKO CEMO

All include three COF tuners, microprocessor, 1000 Hz 10V tuning base, switching by a single pole to earth

A MW/LW (150 to 350kHz LW range) with ferrite rod antenna

B As A but also including SW1 or SW2 (specify.)

SW1 = 1.8 to 4MHz SW2 = 5 to 16MHz

C With both SW ranges

Prices one off INC VAT

A	£14.43	B	£15.90	C	£17.50	(Custom types OAI)
---	--------	---	--------	---	--------	--------------------

FREQUENCY READOUT LSI from OKI, with a one-chip answer to most digital frequency display needs (and various modules).

Crystal and ceramic ladder filters from leading manufacturers, ferrite rods, various ferrite beads and a range of crystals for 'standard' frequencies and both AM and FM radio control at 27MHz. Trimmer capacitors.

METERS - a new range of linear movement types, plus many 'indicator' types for VU, a types of tuning indicators etc.

SOCKETS - a new range that are better quality than Texas low profile, yet better priced.

Modules for AM/FM/STEREO, complete kits for tuners, audio amplifiers from Larsholt.


SWITCHES - complete low cost DIY systems for push button arrays, keyboard switches,

DOUBLE BALANCED MIXERS - MCL SBL1
replacement for MD108 etc. And cheaper.

OUR LATEST MOVING EXPERIENCE : At last, we have moved to the address below. There is car parking for customers approaching via North Service Road (an extension of North Road Avenue, entrance opposite the Brentwood Fire Station.) Pedestrian access from the High Street (alongside 117 High Street). The new building is six times bigger than our Gresham Road offices, and we will be installing a much expanded sales counter in the fullness of time. **NEW TELEPHONE NUMBER (0277) 230909, TELEX NUMBER (as before) 995194 AMBIT G.** See you there !

65

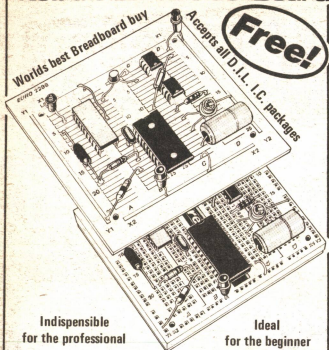First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects). Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2 including 1 or 2 EuroSolderBoards FREE

Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-trimmed tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's or FREE with every EuroBreadBoard)

And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and tracks. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.
Please send me:-

- | | | | |
|--|----------|-----------------------|--------|
| 1 EuroBreadBoard
(plus 1 free EuroSolderBoard) | @ £ 6.20 | ☐ | Please |
| or 2 EuroBreadBoards
(plus 2 free EuroSolderBoards) | @ £11.70 | ☐ | |
| or 3 EuroSolderBoards | @ £ 2.00 | ☐ | Tick |
| or 1 EuroSolderSucker | @ £ 7.25 | ☐ | |

All prices are applicable from Jan. 1st 1980 and include VAT & PP but add 15% for overseas orders.

Name
Company
Address

Tel. No.
Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

TUNE IN!

Build the World Famous CHROMA-CHIME



Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built ABS cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

ONLY £9.95
+ 75p p&p
UK ONLY

* Save pounds on normal retail price by building yourself

TMS 1000N — MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.

New low price only **£4.95** inc. p&p

R/C MODELLERS - LISTEN FOR THE C.B. MENACE GET A 27MHZ MONITOR

- * Audibly confirm your channel's clear.
- * Tunes over whole 27mhz model band.(CB)
- * Receives normal broadcast AM/FM bands as well.
- * Sensitive with telescopic aerial.
- * Totally portable.
- * Runs on standard batteries.

This neat three band Superhet receiver not only provides an invaluable service, checking your channel and TX, but gives normal broadcast reception when you need it as well. Costing less than a decent Servo, you'll find it cheap and reassuring insurance!

ONLY £17.95
INC. V.A.T. AND P.&P.



ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Chromatronics, Riverway, Harlow, Essex.

Please send me: EE/1/80
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.
NAME _____
ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS


Everyday Electronics, January 1980

STARCHASER 4000

THE NEW FOUR CHANNEL LIGHTING CONTROLLER



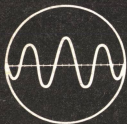- 4 channels 750W each
 - over 1000 different sequence patterns and effects
 - 3 alternative sound triggers
 - A.G.C.
 - simulated strobing
 - zero reference triac firing
 - superb TUAC quality and reliability
- £99.00 inc. VAT.**



TUAC

TUAC Ltd., 121 Charlmont Road, SW17.
Tel: 01-672 3137/9080
PRICE INCLUDES VAT. P+P FREE (at 1.10.79)

TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD, or quote Access/Barclaycard No. and post to TUAC LTD, 121 Charlmont Road, London SW17 9AB. We accept telephone orders from Access/Barclaycard Holders. Phone 01-672 9080.

TUAC MAIN DISTRIBUTORS (Callers Only)

Birmingham, George Matthews, 85/87 Hurst Street, (Tel: 622 1941).
Canterbury, Soco, 9 The Friars, (Tel: 60948).
Crews, Cookies Disco Centre, 126/128 West Street, (Tel: 47391).
Exeter, Electrosure, Fore Street, (Tel: 56687).
London, Garland Bros., Deptford Broadway, (Tel: 01 692 4412).
London, Session Music, 163 Mitcham Road, Tooting, (Tel: 01-672 34113) Mon-Sat 10am to 5.30pm. Closed Wed.
Luton, Luton Disco Centre, 88 Wellington Street, (Tel: 411733).
Manchester, A1 Music, 88 Oxford Street, (Tel: 236 0340).
Middlesbrough, Salcofen, 43 Borough Road, (Tel: 242851).
Southampton, Memhouse, 82 St. Mary Street, (Tel: 28028).

DO YOU EVER WISH YOU HAD A FEW MORE HANDS?

YOU KNOW WHAT ITS LIKE WHEN YOU'RE ABOUT TO START THAT NEW PROJECT — ARMED WITH A NICELY HOT SOLDERING IRON IN ONE HAND, THE SOLDER IN THE OTHER, YOU SUDDENLY FIND YOU'VE NO HANDS LEFT TO HOLD THE CIRCUIT BOARD AND COMPONENT, LET ALONE THE HEAT SINK.

Experience a new freedom with . . .

A twist of the clamping control nut and the Board is held securely. The jaws can then be flipped across so that either side of the board is accessible at will. Flexible arms terminating in crocodile clips hold components and in addition an arm can be provided to hold a magnifying lens to reduce the strain on those valuable eyes of yours.

Provision is made for the fitting of up to four flexible arms if required.

ALL DESIGNED TO ENABLE YOU TO DERIVE GREATER PLEASURE FROM YOUR HOBBY.

ABSONGLEN LIMITED,

The Forge, Staplow Cottage,
Staplow, LEDBURY, Herefordshire HR8 1NP

Please supply Minibench @ £13.95 each
Flexible Arms with Clips @ £ 4.25 each
Flexible Arms with Lens @ £ 5.25 each
Postage and Packing £ 1.00
Cheque/Postal Order enclosed for £
POST COUPON TODAY TO—
Messrs. ABSONGLEN LIMITED, THE FORGE,
STAPLOW COTTAGE, STAPLOW,
LEDBURY, HEREFORDSHIRE HR8 1NP.



THE MINIBENCH*



* Trade Mark

Patent Applied For


Name.....

Address.....

Postal Code.....

Simply ahead..

ILP'S NEW GENERATION OF HIGH

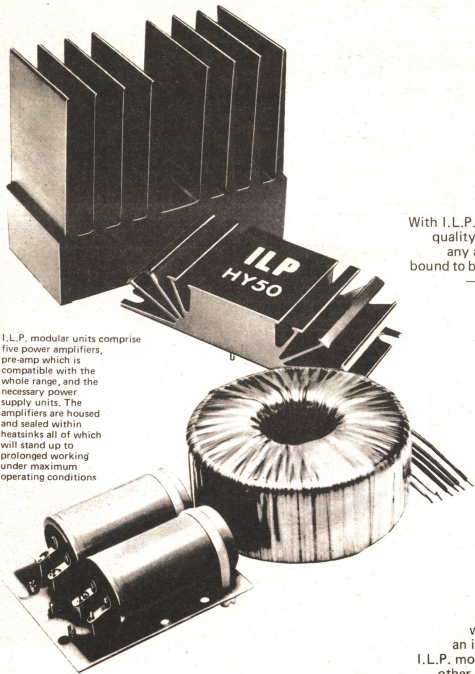

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions

With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance

— and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain

— the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance.

These have stood the test of time far longer than normally expected from

ordinary commercial modules. So we have concentrated on

improvements whereby our products will meet even more stringent demands

such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of

which can prove merciless to an indifferent amplifier system.



I.L.P. modules are for laboratory and other specialised applications too.

**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

and staying there

PERFORMANCE MODULAR UNITS

HY5 PRE-AMPLIFIER

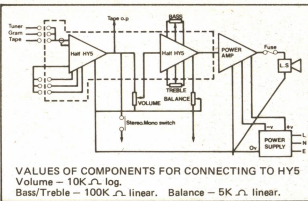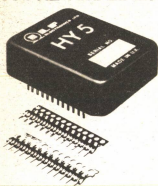


VALUES OF COMPONENTS FOR CONNECTING TO HY5
Volume — 10K Ω log.
Bass/Treble — 100K Ω linear. Balance — 5K Ω linear.

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm, and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz—0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

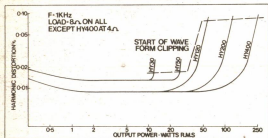

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0 +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0 +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0 +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0 +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0 +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance — all models 4 - 16 Ω
Input sensitivity — all models 500 mV
Input impedance — all models 100K Ω
Frequency response — all models 10Hz - 45Hz - 3dB

THE POWER SUPPLY UNITS

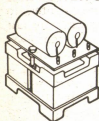

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms — one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30	±15V at 100ma to drive up to five HY5 pre-amps	£4.50 + £0.68 VAT
PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU 180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT

**NO QUIBBLE
5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
INTEGRAL
HEATSINKS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE
—see below**

★ ALL U.K. ORDERS DESPATCHED POST PAID HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope — we pay postage on all letters sent to us by readers of this journal.



ELECTRONICS LTD.

FREEPOST 3 Graham Bell House, Roper Close,
Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 Telex 965780

Please supply Total purchase price £

I enclose Cheque ☐ Postal Orders ☐ International Money Order ☐

Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature

ELECTROVALUE CATALOGUE 10

Ready early December

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

FREE

(You don't even have to pay postage)

IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

● We give discounts

on C.W.O. orders, except for a few items market Net or N in our price lists.

5% on orders, list value £10 or more

10% on orders list value £25 or more.

Not applicable on Access or Barclaycard purchase orders.

● We pay postage

In U.K. on orders list value £5 or over. If under, add 30p handling charge.

● We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

● We guarantee

all products brand new, clean and maker's spec. No seconds, no surplus.

● Appointed distributors for SIEMENS, VERO, ISKRA, NASCOM and many others.

OUR NEW CATALOGUE No 10

Over 120 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

ELECTROVALUE LTD

HEAD OFFICE (Mail Orders)

28(A) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London prefix 87. STD 0784) Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)

680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432 4945.

GREENWELD

443D MILLBROOK ROAD, SOUTHAMPTON SO1 0HX
All prices include VAT—just add 30p post. Tel (0703) 772501



COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors, diodes and I.C.'s. All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts! All parts contained in clearly marked bags in a plastic storage cabinet 232 x 121 x 165mm with 9 drawers into which all parts can be neatly located. If bought individually parts plus case would cost over £47 but we are offering this for **ONLY £21.95 + £1 p.p.** Simply send a cheque or P/O for **£22.95** for immediate despatch.

CONTENTS:

- 200 ½ watt resistors
- 200 Wire wound resistors
- 70 Ceramic Capacitors
- 70 Polyester Capacitors
- 56 Electrolytic Capacitors
- 12 Transistors
- 12 I.C.'s
- 30 L.E.D.'s
- 35 Diodes and rectifiers

Also together £14 components.

Price includes current catalogue and Greenweld pen for ordering supplies. Plus **FREE** surprise gift.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etchant pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.95**

KITS OF BITS FOR EE PROJECTS

We supply parts for nearly all EE projects—for a detailed components list of this month's, and previous articles, please send SAE.



VEROBLOC BREADBOARD

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC. Blocks and be joined together. Bus strips on X & Y axis—total 300 connection points for just **£3.75**.

VU METERS

V002 Twin type, 2 meters 40 x 40mm and driver board, supplied with circuit and connection data. **£2.95**

V003 New type, just in. Twin type moulded in one piece, 80 x 40mm (no driver board but suitable circuit supplied). **£2.95**

THE NEW 1980 GREENWELD CATALOGUE

FEATURES INCLUDE:

- 60p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- PRICE 40p + 20p POST

WIRE & FLEX

Solid core—ideal for breadboards etc. 30 x 3m lengths many assorted colours, total 100m for **£1.30**.
Flex pads—5 x 5m lengths of multi-strand thin flex, ideal for wiring up circuits. Only **35p**

3W Amp Module

Ready built and tested, this handy amplifier will prove very useful around the workshop. Just requires 17V ac source (and 8R spkr) as bridge rect and smoothing cap are mounted on the PCB. The 4 transistor circuit provides enough sensitivity for most applications. Supplied complete with circuit diagram and wiring details.

Only **£1.75**. Suitable transformer **£2.20**.



VEROCASE SLEAVE

3 popular models of Verocase at drastically reduced prices—these were part of their standard range (75-141 etc.) but are in GREEN and have been discontinued by Vero. We have purchased their entire stock and offer them as below:

Type No	Size	Price
21050	205 x 140 x 75mm	£2.70
21052	145 x 85 x 60mm	£1.70
21053	125 x 65 x 40mm	£1.40

1A 400V RECTIFIERS

Plastic, like 1N4004, type 358F these diodes have preformed leads for horizontal mntg (15mm VC). Super saver price—100 for **£2.30**; 500/£10 1000/£10

BUZZERS & MOTORS & RELAYS

Z401 Powerful 6V DC Buzzer all metal construction 50mm dia x 20mm 70p.
Z402 Miniature type Buzzer 3-5V, only 22 x 15 x 16mm. Very neat 65p.


Z400 Miniature 6V DC motor, high quality type 30mm dia x 25mm high, with 12mm spindle. Only **£1**.

Z403 12V high torque motor 30mm dia x 40mm high, with 10mm spindle. **65p**.

W082 Heavy duty 12V relay, ideal for car use—single 1.5A max contact. Coil 20V. W080 DIL reed relay—SPCO 2-4V-10V 800R coil. Only **£2.25**.

TEACH IN 80

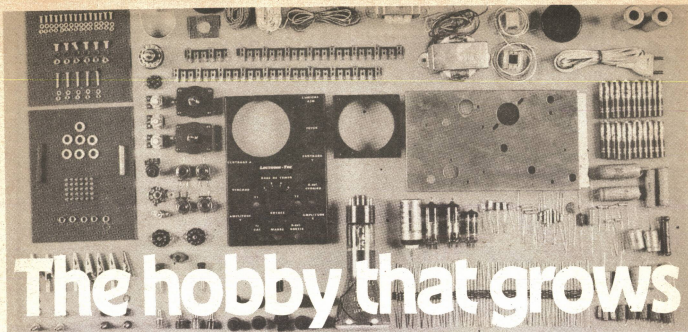We are again supplying all parts required for this major series which started in October. The price for all the Tutor Pack parts is **£19.50**. Also supplied without breadboard for **£13.50**. The price for the additional components required for Parts 1-6 is **£2.00**. All prices include VAT and Postage. Reprints of Oct & Nov parts **30p** ea.



The hobby that grows

What you see above is a kit of parts that builds into a fully working oscilloscope.

No toy, this vital piece of functional equipment can be found in any professional electronics workshop. It is a valuable instrument of true professional quality.

By building the oscilloscope you will be taking the first steps to a rewarding hobby that knows no bounds.

Each constructional stage is a complete lesson

in the basics of electronics practice and carefully designed to be understood by those with no previous knowledge. Once built, this instrument can be used to complete a course of practical study and experimentation that will reveal the secrets of printed circuitry, testing and servicing of T.V. and radio and the vast majority of electronic equipment.

Invaluable knowledge that pays big dividends. Send today for the free colour brochure and start growing a new hobby.

and grows.

1. Build an oscilloscope.


As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

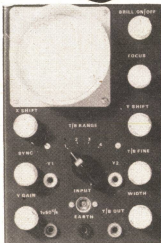3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.



4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



EEH/1/80

NAME

ADDRESS

Block Caps Please

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO and
ELECTRONICS SCHOOL**

P.O. Box 156, Jersey,
Channel Islands.

24 TUNE DOOR CHIMES

DOOR TUNES £17.13 + VAT.

Widdig's Volumester announces a featured that doesn't get boring. Ding-Dong or Buzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but it is also very functional and beautifully designed to enhance your home. There is something for Christmas, something for your carter, visitors or your relative from the coast, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.

T.V. GAMES

PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will long pass with ingenuity technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Street Fighter. Further cartridges are to be released later this year, including Task Battle, Hunt the Salt and Target. The console comes complete with two removable plastic player controls to enable you to move in all four directions (up/down/left/right) and back into these plastic controls are built in and four buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on screen and built-in. Unlike scores are transmitted through the TV's speaker, ensuring the actual game being played. Manufactured by Widdig's Volumester and guaranteed for one year.



EXTRA CARTRIDGES:

ROAD RACE - £8.87 + VAT.
Grand Prix motor racing with gear changes, crash zones
SUPER WIPEDOUT - £8.17 + VAT.
10 different games of blasting obstacles off the screen
STUNT RIDER - £12.16 + VAT.
Motorcycle speed trials, jumping obstacles, leaving various
trails of up to 24 lines etc.
NON-PROGRAMMABLE T.V. GAMES

6 Game - COLOURSCORE II - £13.58 + VAT.
16 Game COLOUR SPORTSWORLD £22.50 + VAT.

CHESS COMPUTERS

STAR CHESS - £55.09 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

Using your own TV to display the board and pieces, Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess, it adds your own personal interest and interest to the game. For those who have never played Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange itself for itself to opponents. The unit comes complete with a free 18V motor adapter, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 - £85.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The 7th, compact, portable console can be set to play at seven different levels of ability from beginner to expert, including 'Mine in two' and 'Chess by mail'. The computer will only make responses which obey international chess rules. Carries, on preset, and pressing a piece on all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.

Pieces include unit with wood grained housing, and Stewart design chess pieces. Computer plays black or white and square itself and computer complete with a motor adapter and 12 months guarantee.

OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

CHESS CHAMPION - 6 LEVELS £47.39 + VAT.
CHESS CHALLENGER - 10 LEVELS £138.70 + VAT.
BORIS - MULTI-LEVEL TALKING DISPLAY £163.04 + VAT.

DRAUGHTS COMPUTERS

CHECKER 2 LEVELS £43.00 + VAT. CHALLENGER 4 LEVELS £78.00 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision making microprocessor as its brain. Its high level of thinking enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machines does not permit illegal moves and can solve set problems. Computer games complete with instructions, motor adapter and twelve months guarantee.

PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



FOR FREE BROCHURES - SEND S.A.E.

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling - demonstrations daily - open from Sun 5.30pm-Sun 10pm (last 10pm).

To order by telephone please quote your name, address and Access/Barclay card number.

Postage and Packing FREE.

AJD DIRECT SUPPLIES LIMITED, Dept. EE1 102 Bellegrave Road, Welling, Kent DA16 3DD. Tel: 01-303 9145 (Day) 01-850 8862 (Evenings)

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented clip-on, easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no need for the contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the arcing from the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell period which allows the coil a longer period of time to store its energy before discharging into the plugs. The unit includes built-in static immunity, systems function light, and security changeover switch. Will work on all new computers.



Fits all 12V negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.

Roger Clark the world famous rally driver says 'Sparkrite electronic ignition systems are the best you can buy'.



Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Assoc.
82 Bath Street, Walsall WS1 3DE

**Electronics Design Associates, Dept. EE180
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791**

Name _____

Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X5KIT £16.95

ACCESS OR BARCLAY CARD No.

£

Cheque No.

Send SAE if brochure only required.

There's never been anything like it!

The Greatest advance in inter-connection in 50 Years

Solderless Circuit Boards using CONDUCTIVE ELASTOMER MULTICONTACTS for equivalents of double sided, plated thro' hole and multilayer PCB's.

- NO SOLDERING
- BUILD YOUR CIRCUITS JUST ONCE IN MINUTES
- ACCEPTS ALL IC's UP TO 60 PINS
- WIRES AND COMPONENTS CAN BE CHANGED WITHOUT DISTURBING OTHERS
- 12 DIL-14 IC CAPACITY ON SMALL WONDERBOARD ILLUSTRATED

WONDERBOARD


Send cheque or postal order to:—

CHARCROFT ELECTRONICS LTD.

CHARCROFT HOUSE, STURMER, HAVERHILL, SUFFOLK. Tel: 5700 Telex: 817574




Wiring side

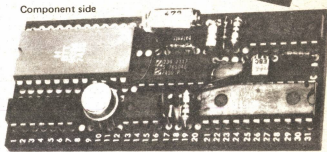

Component side

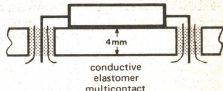£3.00 12 IC
12 IC 48 IC
Small Wonder Big Wonder
(inc. VAT and p & p)



conductive elastomer multicontact

TRANSFORMERS Continuous Ratings + VAT 15%

30 VOLT RANGE
Pri 220/240 sec 0-15-30-34-30V
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V and 15V-0-15V.

Ref	Amperes	Price	P & P
112	0.5	2.90	0.90
79	1.0	3.83	1.10
3	2.0	6.35	1.10
30	3.0	8.82	1.31
21	4.0	8.79	1.31
31	5.0	10.45	1.52
117	6.0	12.29	1.67
88	8.0	14.45	1.89
99	10.0	18.98	1.89
90	12.0	21.09	2.24
21	15.0	24.15	2.39
92	2.0	32.40	O.A.

50 VOLT RANGE
Pri 220/240V Sec 0-30-25-35-40-50V
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 30, 40 or 20V-0-20V and 25V-0-25V.

Ref	Amperes	Price	P & P
102	0.5	3.15	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.57
106	4.0	12.82	1.75
107	6.0	16.27	1.99
118	8.0	22.29	2.39
119	10.0	27.46	O.A.
109	12.0	32.89	O.A.

MAINS ISOLATORS (Screened)
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
142	20	4.54	0.91
149	60	7.27	1.10
150	100	8.38	1.31
151	200	11.38	1.31
152	250	14.61	1.73
153	350	18.47	2.12
154	500	25.52	2.47
155	750	32.85	O.A.
156	1000	40.82	O.A.
157	1500	56.82	O.A.
158	2000	67.89	O.A.
159	3000	95.33	O.A.

*Pri 0-250-240V Sec 115 or 240V.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

Ref	VA	Price	P & P
20	6.55	1.94	56W
75	4.58	1.31	64W
120	11.86	1.31	4W
200	12.62	1.67	60W
250	12.53	1.67	60W
500	29.13	1.89	67W
750	29.67	2.55	67W
1500	42.82	O.A.	93W
2000	54.97	O.A.	93W

SCREENED MINIATURES

Ref	mA	Volts	Price	P & P
238	200	3-25	2.53	0.63
212	1A, 1A	0-4, 0-6	2.14	0.90
213	100	0-0-9	2.35	0.44
238	320	0-4, 0-9	2.15	0.44
236	220	0-15, 0-15	2.19	0.44
239	50MA	12-15	2.83	0.37
214	300, 300	0-20, 0-20	3.08	0.90
221	700 (DC)	20-12-0-12-20	3.75	0.90
208	1A, 1A	0-15-20, 0-15-20	5.89	1.10
203	550, 550	0-15-27, 0-15-27	4.39	1.10
204	1A, 1A	0-15-27, 0-15-27	6.44	1.10

12 OR 24V OR 12-0-12V

Ref	12V	24V	Price	P & P
111	0.5	0.25	2.42	0.52
213	1.0	0.5	2.90	0.90
71	2	1	3.88	0.90
18	4	2	4.48	1.10
85	0.5	2.5	6.16	1.10
70	6	3	6.99	1.10
108	8	4	8.16	1.31
72	10	5	8.93	1.31
116	12	6	9.89	1.52
117	16	8	11.79	1.37
115	20	10	15.38	2.38
187	30	15	19.72	2.38
226	60	30	40.41	O.A.

TEST METERS P & P £1.15 15% VAT

AVO 5 MK5

AVO 71

AVO 73

AVO MMS minor

Wec Megger

AUTO TRANSFORMERS

VA Step up Step down E. P & P

113 15 0-115-210-240V 2.73 0.81

75 15 0-115-210-240V 4.41 1.10

4 150 0-115-200-220-240V 5.89 1.10

67 500 12.69 1.91

84 1000 29.64 2.39

83 1500 25.61 O.A.

95 2000 38.30 O.A.

73 3000 65.13 O.A.

ELECTRONIC CONSTRUCTION KIT

Home electronic starter. Start simply and progress to a TRF radio or electronic organ. No assembly in presentation box. Instructions. £5.29. P & P 95p. VAT 15%.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/7/8

Nearest Tube Stations: Aldgate & Liverpool St.

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City and Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept Q768 Intertex House, London

SW9 4JJ or telephone 622 9911

Subject of Interest

Name

Address

Tel: Asc:

M.E.C.A.
14 HOPETOUN STR.,
BATHGATE
WEST LOTHIAN
Tel: Glasgow 631371

FREE 4 RECTIFIER DIODES

in 4003 or 4005 ON ALL ORDERS
dated before 1.1.1980

TERMS: C.W.O. No Min. 15p P & P.
ACCESS & BARCLAYCARD ACCEPTED
Min. £5 Post & Packing 25p.
GOVERNMENT, SCHOOLS, COLLEGES
ORDERS ACCEPTED
Send or Phone for Catalogue.

CMOS	4049	26p	N LSN	4049	26p	N LSN	AUDIO	100+ Less 20%
4000	8p	4050	26p	7411	15p	18p	7490	25p
4001	11p	4052	45p	7412	15p	40p	7491	40p
4002	12p	4053	45p	7413	15p	30p	7492	25p
4004	25p	4056	30p	7414	45p	65p	7493	25p
4006	70p	4069	70p	7415	15p	40p	7494	45p
4007	12p	4071	15p	7417	24p	24p	7495	45p
4008	45p	4081	16p	7420	10p	16p	7496	45p
4009	25p	4082	7p	7426	15p	15p	74100	75p
4010	26p	4507	48p	7427	15p	15p	74107	15p
4011	15p	4511	55p	7430	12p	16p	74121	32p
4012	12p	4512	65p	7432	12p	18p	74122	35p
4013	26p	4515	195p	7437	12p	20p	74123	35p
4014	55p	4519	42p	7438	13p	25p	74125	30p
4015	50p	4522	70p	7440	12p	22p	74126	25p
4016	21p	4526	70p	7441	52p	44p	74132	44p
4017	45p	4528	70p	7442	26p	45p	74141	45p
4018	45p	4529	70p	7443	42p	42p	74150	53p
4019	25p	MC14409	999p	7444	42p	42p	74151	39p
4020	50p	MC14419	295p	7445	42p	42p	74153	45p
4021	50p	MC1451	99p	7446	42p	42p	74154	120p
4022	45p	All prices		7447	42p	68p	74156	39p
4023	12p	Include V.A.T.		7448	42p	48p	74157	39p
4024	45p	BUFFERED		7450	13p	20p	74161	49p
4025	12p	types on request		7451	13p	20p	74163	49p
4026	25p	according to our		7452	13p	13p	74164	57p
4027	25p	stock position.		7454	13p	16p	74165	59p
4028	45p			7460	13p	16p	74166	60p
4029	60p			7470	26p	26p	74175	55p
4030	26p	TTL—		7472	26p	26p	74176	49p
4033	80p	N LSN		7473	16p	23p	74181	125p
4034	150p	7400	7p	7474	19p	25p	74182	45p
4035	50p	7402	9p	7475	26p	40p	74190	69p
4037	90p	7403	9p	7476	25p	30p	74191	69p
4040	50p	7404	7p	7480	35p	35p	74192	69p
4041	45p	7405	13p	7482	45p	55p	74193	65p
4042	40p	7406	15p	7483	45p	58p	74194	55p
4043	30p	7407	24p	7485	60p	60p	74195	49p
4044	50p	7408	9p	7486	60p	60p	74196	49p
4046	75p	7409	9p	7488	29p	30p	74197	49p
4048	50p	7410	9p	7489	29p	30p		

CAPACITORS—

ELECTROLYTIC, RADIAL
LEAD

Values	16V	40V	63V
1uF	3p	3p	3p
2.2uF	3p	3p	3p
3.3uF	3p	3p	3p
4.7uF	3p	3p	3p
10uF	3p	3p	3p
22uF	3p	4p	5p
33uF	3p	4p	5p
47uF	4p	5p	6p
68uF	5p	7p	7p
100uF	4.5p	8p	9p
150uF	7p	9p	11p
220uF	8p	10p	14p
330uF	7.5p	14p	16p
470uF	8p	16p	20p
680uF	11p	20p	25p
1000uF	12p	21p	34p
2200uF	22p	42p	—

TRANSISTORS—

Standard A	C
TIP 23	27p
TIP 30	35p
TIP 31	32p
TIP 32	38p
TIP 41	50p
TIP 42	45p
2N3055 (TO3)	33p
2N3054	33p
BC108	7.5p
BC107	7.5p

MAIL ORDER DEPT.

CRESCENT RADIO LTD.

I. ST. MICHAELS TERRACE, WOOD GREEN, LONDON, N22. 4SJ.
PHONE 01-888 3306



"FLIP"

Push button heads or tails.
Complete kit and full instructions supplied.
A pocket game.
Easy to build and great to play.
Kit price—£5.25 + 15% VAT. Post free.

4 OHM DROU MOUNTING CAR LOUSPEAKERS



High performance, drou mounting.
5 1/2 inch units with smart front grill.
10 oz magnet, 12 watts, 4 ohms.
In attractive see-through carton.
£12.40 + 15% VAT, per pair.

MORSE KEY CR.38

All metal, cast base, professional high speed key. Fine adjustment. Mounted on bakelite base.
Dimensions: (Base) 120 x 75mm
£3.90 + 15% VAT

A 'CRESCENT' 'SUPERBU' LOUSPEAKER

Goodmans 5" 8 ohm long throw H/D loudspeaker.
Mounting plate is integral with L/S chassis and has fixing holes with centres spaced 5 1/2" (diagonally).
ONLY £6.00 + 15% VAT



"P&P" ORDERS UP TO £5. Add 30p
ORDERS £5-£10. Add 50p
All orders over £10 post free!
Please add VAT as shown.
S.A.E. with all enquiries please



Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N13.
ALSO. 13 SOUTH MALL, EDMONTON GREEN, EDMONTON.

LOUSPEAKERS 90p

(57mm) 8 + 15% VAT
(please state impedance req'd)

PSI STABILISED POWER SUPPLY

240v AC input. Outputs: 3, 6, 7.5 and 9 volts DC at maximum 400 ma. Three switches: On-Off, Polarity Reversing and Voltage Change. Regulated to supply exact marked voltages from no load up to maximum current. Dimensions: 127 x 76 x 57mm. £4.50 + 15% VAT.

PS2 12 VOLT HEAVY DUTY POWER SUPPLY

12 volt 1.5 amp suitable for using auto cassettes from domestic mains. Approx. size: 105 x 100 x 60mm. £10 Inc. VAT.

CR4110 DESOLDERING PUMP



ONLY £6 + 15% VAT

High suction pump with automatic ejection. Knurled, anti corrosive casing. Teflon nozzle.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000W lighting per channel, max. 12V. This 3 channel unit (to 100p) is housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions supplied. S.A.E. for spec. sheet. ONLY £20.00 + 15% VAT

CR LVI 12V DRILL

£12.00 + 15% VAT
BRITISH MADE "Versadrill", 12 volts DC. Compact battery operated power tool, sufficiently powerful to perform all the operations associated with 240v drills. Dimensions:— 150 x 50mm (dia.)

EE RADIO CONTROL SYSTEM

In conjunction with the present set of articles in *Everyday Electronics* the items that we manufacture comprise transmitter cases, control sticks, receiver boxes, battery boxes, auxiliary levers, plug and sockets, aeriels, etc.

We also have extensive tool room facilities manufacturing moulding dies and press tools. We can supply precision turned parts on Swiss sliding head automatics. We can cut spur gears up to 2in. diameter and bevel gears, and our moulding capacity is up to 6oz. in virtually any material.

We do not handle electronics or electronic components.

S.L.M. (Model) ENGINEERS LTD.

Chiltern Road, Prestbury.

Tel: Cheltenham 25488

SMALL ADS

The prepaid rate for classified advertisements is 10 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £5.00 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

For Sale

NEW BACK ISSUES OF "EVERYDAY ELECTRONICS" Available 75p each Post Free, open PO/Cheque returned if not in stock. **BELL'S TELEVISION SERVICES** 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

Receivers and Components

COMPONENTS AT SILLY PRICES. 1,000 mixed resistors £3.60. SAE lists. W.V.E.2, Craigo Farm, Tintern, Gwent.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HANDING & CO.** 103 South Brink, Wisbech, Cambs, 0645 4188. Immediate settlement.

NO LICENSE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-70 plus 25p P. & P.

"Brain-Freeze" em with a MINI-STROBE Electronics Kit, pocket-sized "lightning flashes" vari-speed, for discos and parties. A mere £4-50 plus 25p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint secret messages with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P.

LOTS MORE! Send 25p for lists. Prices include VAT.

BOFFIN FACTS

4 CUNIFFE ROAD, STONELEIGH
EWELL, SURREY. (E.E.)

DISCOVER ELECTRONICS. Build forty easy projects including: Metal Detector, Breathalyzer, Radios, Stethoscope, Lie Detector, Touch time-switches, Burglar alarms etc. Circuits, plans all for £1.50 including FREE circuit board. Mail only. **RIDLEY PHOTO/ELECTRONICS**, Box 62, 111 Rockpark Road, Uckfield, Sussex.

P.C.B.s Paxolin 101" x 41" 4-61-30, 12" x 91" 85p-110" x 111" £1.40, D.S. 10" x 81" 85p. Fibreglass 12" x 70" £1.40, 14" x 91" 85p, D.S. 10" x 77" £1.50, Panel with 40 assorted 74 series I.C.s £1.60, 20 ended Neos £1.20, Small 20 ended Neos Audio Amps 3-£1.20, 300 Small Components, Trans, Diodes £1.60, 74s Assorted Components £3.75, List 15p refundable. Post 50p. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

100 ASSORTED COMPONENTS 115p, 100 resistors 75p, 10 mains neons 50p, 20 micro-switches 150p, 50 red switches 200p. Add 25p p&p. **DURRANTS**, 9 St. Mary's Street, Shrewsbury, Salop.

Electronic Timers	40p	Small Read Switch	10p
Flashing Red L.E.D.s	85p	Large Read Switch	15p
TL309 Red L.E.D.s	35p	Changeover Type	25p
Large Red L.E.D.s	15p	Magnetic Reed	15p
Oblong Red/Green	60p	Reed Relay 3-V DC	40p
Large Copper wire	15p	Key Switch	41 50p
30, 34, 38, 28, 40 swg 11 ft		Type Recorder Motor	
BC107/119 10p CRP12	85p	Reg 9v DC 1" x 2" 85p	
30 Speaker 20" 18p		Pots 10k, 1M Lin	15p
80G Speaker 21" 85p		R.F. Chokes	15p
Small Speakers	15p	20 Axial Resistors	15p
Mercury switches	75p	30 Unassorted OA91	25p
Stainless Steel Rod	15p	Resistor Mats	15p
machined 1" x 6" 18p		Resistor Mats	15p
4,700uF 10v elect	40p	Resistors 1W 5% 2p ea	

GRIMSBY ELECTRONICS

17 BELLEVUE ROAD, GRIMSBY, S. HUMBERSIDE
CALLERS TO OUR LAMBERT RD. COMPONENTS SHOP

NOTICE TO WHIST

Whist prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

10 MIXED COLOURS, sizes, LEDs £1-15p.
Lists 15p. Sole Electronics, EE, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

QUALITY ELECTRONIC COMPONENTS AT LOW PRICES

Write or telephone for free pamphlet to:

HARRISON BROS. DEPT E.E.

P.O. Box 55, Westcliff-on-Sea, Essex, SS0 7LQ.
Tel. Southend-on-Sea 23235

Miscellaneous

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Photolab Light Sensitive Lacquer—now greatly improved and very much faster. Aerosol cans with full instructions. £2-25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1-70 sq. ft. Post/packing 60p. **WHITE HOUSE ELECTRONICS**, P.O. Box 19, Castle Drive, Penzance, Cornwall.

E.E. Radio Control System PCB's

Professional quality glassfibre, Fry's solder tinted and drilled.

Dec. 79 Transmitter **£1 47**
Receiver—TBA

Postage: Please add 25p postage and packing to complete order.

PROTO DESIGN

14 Downham Road, Ramden Heath
Billerica, Essex CM11 1PU
Telephone 0268-710722

NORTHERN IRELAND. Build your own Computer. Nascom-1 Microcomputer kits. From P & O Computers (NI), 81 Dublin Rd, Belfast BT2 7HF. Tel: 22010 evenings. Donaghmore 312. Belfast G21066.

LEARN ELECTRONICS THE EASY WAY. Build: amplifiers, oscillators, detectors, testers, flashers, metronomes, etc, more than 25 projects, with our multi-kits, complete instruction manual supplied. Send £15 to: Major Oak Services, 33 Lillian Avenue, London W3.

NEW

QUALITY KITS FROM DENMARK

Easy-to-build, sure-fire kits with full English instructions
Latest IC circuit designs

JK01 AF Amp	£6.75	JK06 27MHz Xtal TX	£9.85
JK02 Mix Amp	£6.75	JK07 Tone Decoder	£9.85
JK03 Sig. Gen	£9.85	JK08 Triac Control	£9.95
JK04 FM Tuner	£9.95	JK09 Birdie Bleeper	£9.95
JK05 27MHz Xtal RX	£10.50	HF61 Beginners kit	£6.50

Prices include VAT

Stocks limited due to world-wide demand

ORDER NOW

Full money back guarantee

TECHNOCENTRE LTD

SAE for FREE Kit Guide

Mail order

54 Adcott Road
Middlesbrough TS5 7ES

NI-CAD BATT. packs. Contains 9-AA cells, 5 sub c cells (1-2AH). Mains charger £8-50 inc. p.p. E.D.S., 66 Brook Lane, Warshaw, Southampton.

C.C. CONSULTANTS. Printed circuit boards for the popular Everyday Electronics Lab Centre are now in stock still at the special price of £5-50+35p P&P. Enclose remittance with order to C.C. Consultants, Dept EE, 3 Gainsborough Drive, Worle, Weston-super-Mare, Avon BS22 9PP.

THE SCIENTIFIC WIRE COMPANY

PO Box 36, London E.4.
Reg. Office, 52 Coningsby Gardens.

ENAMELLED COPPER WIRE			
SWG	110	80	202
10-19	2.85	1.45	1.75
20-25	2.85	1.45	80
26-34	3.05	1.75	1.00
35-40	3.45	2.15	1.15
41-43	4.55	2.55	1.35
44-48	5.55	3.05	2.15
49	8.00	3.00	3.00
48	15.00	9.00	6.00

SILVER PLATED COPPER WIRE

14, 16, 18	4.50	2.25	1.44
20 & 22	5.00	2.85	1.74
24 & 26	5.70	3.11	2.22
28 & 30	6.37	3.86	2.35

Prices include P & P and VAT.
SAE brings full list of copper & resistance wires.
Dealer enquiries invited.

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Phone 31803. No lists, enquiries S.A.E.

AERIAL BOOSTERS

Improves weak VHF radio & television reception.

B45-UHF TV, B11-VHF RADIO, B11 A-2 metres.

For next to the set fitting.

PRICE £6. S.A.E. FOR LEAFLETS.

ELECTRONIC MAILORDER LTD.

Ramsbottom, Bury, Lancs, BLO 9AG.

Educational

COURSES—RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination and obtain your G8 Licence, with an RRC home study course. For details of this, and other courses (GCE, professional examinations etc.) write or phone: **THE RAPID RESULTS COLLEGE**, Dept JRI, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service).

Record Accessories

STYL. CARTRIDGES FOR MUSIC CENTRES &c. FREE List No. 29. For S.A.E. includes Leads, Mikes, Phones, etc. **FELSTAD ELECTRONICS (EE)**, LONGLEY LANE, GATLEY, CHEADLE, CHES SK4 4EE.

Service Sheets

SERVICE SHEETS from 50p and SAE. Catalogue 25p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. **BELL'S TELEVISION SERVICE** on service sheets of Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S. 100 King's Rd, Harrogate, N. Yorkshire. Tel: 0423 55885.

PLEASE MENTION

EVERYDAY

ELECTRONICS

WHEN REPLYING

TO

ADVERTISEMENTS

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of *Everyday Electronics* for
 insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)

[illegible]

NAME

ADDRESS

Send to: Classified Advertisement Manager

EVERYDAY ELECTRONICS

GMG, Classified Advertisements Dept., Room 2337,
King's Reach Tower, Stamford Street, London SE1 9LS.
Telephone 01-261 5942

Rate:
10p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

KITS FOR E.E. PROJECTS

VACUUM RADIO (ZB 1)	Sept 79	\$3.50
TRANSISTOR TESTER (ZB 2)	Sept 79	\$3.50
LOW POWER AUDIO AMPLIFIER WITHOUT CASE (ZB 3)	Sept 79	\$2.50
SEE LIST (ZB 4)		
WARBLING TUNER (ZB 5)	Aug 78	\$5.80
POWER SUPPLY #1 (ZB 6)	Aug 78	\$2.50
ELECTRONIC TUNING CIRCUIT (ZB 7)	Aug 78	\$2.50
SWANEE WHISTLER (ZB 8)	Aug 79	\$3.50
TRAILER FLASHER UNIT (ZB 9)	Aug 79	\$3.50
TOUCH-ON PILOT LIGHT LESS CASE (ZB 10)	Aug 79	\$1.70
SEE LIST (ZB 11)		
QUIZ REFERENCE (ZB 12)	Aug 79	\$4.00
SOLDERING IRON BIT SAVER (ZB 13)	July 79	\$1.50
CONFERENCE BOARD SLIDES 1 EXT UNIT (ZB 14)	July 79	\$2.50
VOLTAGE SPLITTER (ZB 15)	July 79	\$3.50
SEE LIST (ZB 16)		
DARKROOM TIMER (ZB 17)	July 79	\$2.50
TREMOLO UNIT (ZB 18)	June 79	\$10.00
ELECTRONIC CANARY (ZB 19)	June 79	\$10.00
MEL LOCATOR (ZB 20)	June 79	\$10.00
METER AMPLIFIER (ZB 21)	June 79	\$10.00
QUAD SIMULATOR (ZB 22)	June 79	\$10.00
INDICATOR BOARD (ZB 23)	May 79	\$15.00
ELECTRONIC DECK (ZB 24)	May 79	\$15.00
SHORT WAVE CONVERTER (ZB 25)	May 79	\$13.75
SHAYER INVERTER (ZB 26)	April 79	\$12.50
TOUCH BLEEPER (ZB 27)	April 79	\$12.50
CHOKE WARNING DEVICE (ZB 28)	April 79	\$7.50
SEE LIST (ZB 29)		
POWER SUPPLY (ZB 30)	Feb 79	\$27.00
SEE LIST (ZB 31)		
LIGHTS REMINDER FOR CAR (ZB 32)	Jan 79	\$4.00

All above lists include parts as described in article, i.e. zero board or p.s. board, etc. as needed.

TEACH-IN '80

New to electronics, then start at the beginning. All electronic components for construction of Tutor Deck and Teach-in experiments during the first six parts of the series. Lists A and B £18.50.

ALL PRICES INCLUDE V.A.T.
BARCLAY/VISA/ACCESS CARDS ACCEPTED.
MINIMUM TELEPHONE ORDERS £5.00.

T. POWELL

306 ST. PAUL'S ROAD, LONDON N.1 01-226-1489
SHOP HOURS: MON-FRI 9 a.m.-5.30 p.m.. SATURDAY 9 a.m.-4.30 p.m.



FIRST
and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation *second to none* for our catalogue—and for the service that backs it up. Experience both for yourself. Just send £1.30 with the coupon and a catalogue will come by return of post.

TREAT YOURSELF
for Xmas!

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.
Dept. EE., 234-240 London Road, Mitcham, Surrey CR4 3HD
Phone: 01-843 8422

Please write your Name and Address in block capitals

NAME

ADDRESS _____

本報刊例：第一版每行每日收費壹佰元，第二、三、四版每行每日收費捌拾元，第五至第八版每行每日收費陸拾元。長期刊登另有優惠，歡迎垂詢。

100 99 98 97 96 95 94 93 92 91 90 89 88 87 86 85 84 83 82 81 80 79 78 77 76 75 74 73 72 71 70 69 68 67 66 65 64 63 62 61 60 59 58 57 56 55 54 53 52 51 50 49 48 47 46 45 44 43 42 41 40 39 38 37 36 35 34 33 32 31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

DATE _____ DAY _____

HOME RADIO (Components) LTD., Dept. EE
234-240 London Road, Mitcham, Surrey, CR4 3ND

234-240 LONDON ROAD, WILMINGTON, SURREY CR9 3AB




POST THIS COUPON
with cheque or P.O. for £1.30

(Regn. No
London 912966)

Electronics Make a job~or hobby~of it

The opportunities in electronics, today, and for the future are limitless - throughout the world - jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics - especially for the servicing of radio, T.V. and all associated equipment - can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on the world market.

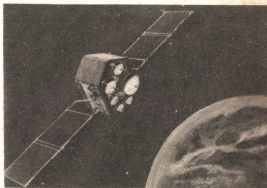We give modern training courses in all fields of electronics - practical D.I.Y. courses - courses for City and Guild exams, the Radio Amateur Licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years of experience in the subject. - Details sent without any obligation from . . .



Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

EEB1/80

Block caps please

INDEX TO ADVERTISERS

Absonglen Ltd. 62	Fringewood Electronics 48	Phonosonics 48
A.J.D. 74	Greenwel 70	Powell, T. 79
Ambit 65	George Sales, David 66	R.S.T. 73
Barrie Electronics 75	Harvelec 60	Radio Components Specialities 6
Bi-Pak 8, 9	Home Radio 79	Saxon Entertainments 53
Birkett, J. 72	I.L.P. Electronics 68, 69	Science of Cambridge 51
B.N.R.E.S. 7, 71, 80	Intertext (ICS) 75	S.L.M. Engineers 76
Butterworths 72	Maplin Electronic Supplies Ltd. 3	Stevenson, C. N. 43
Charcroft Electronics 75	Magenta Electronics 3	Swanley Electronics 60
Chromasonics 72	Maplin Electronic Supplies Ltd. 59, Cover iv	Tandy 55
Chromatronics 66	Marshall, A. 56	Technomatic 2
Collier McMillan (B.I.E.T.) 48	M.E.C.A. 76	Tempus 77
Comp Shop Cover iii	Metac 4, 5	T.K. Electronics 6
Continental Specialities Corporation 56	Watford Electronics Cover ii	TUAC 62
Crescent Radio 76	West London Direct Supplies 77	
E.D.A. 74	Wilmslow Audio 60	
Electrovalve 70		
Electroni-Kit 2		



GRANDSTAND

VIDEO ENTERTAINMENT COMPUTER

Space-age computer technology brings an amazing variety of games which you play in the comfort of your own armchair stadium at home. Get in with the action without getting out! Fun for all the family, it plays the generation game with live TV action to suit all ages. Once you've been in control of the TV, normal service might never be resumed again! It's so excitingly different ... great for parties and to make the evening when visitors call.

CARTRIDGES AVAILABLE AT £11.99

Video-cart-1: 1-player games—"Noughts and Crosses," "Shooting Gallery," "Doodle" and "Quadradoodle"
Video-cart-2: 2-player "Desert Fox" and 1-player "Shooting Gallery"
Video-cart-3: 1 and 2-player "Video Blackjack"
Video-cart-4: 1 and 2-player "Spitfire"
Video-cart-5: 2-player "Space War"
Video-cart-6: 1-player "Math Quiz 1" (addition-subtraction)

Video-cart-8: 1-player "Mind Reader"
Video-cart-9: 2-player "Drag Strip"
Video-cart-10: 1 and 2-player "Maze" and "Cat & Mouse"
Video-cart-11: 2-player "Backgammon" and "Acry-Ducy"
Video-cart-12: 2-player "Baseball"
Video-cart-13: 1 and 2-player "Torpedo Alley" and "Robot War"

Video-cart-14: 1 and 2-player "Sonar Search"
Video-cart-15: 1 and 2-player "Memory Match"
Video-cart-16: 1 and 2-player "Dodge It"
Video-cart-17: 1 and 2-player "Pinball Challenge"
Video-cart-18: 1 and 2-player "Hangman"
Video-cart-20: 1 and 2-player "Video Whirl"
Video-cart-21: 1 and 2-player "Bowling"



HITACHI PROFESSIONAL



MONITORS 9" — £129 + VAT
 12" — £199 + VAT

- **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability.
- **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved at picture center
- **Stable picture** Even played back pictures of VTR can be displayed without jittering.
- **Looping video input** Video input can be looped through with built-in termination switch.
- **External sync operation** (available as option for U and C types)
- **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

Break the language barrier £138 + VAT



At a price equivalent to learning one language, LEXICON offers you, English, Spanish, French, German, Italian and Greek. The LEX1000 comes to you with the person to person module which contains 6 languages, deluxe carrying case and a charger adaptor using its own power source which will give you 4-5 hours continuous use, and can easily be re-charged from the mains supply, wherever you may be in the world. Every additional module carries a concise and understandable instruction book. Your deluxe carrying case has room for two additional modules.

ETI TV PINBALL FEATURING BREAKOUT

CHIP & PCB £14.90 ALL OTHER PARTS ALSO EX-STOCK

MODULATORS UHF Channel 36

Standard 6 meg band width £2.25 EX-STOCK
 High Quality 8 meg band width £4.90

SHORT C12 CASSETTES FOR COMPUTER PROGRAMMES 10 for £4.00

video 100

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz & 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

Only £79 + VAT



UNIVERSAL POWER SUPPLY

Suitable for Nascom I, Nascom II, Superboard and all computers requiring these specifications.
 +5V @ 3 amps +12V @ 1 amp -5V @ 500 mills —12V @ 500 mills
 Easy to construct — complete with transformer. Our price £24.90

THE ATARI VIDEO COMPUTER SYSTEM £138 + VAT



Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges! Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous. You'll have thrill after thrill, whether you're in the thick of a dogfight, screaming around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on color TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

Cartridges now available All at £13.90 each + VAT
 Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score, Space War, Sky Diver, Air Sea Battle Codebreaker, Miniature Golf

Extra Paddle Controllers—£14.90 + VAT
 Keyboard Controllers—£16.90 + VAT

SPECIAL OFFER WHILE STOCKS LAST:
 Free extra cartridge of your choice, please state 1st, 2nd and 3rd preference.



Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CARD or AMERICAN EXPRESS number.
 CREDIT FACILITIES ARRANGED — send S.A.E. for application form.
 14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G
 Telephone: 01-441 2922 (Sales) 01-449 6596
 OPEN - 10 am - 7 pm — Monday to Saturday
 NOW OPEN ALL DAY SUNDAY — For Shop Sales Only
 Close to New Barnet BR Station — Moorgate Line.



MAPLIN



This superb organ – build the first working section for just over £100. Full specification in our catalogue.



Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.




61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 250 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

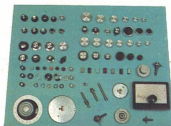Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!




The 3800 synthesiser build it (leaving at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



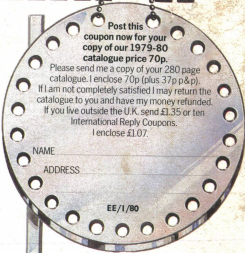Speakers from 1½ inch to 15 inch; megaphone. PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:—
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff-on-Sea, Essex.
(Closed on Monday).
Telephone: Southend (0702) 554000.